


ECG Monitor

**Single Lead Analog
Heart Rate Monitor**

ECG Waveform

ECG Monitor


ECG Waveform

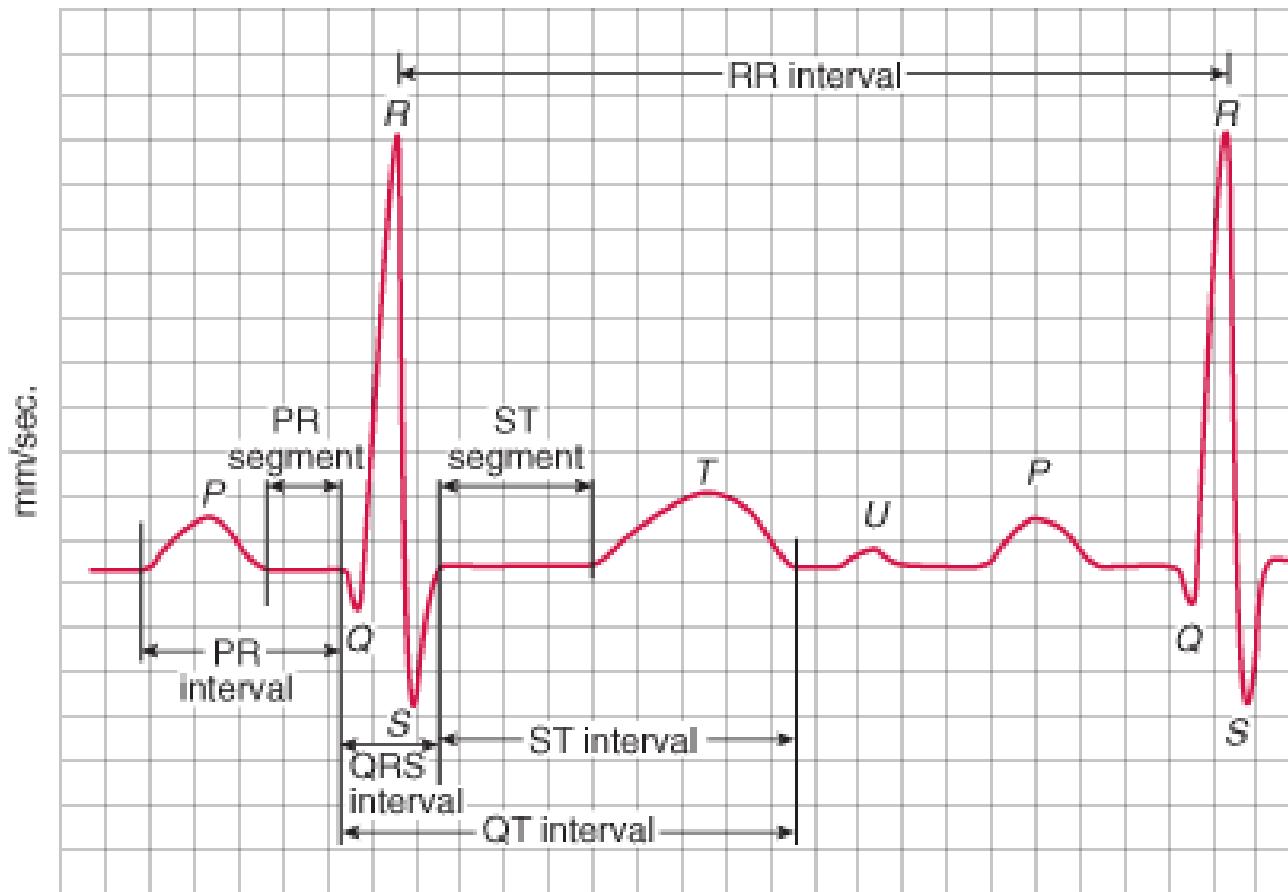

Wave	Amplitude (mV)	Duration (sec)
P	0.25	0.12 – 0.22 (P – R interval)
R	1.06	0.07 – 0.1
T	0.1 – 0.5	0.05 – 0.15 (S – T segment)
QRS Complex	-	0.09

ECG Monitor

ECG Waveform

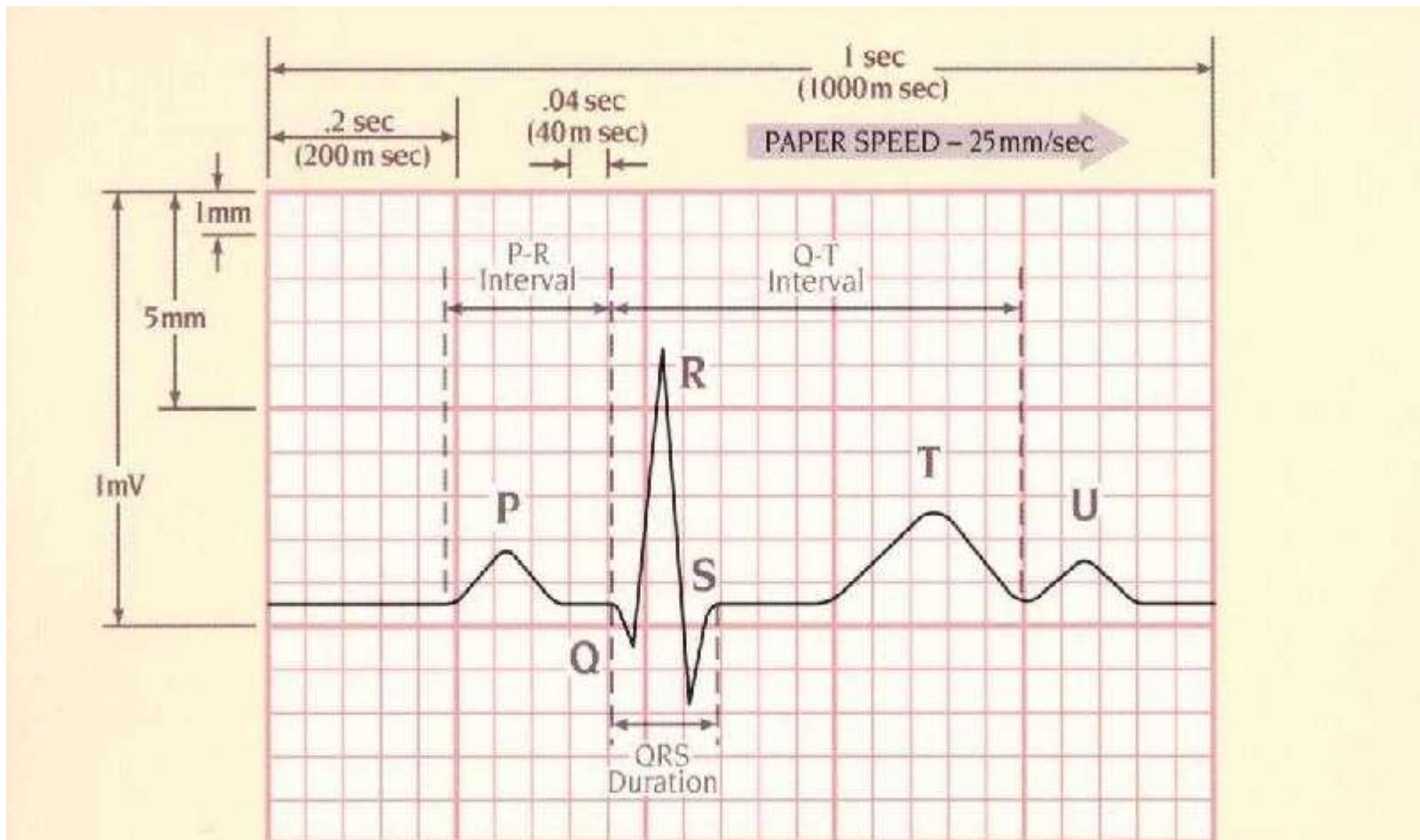

**VERTICAL
AXIS**

1 Small Square = 1mm (0.1mV)
1 Large Square = 5mm (0.5mV)
2 Large Squares = 1mV

**HORIZONTAL
AXIS**


1 Small Square = .04 sec (40 m sec)
1 Large Square = .2 sec (200 m sec)
5 Large Squares = 1 sec (1000 m sec)

ECG Monitor


ECG Waveform

[Electrocardiography - Wikipedia](#)

Animation of a normal ECG wave

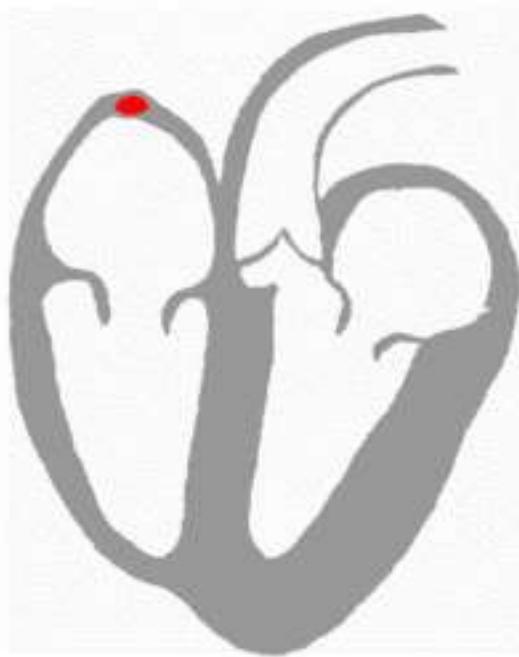

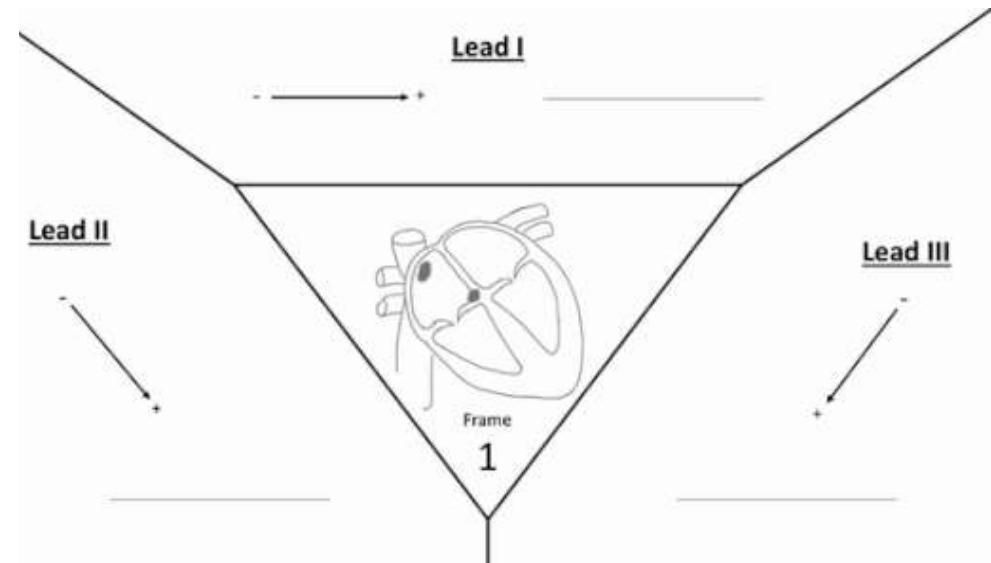Formation of limb waveforms during a pulse




ECG Monitor

ECG Leads

Table 2. Definition of ECG Leads

Lead type	Electrodes used	Definition
Bipolar or limb leads (Einthoven)	LA, RA, LL, RL	$I = LA - RA$ $II = LL - RA$ $III = LL - LA$
Augmented (Goldberger)	LA, RA, LL, RL	$aV_R = RA - 0.5(LA + LL)$ $aV_L = LA - 0.5(LL + RA)$ $aV_F = LL - 0.5(LA + RA)$
Unipolar chest leads (Wilson)	V ₁ , V ₂ , V ₃ , V ₄ , V ₅ , V ₆	$V_1 = v_1 - (LA + RA + LL)/3$ $V_2 = v_2 - (LA + RA + LL)/3$ $V_3 = v_3 - (LA + RA + LL)/3$ $V_4 = v_4 - (LA + RA + LL)/3$ $V_5 = v_5 - (LA + RA + LL)/3$ $V_6 = v_6 - (LA + RA + LL)/3$
Orthogonal vector leads (Frank)	I, E, C, A, M, H, F	$X = 0.610A + 0.171C - 0.781I$ $Y = 0.655F + 0.345M - 1.000H$ $Z = 0.133A + 0.736M - 0.264I - 0.374E - 0.231C$


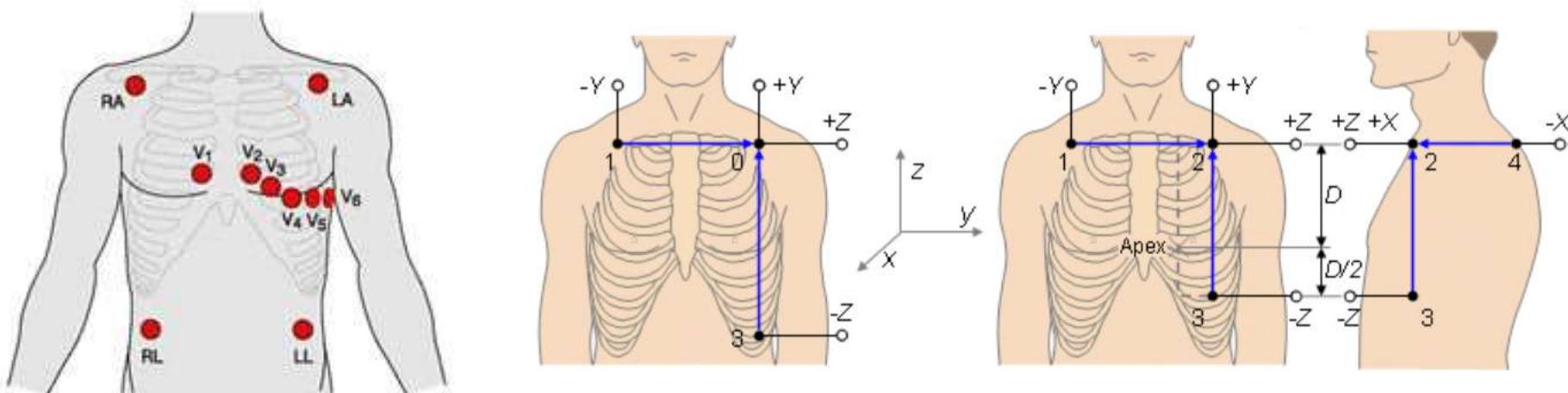


ECG Monitor

ECG Leads

[Electrocardiography - Wikipedia](#)

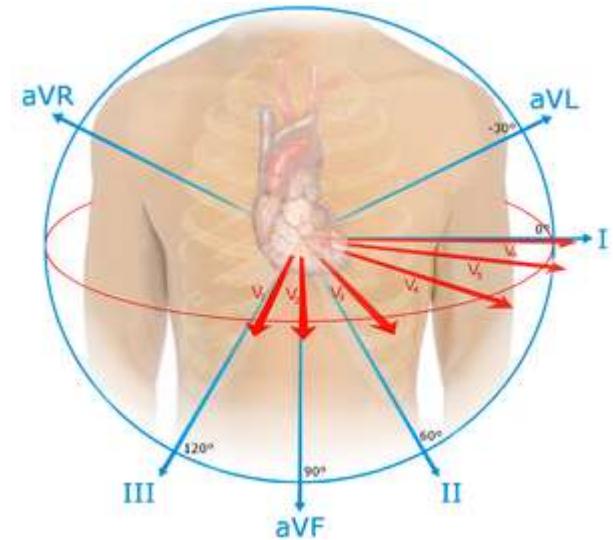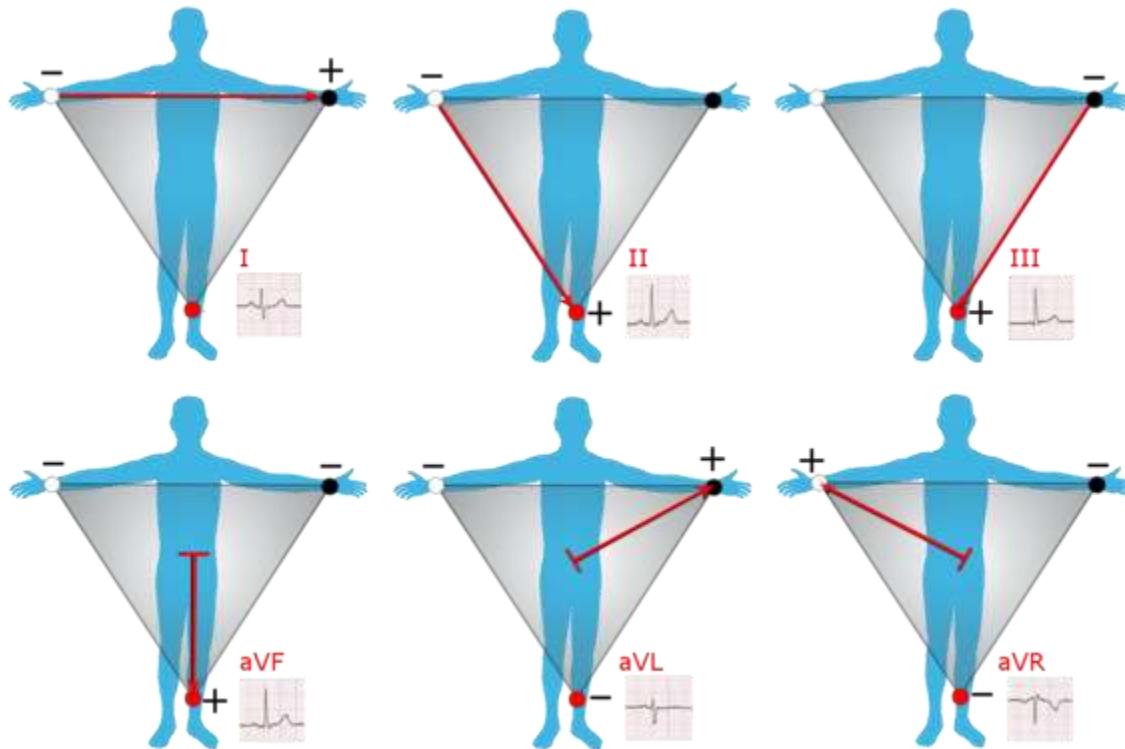The limb leads and augmented limb leads (Wilson's central terminal is used as the negative pole for the latter in this representation)




ECG Monitor

ECG Leads

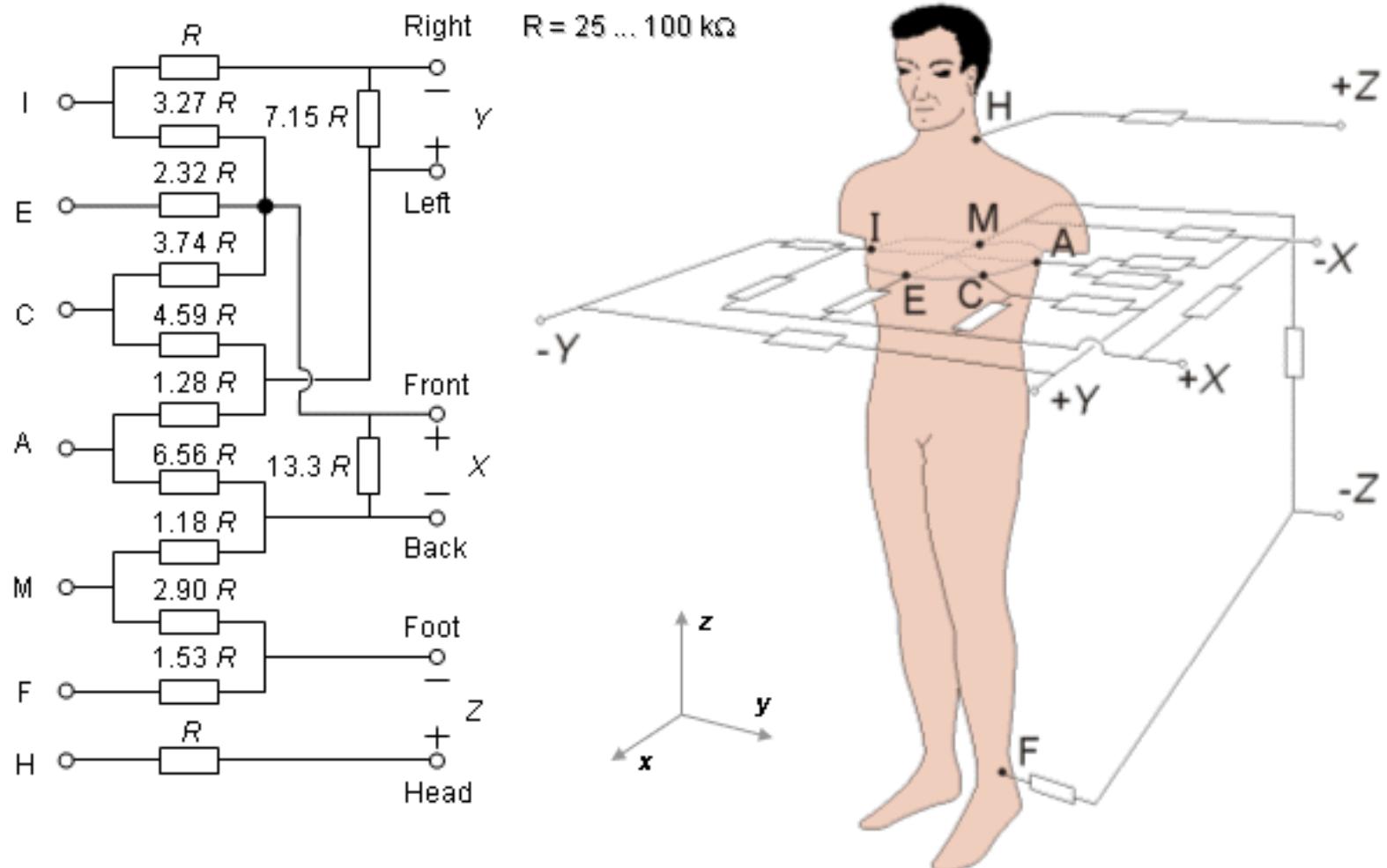
[16. Vectorcardiographic Lead Systems \(bem.fi\)](#)

The lead matrix of the Frank VCG-system. The electrodes are marked I, E, C, A, M, F, and H, and their anatomical positions are shown. The resistor matrix results in the establishment of normalized x-, y-, and z-component lead vectors, as described in the text.




ECG Monitor

ECG Espectra

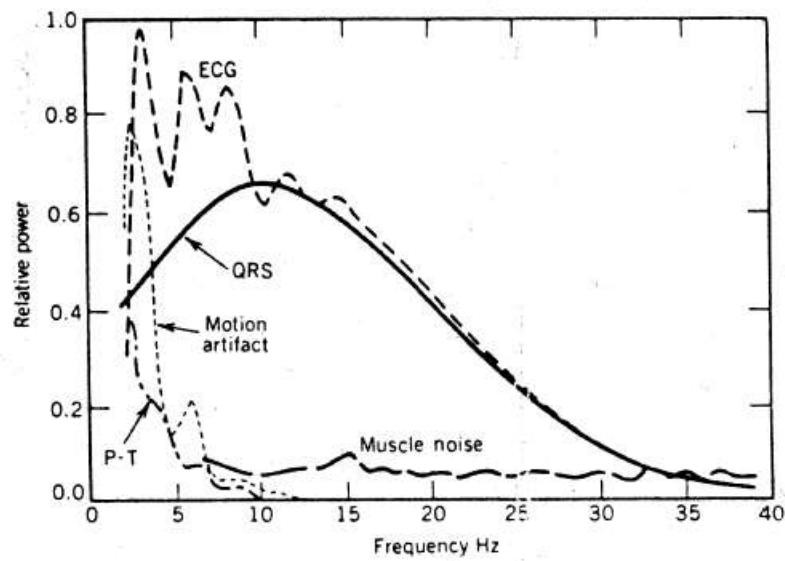

(a)

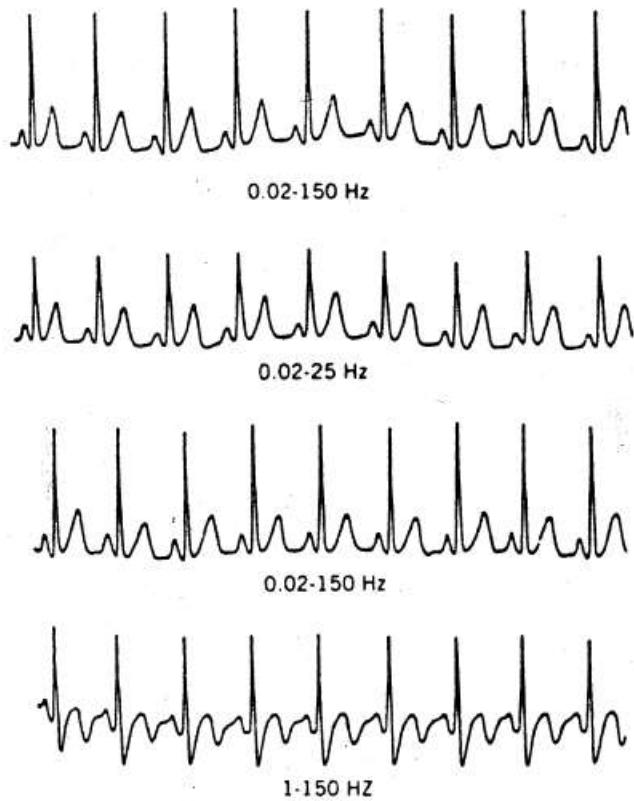

(b)

ECG Monitor

Introduction to Electrocardiograph, Maxim AN4693

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4693>

Overview

An electrocardiogram (ECG or EKG) is the measurement and graphic representation, with respect to time, of the electrical signals associated with the heart muscles. Applications of an ECG range from monitoring heart rate to the diagnosis of specific heart conditions. The basics of ECG measurement are the same for all applications, but the details and requirements for electrical components vary greatly. Electrocardiographs, or ECG devices, range from portable handheld units costing less than \$200, to units that cost over \$5,000 and are the size of facsimile machines. An ECG may even be embedded in a separate piece of equipment, such as a patient monitor or an automatic external defibrillator (AED).

All ECGs pick up heart signals through electrodes connected externally to specific locations on the body. The heart signals are generated by the body and have amplitudes of a few millivolts. The specific locations of the electrodes allow the heart's electrical activity to be viewed from different angles, each of which is displayed as a channel on the ECG printout. Each channel represents the differential voltage between two of the electrodes, or the differential voltage between one electrode and the average voltage from several electrodes. The different combinations of electrodes allow more channels to be displayed than there are electrodes. The channels are commonly referred to as "leads," so a 12-lead ECG device has 12 separate channels displayed graphically. The number of leads varies from 1 to 12 depending on the application. Unfortunately, the wires running to the electrodes are occasionally referred to as leads as well. This can create confusion, as a 12-lead (12-channel) ECG device only requires 10 electrodes (10 wires), so be careful of the context in which "lead" is used.

In addition to the biological signals, most ECGs also detect two manmade signals. The most important of these signals comes from implanted pacemakers and is referred to simply as "pace." The pace signal is relatively short, tens of microseconds to a couple of milliseconds, with an amplitude ranging from a few millivolts to nearly a volt. Often, the ECG must detect the presence of a pace signal while simultaneously preventing it from distorting the signals from the heart.


The second manmade signal is for detecting "lead-off," which is when an electrode is making poor electrical contact. Many ECG devices must provide an alert when this poor contact occurs. Therefore, the ECG device generates a signal to measure the impedance between the electrode and the body for detecting a lead-off occurrence. The measurement may be AC, DC, or both. In some ECG devices, respiration rate is also detected by analyzing the impedance from the lead-off measurement. Lead-off detection is continuous and should not interfere with accurate measurement of the heart signals.

ECG Monitor

Introduction to Electrocardiograph, Maxim AN4693

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4693>

Functional Block Diagram 2010

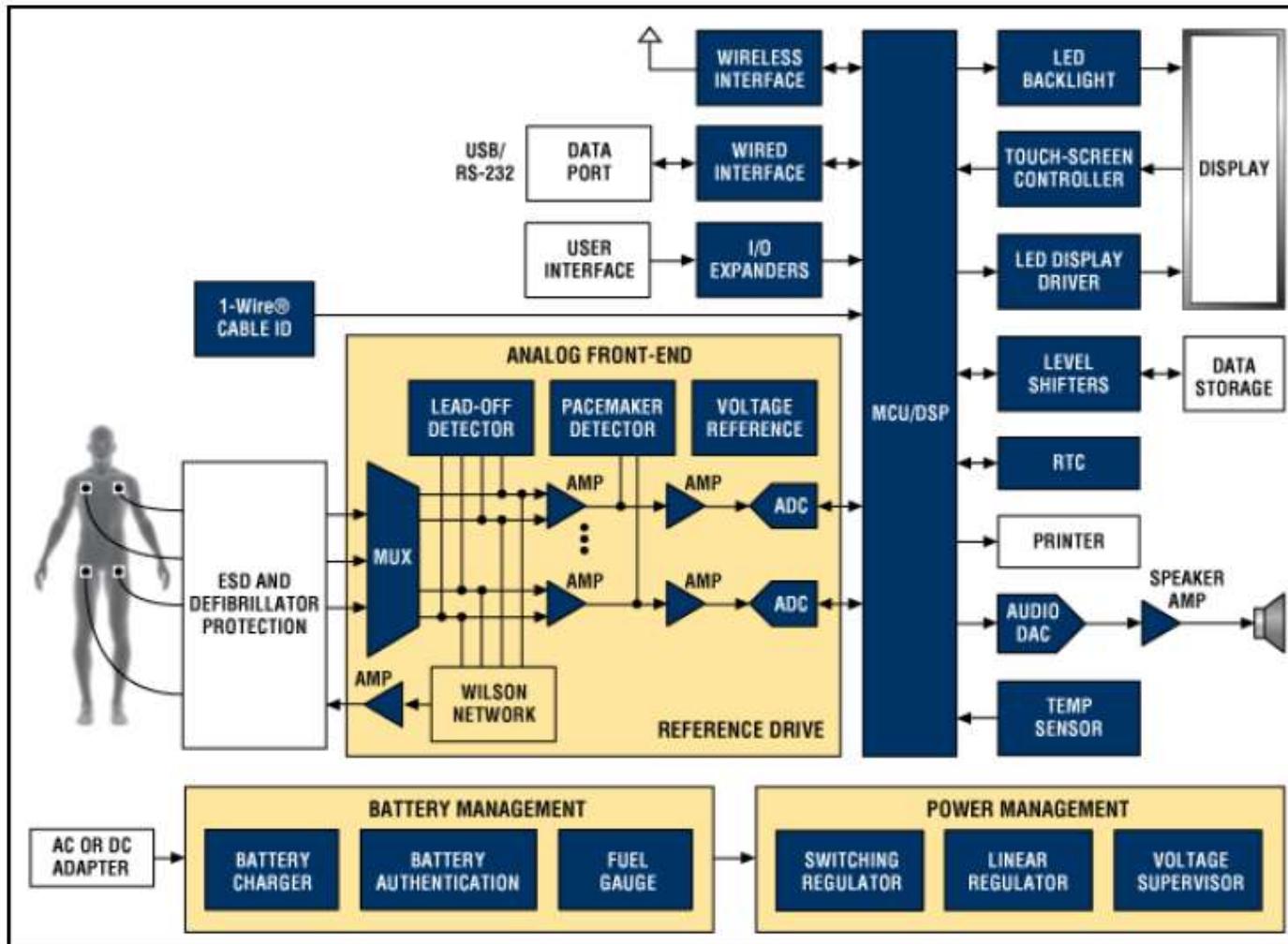

Full-featured ECG functional block diagram. For a list of Maxim's recommended solutions for an ECG design, please go to: www.maximintegrated.com/ECG.

ECG Monitor

Introduction to Electrocardiograph, Maxim AN4693

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4693>

Features

Understanding the required electronic components for an ECG is easier if it is separated into the analog front-end (AFE), which digitizes these signals, and "the rest of the system," which analyzes, displays, stores and transmits the data. AFEs share the same basic requirements, but differ in the number of leads, fidelity of signal, interference that must be rejected, and so on. The rest of the system differs more radically according to whether features are or are not present. Typical features include a built-in display, the ability to print a hard copy, a radio-frequency (RF) link, and rechargeable batteries.

Number of Leads

One of the most obvious features is the number of leads. Some ECGs have only one lead; the maximum number of leads is usually 12. The most common 12-lead ECGs require 10 electrodes. Nine of the electrodes pick up electrical signals and the tenth electrode, on the right leg (RL), is electrically driven by the ECG circuit to reduce the common-mode voltage. The nine input electrodes are: left arm (LA), right arm (RA), left leg (LL), and six precordial (chest) electrodes (V1 through V6). Each lead, or view of the heart, is the differential voltage between one electrode and another electrode or group of electrodes. When electrodes are grouped, their voltage is averaged. RA, LA, and LL are averaged for six of the leads (views) and become one side of the differential pair, while V1 to V6 are individually used for the other side of the differential pair. Three of the leads measure RA, LA, and LL against the average of the other two electrodes. The remaining three leads come from RA, LA, and LL measured as individual pairs. The six leads based on RA, LA, and LL contain duplicate information, but display it in different ways. Because the information is redundant, it is not necessary to measure all six leads. Some of the channels can be calculated by a DSP as it analyzes data from the measured channels.

While the 12-lead system described here is the most common, it is not the only one. In addition, 12-lead ECGs are capable of operating as a 5-, 3-, or 1-lead systems. The key point here is the need for a switch matrix and averaging circuits when more than one lead is required.

ECG Monitor

Introduction to Electrocardiograph, Maxim AN4693

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4693>

Analog Front-End (AFE)

The primary function of the AFE is to digitize the heart signals. This process is complicated by the need to reject interference from strong RF sources, pace signals, lead-off signals, common-mode line frequency, signals from other muscles, and electrical noise. In addition, the millivolt-level ECG signal can be sitting atop a DC offset that is hundreds of millivolts, with channel-to-channel common-mode voltages differing by over a volt. The electrical connections to the patient must not create a shock hazard or interfere with other medical equipment that may be connected to the patient. The frequency range of interest for the ECG varies somewhat with the application, but is usually around 0.05Hz to 100Hz.

Secondary functions of the AFE are the detection of pace signals, lead-off detections, respiration rate, and patient impedance. All of this is done on several channels simultaneously or near simultaneously. In addition, most ECG devices are required to recover quickly from a defibrillation event, which can saturate the front-end and charge capacitors. This creates a long recovery time for capacitively coupled circuits.

AFE Architectures

The AFE architecture has a large impact on the features. The brute force architecture described below provides high fidelity over a wide frequency range due to its high-resolution, high-conversion-rate ADC. The lack of capacitive coupling and use of a DAC for RL drive enables it to recover very quickly from a defibrillation or RF event. Digitizing the pace signal allows pace analysis that reduces the number of false pace indications and may even detect faults in the pacemaker or its connections. On the down side, the brute force system requires expensive components and uses a great deal of power. In contrast, the minimal AFE features low cost and long battery life, but little else.

ECG Monitor

Introduction to Electrocardiograph, Maxim AN4693

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4693>

AFE Capabilities of Various ECG Applications

Capabilities	Patient Monitor	Diagnostic	Telemetry	Holter	AED	Consumer
High RF immunity	U	U	S	S	S	N
Minimum frequency (Hz)	0.05	0.05	0.1	0.1	0.5	0.5
Maximum frequency (Hz)	500	500	50	150	40	40
ADC sample rate (sps)	1k to 100k	1k to 100k	1024	1024	250+	250+
ADC resolution (bits)	12 to 20	12 to 20	12 to 20	12 to 20	12	10 to 12
Right leg drive	A	A	S	S	N	S
Pace	A	A	U	U	U	S
Lead-off detection	A	A	U	U	A	S
Respiration	U	S	S	S	S	N
Impedance	S	S	S	S	U	N
Defibrillation compatible	A	U	A	U	A	S

A = always, U = usually, S = sometimes, N = never

ECG Monitor

Introduction to Electrocardiograph, Maxim AN4693

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/4693>

Brute force and DSP AFEs. The measurement requirements of an ECG can be met by using the brute force of powerful ADCs to simultaneously digitize the signals on all nine electrodes to a noise-free resolution of about 20 bits at a rate of 200ksps. A digital signal processor (DSP) can then be used to calculate the signal for each lead, isolate the pace signal, isolate the lead-off/respiration signals, and filter out unwanted frequencies. The DSP also calculates values for a digital-to-analog converter (DAC) driving the RL electrode. This AFE method requires the analog-to-digital (ADC) channels to be tightly matched and may require buffering to isolate the ADC sampling capacitance from the relatively high-impedance electrodes. While this approach may meet the measurement requirement, it will not meet the cost or power consumption requirements of most applications.

Minimal AFEs. At the other end of the AFE features spectrum is the 1-lead, consumer-grade ECG. The AFE circuit of this device capacitively couples the input signals to a lowpass differential amplifier that is followed by a 10-bit, 120sps ADC. Capacitively coupling the inputs eliminates DC-offset issues, and lowpass filtering removes the pace signal. There is no common-mode voltage, because the device is battery powered and has only one channel.

Typical ECG AFEs. The circuits in most ECG devices lie between the above two extremes. Instrumentation amplifiers (IAs) are used to reduce the common-mode voltage, eliminate common-mode noise such as line frequency, and provide a buffer for the ADC's sampling capacitance. Filters after the IA remove the pace and lead-off signals before the heart signals are digitized by the ADC. In some cases, the heart signal and its DC offset are directly digitized by a high-resolution ADC. In other cases, highpass filtering or DACs are used to remove the DC offset so that the heart signal can be amplified and digitized by a lower resolution ADC, typically 12 bits. A separate ADC can be used for each lead, or one ADC can be multiplexed to digitize multiple leads. Multiplexing the ADC can cause a slight time skew between channels. How objectionable this skew is depends on the application. If pace detection is needed, the pace signal is picked off by a highpass filter, amplified, and detected by a comparator circuit.

ECG Monitor

Analog Front End (AFE)

<https://www.analog.com/media/en/technical-documentation/data-sheets/AD8233.pdf>



AD8233

FUNCTIONAL BLOCK DIAGRAM

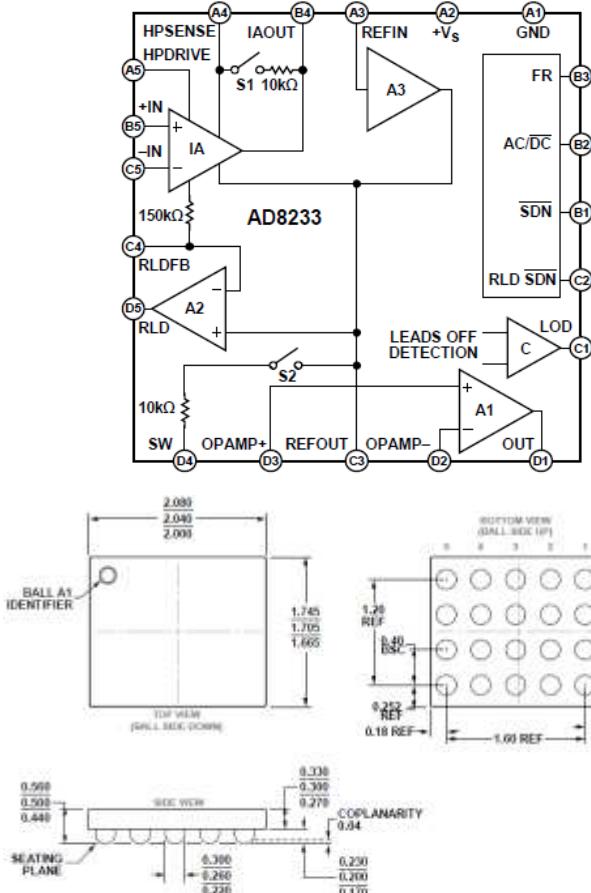


Figure 78. 20-Ball, Backside-Coated, Wafer Level Chip Scale Package (WLCSP) (CB-20-73)

Dimensions shown in millimeters

ES SHOWN IN DC LEADS OFF DETECTION POSITION AND FAST RESTORE DISABLED

\perp = REFOUT

*ALL SWITCHES SHOWN IN DC LEADS OFF DETECTION POSITION AND FAST RESTORE DISABLED
⊥ = REFOUT

Figure 50. Simplified Schematic Diagram

ECG Monitor

Analog Front End (AFE)



AD8233

FEATURES

- Fully integrated, single-lead electrocardiogram (ECG) front end
- Low quiescent supply current: 50 μ A (typical)
- Leads on/off detection while in shutdown (<1 μ A)
- Common-mode rejection ratio: 80 dB (dc to 60 Hz)
- 2 or 3 electrode configurations
- High signal gain ($G = 100$) with dc blocking capabilities
- 2-pole adjustable high-pass filter
- Accepts up to ± 300 mV of half cell potential
- Fast restore feature improves filter settling
- Uncommitted op amp
- 3-pole adjustable low-pass filter with adjustable gain
- Integrated right leg drive (RLD) amplifier with shutdown
- Single-supply operation: 1.7 V to 3.5 V
- Integrated reference buffer generates virtual ground
- Rail-to-rail output
- Internal RFI filter
- 8 kV human body model (HBM) ESD rating
- Shutdown pin
- 2 mm x 1.7 mm WLCSP

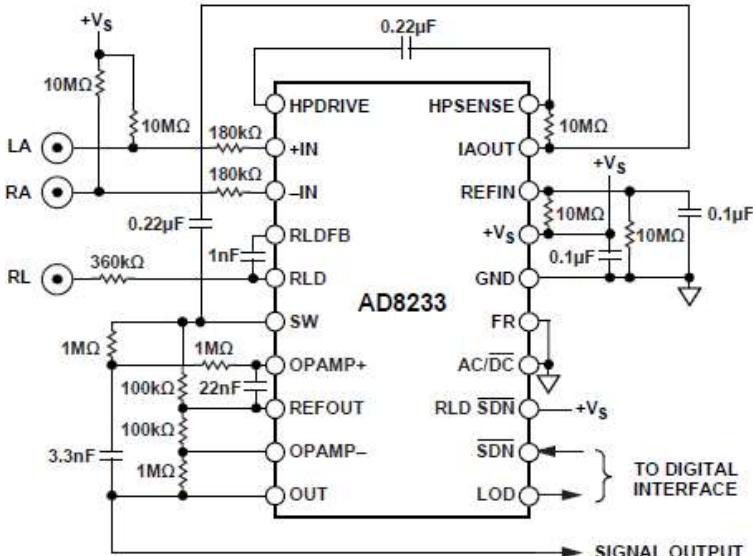


Figure 72. Circuit for HRM at Hands

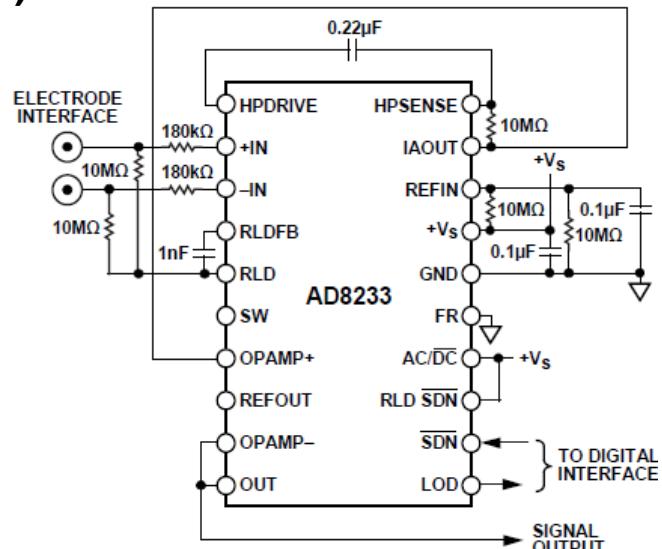


Figure 70. Circuit for HRM Next to the Heart

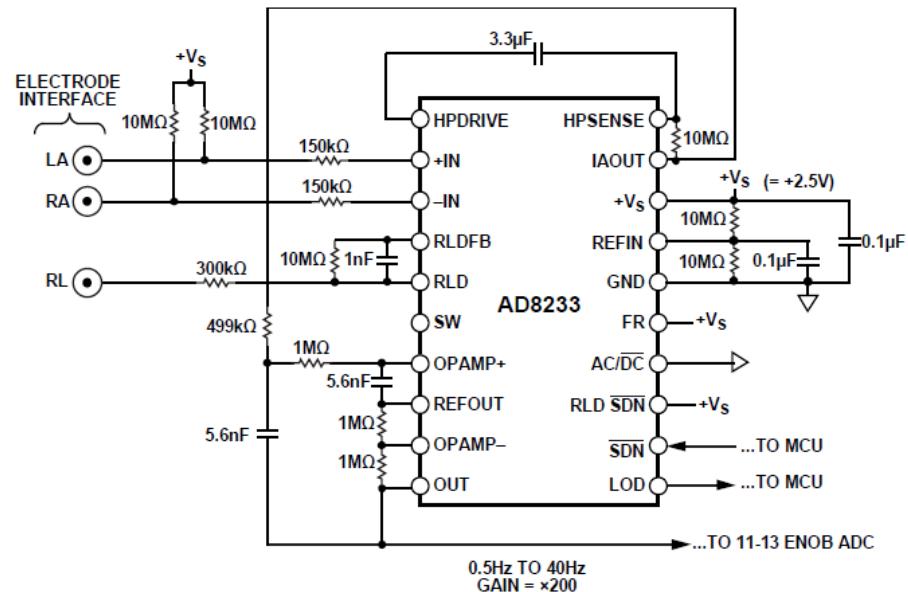



Figure 75. Holter Monitor Circuit



AD8233

ECG Monitor Analog Front End (AFE)

Example Schematic

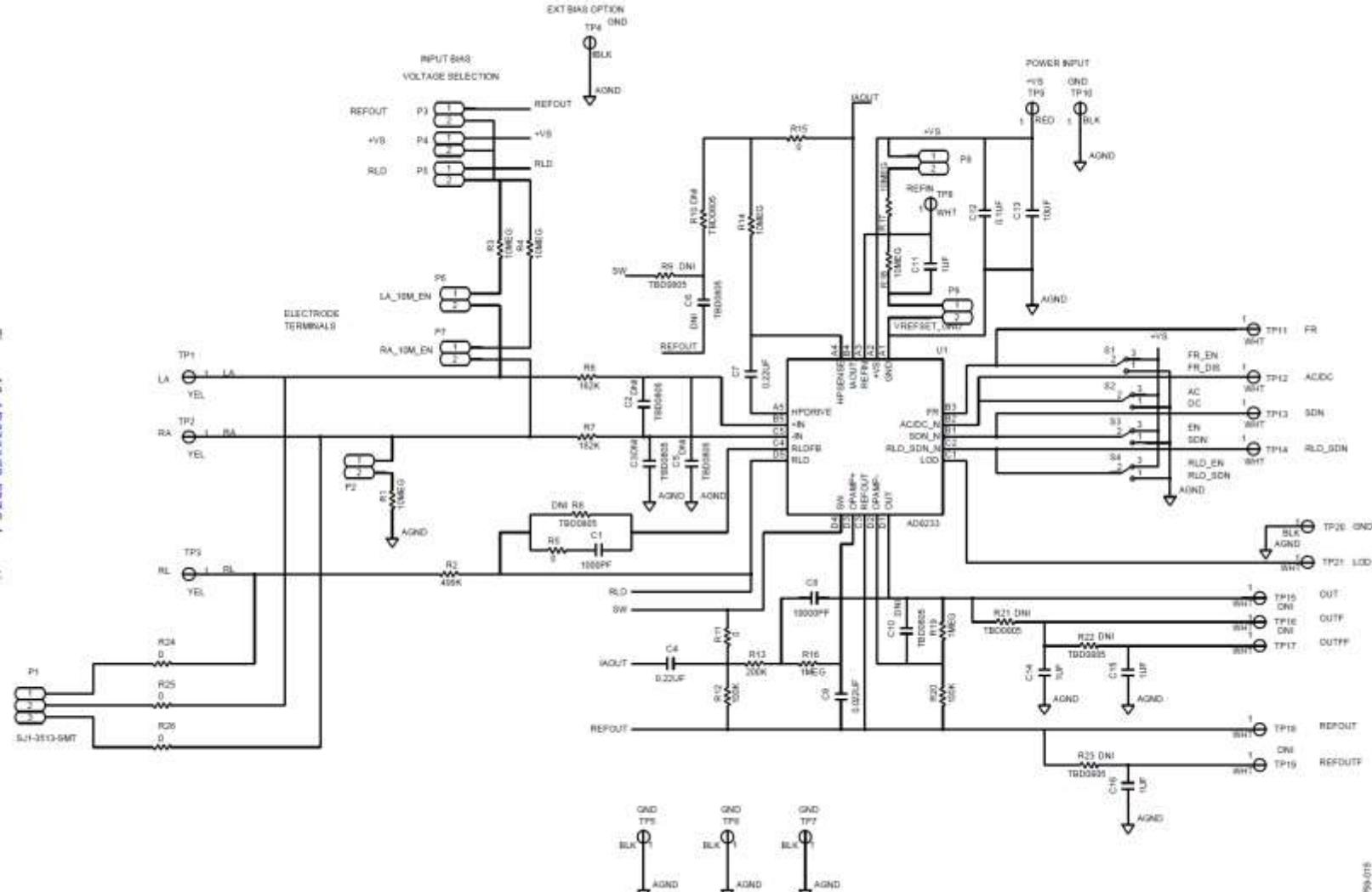

ECG Monitor

Analog Front End (AFE)

<https://www.analog.com/media/en/technical-documentation/data-sheets/AD8233.pdf>



AD8232

FUNCTIONAL BLOCK DIAGRAM

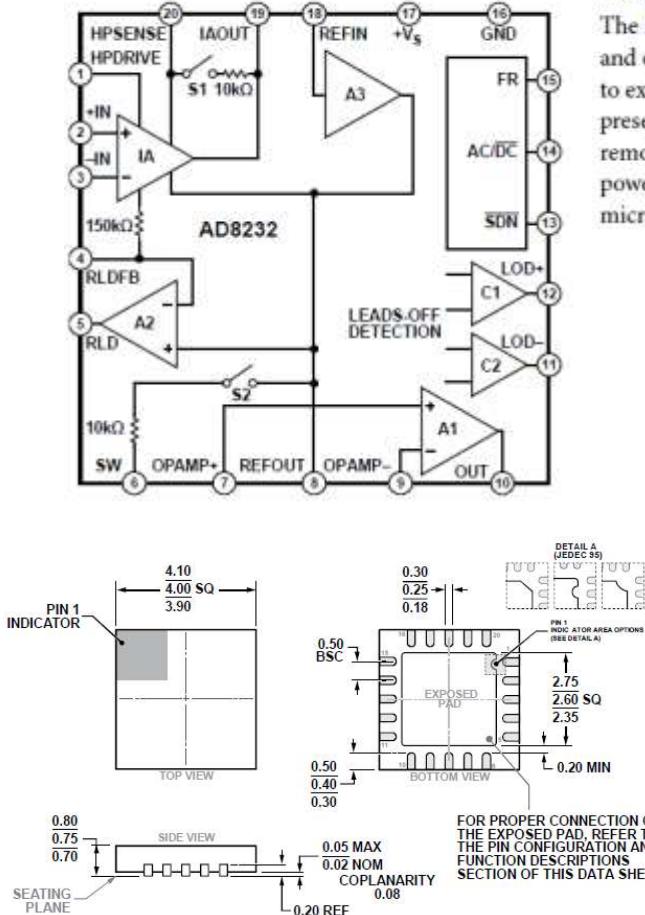


Figure 69. 20-Lead Lead Frame Chip Scale Package [LFCSP]
4 mm × 4 mm Body and 0.75 mm Package Height
(CP-20-8)

Dimensions shown in millimeters


Single-Lead, Heart Rate Monitor Front End

GENERAL DESCRIPTION

The AD8232 is an integrated signal conditioning block for ECG and other biopotential measurement applications. It is designed to extract, amplify, and filter small biopotential signals in the presence of noisy conditions, such as those created by motion or remote electrode placement. This design allows for an ultralow power analog-to-digital converter (ADC) or an embedded microcontroller to acquire the output signal easily.

The AD8232 can implement a two-pole high-pass filter for eliminating motion artifacts and the electrode half-cell potential. This filter is tightly coupled with the instrumentation architecture of the amplifier to allow both large gain and high-pass filtering in a single stage, thereby saving space and cost.

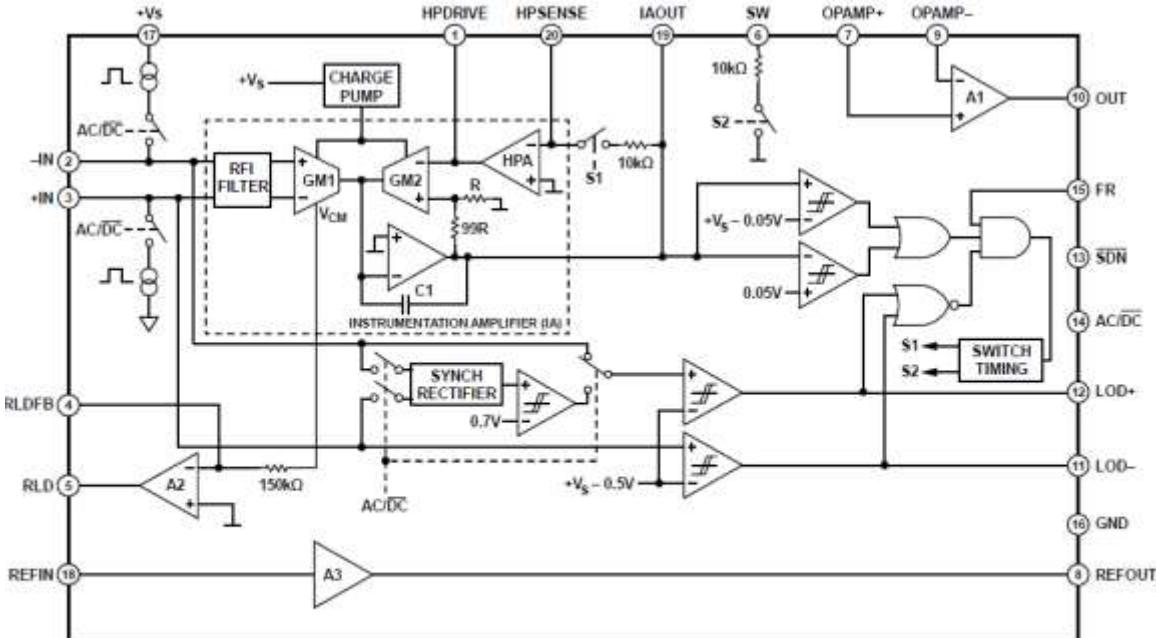An uncommitted operational amplifier enables the AD8232 to create a three-pole low-pass filter to remove additional noise. The user can select the frequency cutoff of all filters to suit different types of applications.



ALL SWITCHES SHOWN IN DC LEADS-OFF DETECTION POSITION AND FAST RESTORE DISABLED
 \perp = REFOUT

Figure 45. Simplified Schematic Diagram



ECG Monitor

Analog Front End (AFE)

HIGH-PASS FILTERING

The [AD8232](#) can implement higher order high-pass filters. A higher filter order yields better artifact rejection but at a cost of increased signal distortion and more passive components on the printed circuit board (PCB).

Two-Pole High-Pass Filter

A two-pole architecture can be implemented by adding a simple ac coupling RC at the output of the instrumentation amplifier, as shown in Figure 55.

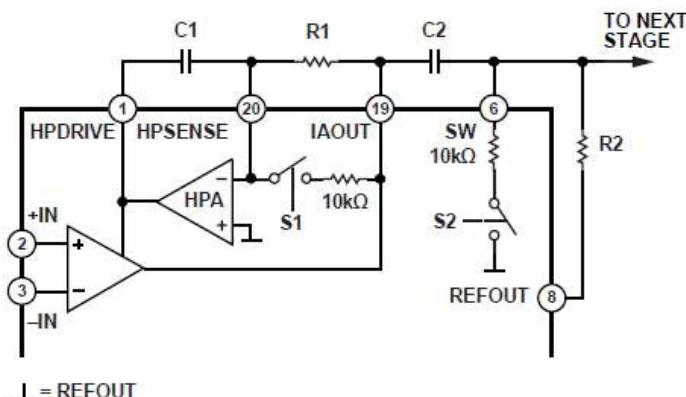


Figure 55. Schematic for a Two-Pole High-Pass Filter

10866-053

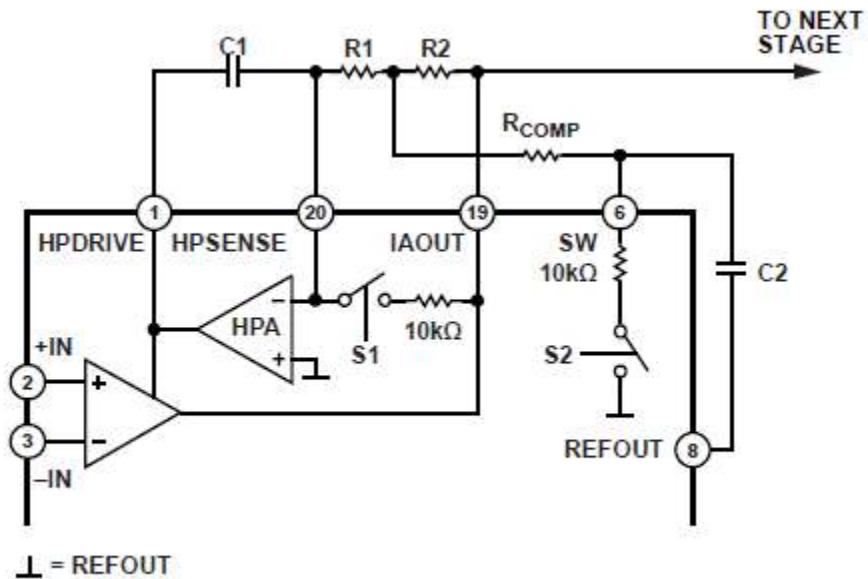


Figure 56. Schematic for an Alternative Two-Pole High-Pass Filter

10866-155

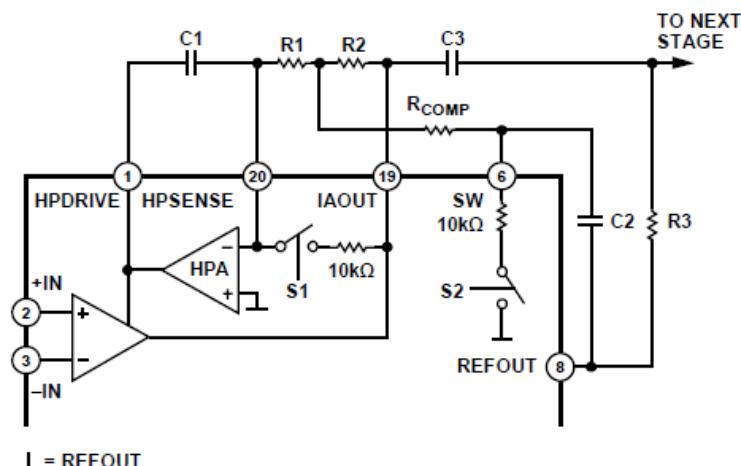


Figure 57. Schematic for a Three-Pole High-Pass Filter



ECG Monitor

Analog Front End (AFE)

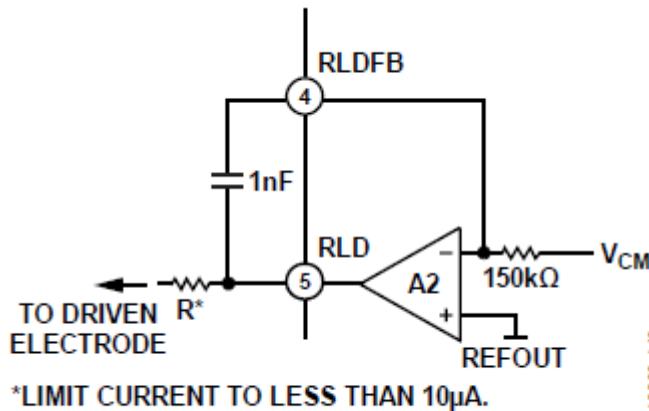


Figure 46. Typical Configuration of Right-Leg Drive Circuit

10966-146

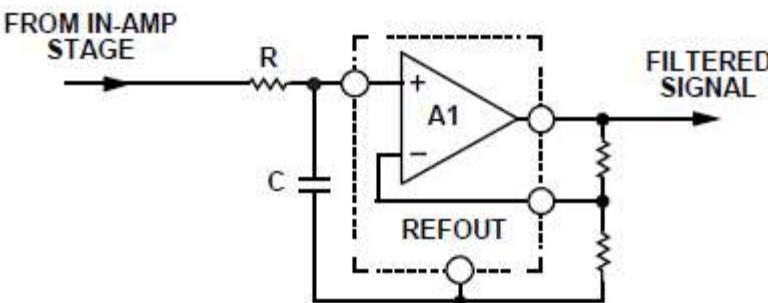


Figure 59. Schematic for a Single-Pole Low-Pass Filter and Additional Gain

10868-158

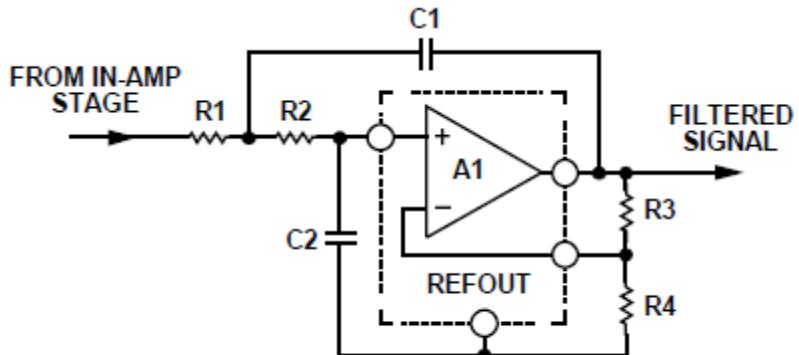


Figure 60. Schematic for a Two-Pole Low-Pass Filter

ECG Monitor

Analog Front End (AFE)



AD8232

HEART RATE MEASUREMENT NEXT TO THE HEART

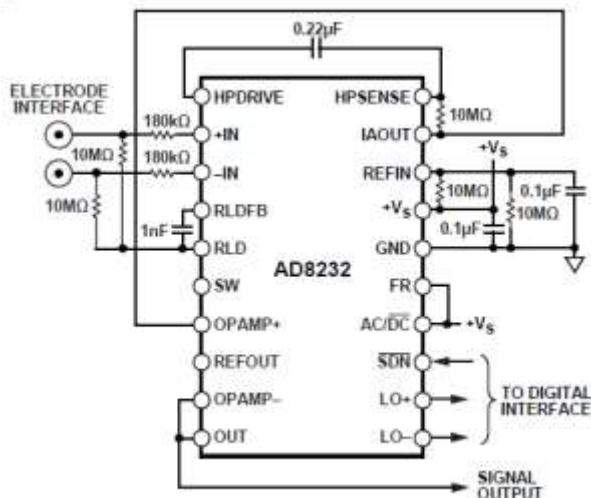


Figure 62. Circuit for Heart Rate Measurement Next to Heart

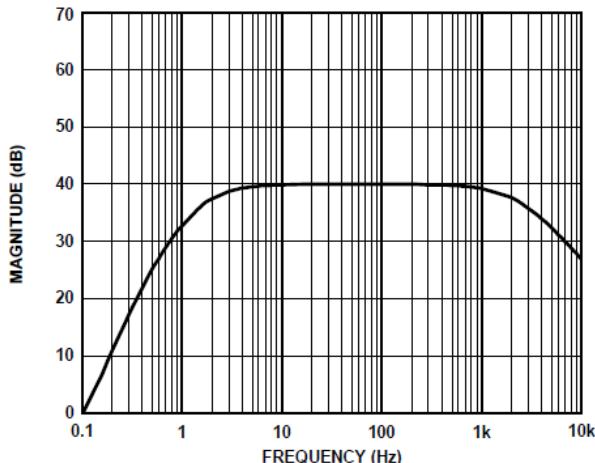


Figure 63. Frequency Response for HRM Next to Heart Circuit

EXERCISE APPLICATION: HEART RATE MEASURED AT THE HANDS

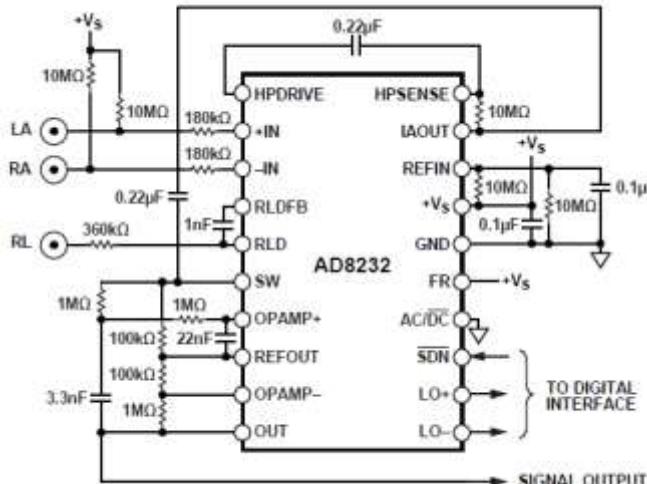


Figure 64. Circuit for Heart Rate Measurement at Hands

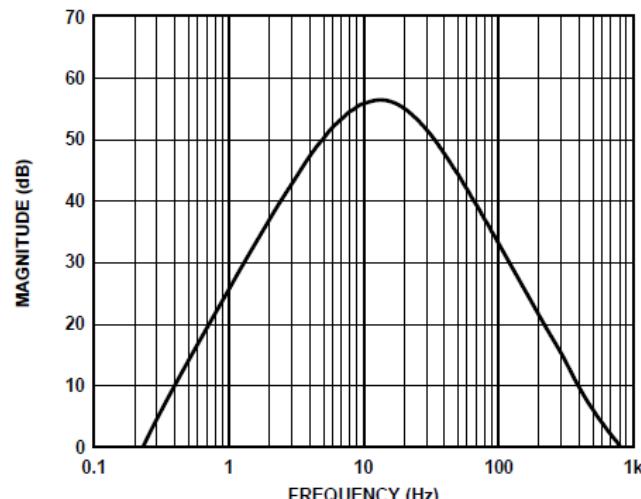


Figure 65. Frequency Response for HRM Circuit Taken at the Hands

ECG Monitor

Analog Front End (AFE)



CARDIAC MONITOR CONFIGURATION

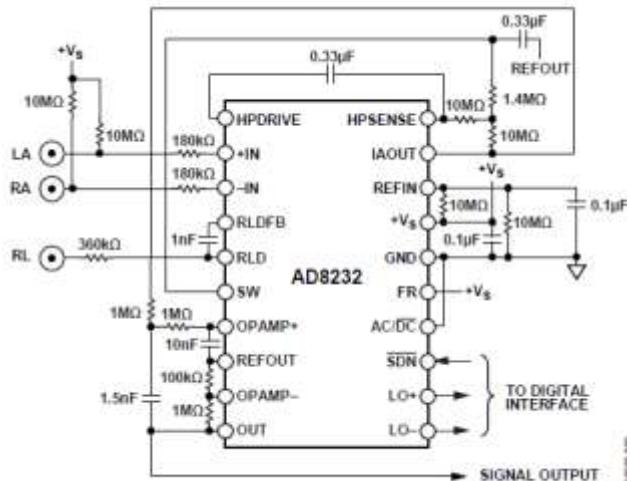


Figure 66. Circuit for ECG Waveform Monitoring


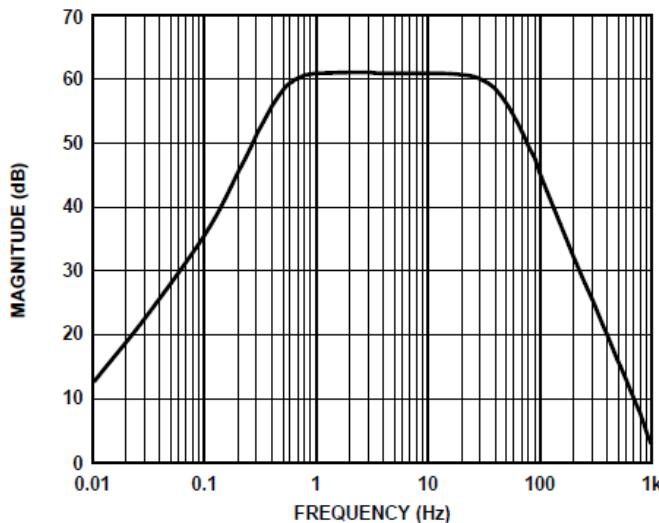


Figure 67. Frequency Response of Cardiac Monitor Circuit

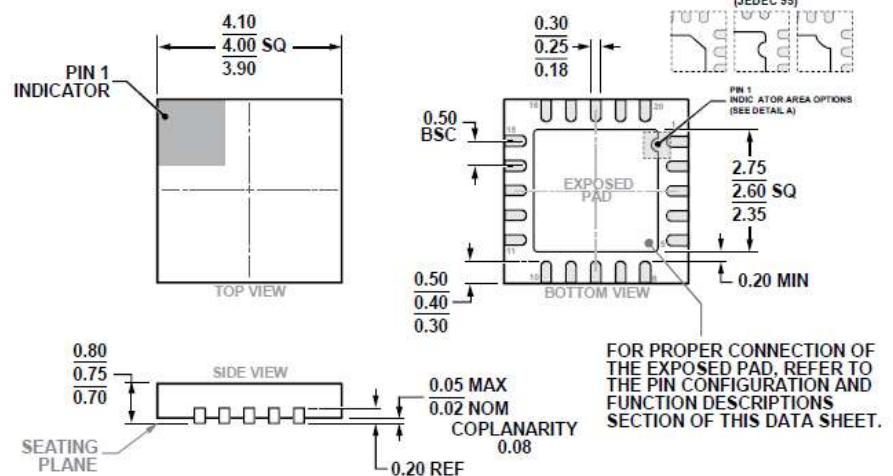

COMPLIANT TO JEDEC STANDARDS MO-220-WGGD-11.

Figure 69. 20-Lead Lead Frame Chip Scale Package [LFCSP]
4 mm × 4 mm Body and 0.75 mm Package Height
(CP-20-8)


Dimensions shown in millimeters



AD8232

Cardiac monitor Configuration

MIKROE ECG 5
SparkFun AD8232

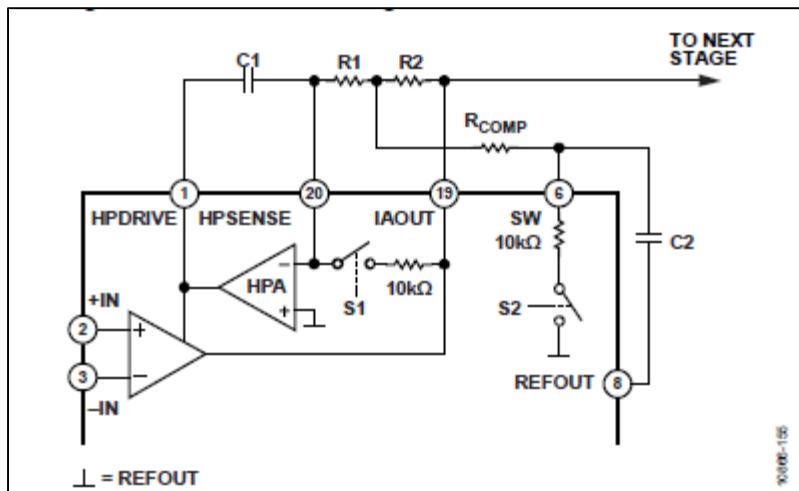

Filtro pasa alto de dos polos para el AD8232

$$R1 = R2 \geq 100 \text{ k}\Omega$$

$$C1 = C2$$

$$R_{COMP} = 0.14 \times R1$$

The cutoff frequency is located at

$$f_c = \frac{10}{2\pi\sqrt{R1 C1 R2 C2}}$$

Formulas del filtro pasa alto

Tanto Sparkfun como MIKROE emplean:

$$R1 = R2 = 10 \text{ M}\Omega$$


$$C1 = C2 = 0.33 \mu\text{F}$$

$$R_{comp} = 1,4 \text{ M}\Omega$$

$$fc = 0,48 \text{ Hz}$$

$$\text{INA DC Gain} = \text{Gain}_{\text{INA}} = 100$$
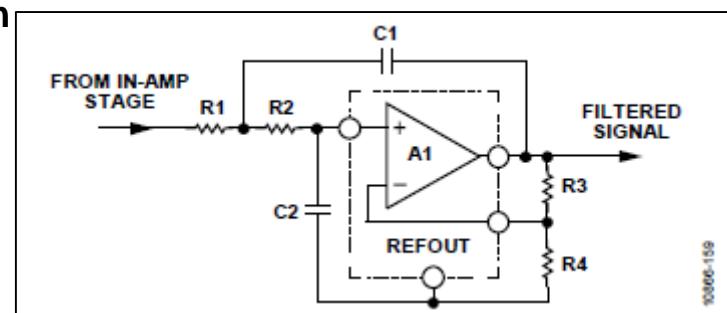
$$\begin{aligned} \text{Total Gain} &= \text{Gain}_{\text{INA}} \times \text{Gain}_{\text{LP}} \\ &= 100 \times 11 = 1100 \\ &= 60.83 \text{ dB} \end{aligned}$$



Filtro pasa bajo de dos polos para el AD8232

$$fc = 1/(2\pi\sqrt{R1 C1 R2 C2})$$

$$\text{Gain} = 1 + R3/R4$$

$$Q = \frac{\sqrt{R1 \times C1 \times R2 \times C2}}{R1 \times C2 + R2 \times C1 + R1 \times C1(1 - \text{Gain})}$$

Formulas del filtro pasa bajo

Tanto Sparkfun como MIKROE emplean:

$$R1 = R2 = R3 = 1 \text{ M}\Omega$$

$$R4 = 100 \text{ k}\Omega$$

$$C1 = 1,5 \text{ nF}$$

$$C2 = 10 \text{ nF}$$

$$fc = 41 \text{ Hz}$$

$$\text{Gain}_{\text{LP}} = 11$$

$$Q = 0,77$$

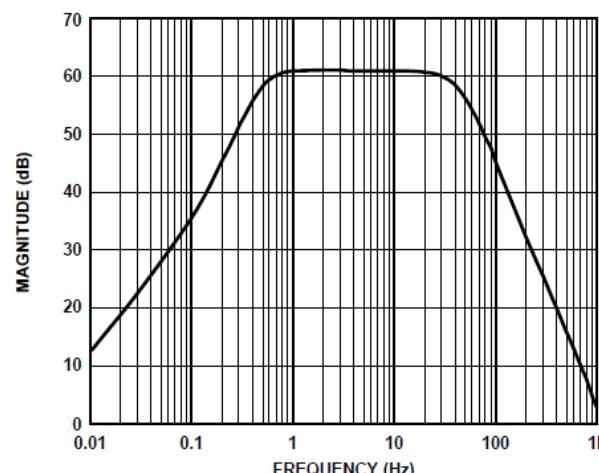


Figure 67. Frequency Response of Cardiac Monitor Circuit

ECG Monitor


Analog Front End (AFE)

OEM example with AD8232

<https://www.sparkfun.com/products/12650>

https://github.com/sparkfun/AD8232_Heart_Rate_Monitor

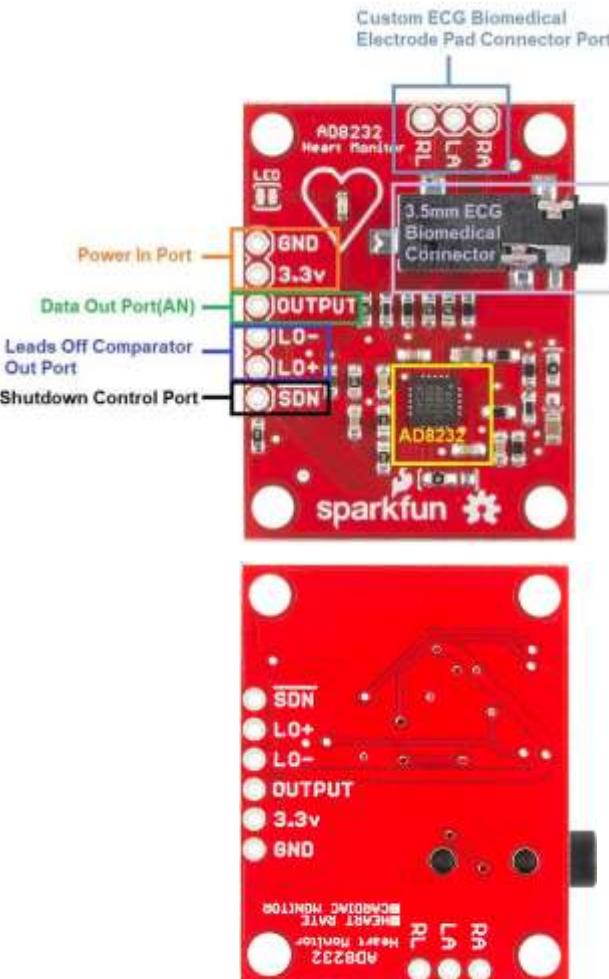SparkFun AD8232 Single Lead Heart Rate Monitor



Pin Description of the AD8232 ECG Module


Pin Name	Description
GND	Power Supply Ground
3.3v	Power Supply 3.3v
Output (ADC)	Operational Amplifier Output. The fully conditioned heart rate signal is present at this output. OUT can be connected to the input of an ADC.
LO-	Leads Off Comparator Output. In dc leads off detection mode, LO- is high when the electrode to -IN is disconnected, and it is low when connected
LO+	Leads Off Comparator Output. In dc leads off detection mode, LO+ is high when the +IN electrode is disconnected, and it is low when connected
SDN	Shutdown Control Input. Drive SDN low to enter the low power shutdown mode.
RA (Right Arm)	RED Biomedical electrode pad RA(input). Instrumentation Amplifier Negative Input. -IN is typically connected to the right arm (RA) electrode
LA (Left Arm)	YELLOW Biomedical electrode pad LA(input). Instrumentation Amplifier Positive Input. +IN is typically connected to the left arm (LA) electrode
RL(Right Leg)	GREEN Biomedical electrode pad RL(input). Right Leg Drive Output. Connect the driven electrode (typically, right leg) to the RLD pin.

ECG Monitor

Analog Front End (AFE)

OEM example with AD8232

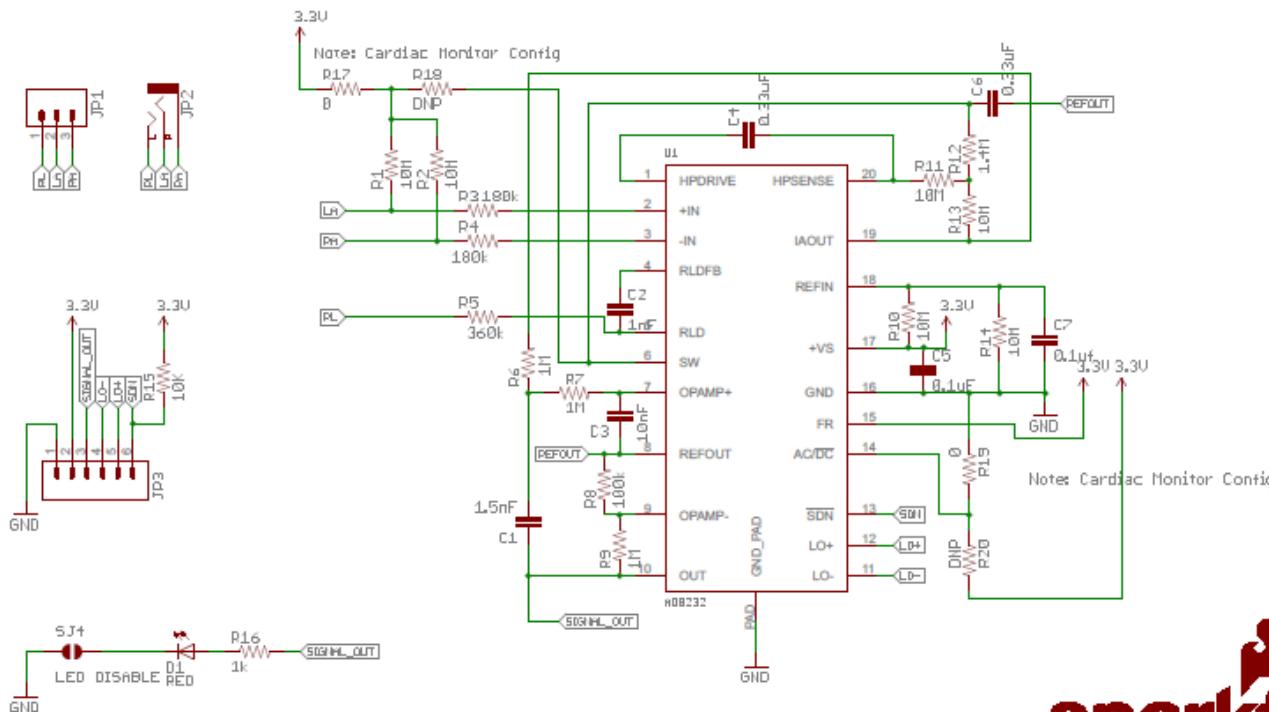SparkFun AD8232 Single Lead Heart Rate Monitor Schematic



Released under the Creative Commons Attribution Share-Alike 3.0 License http://creativecommons.org/licenses/by-sa/3.0		<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>
TITLE: AD8232_Heart_Rate_Monitor_v10		
Design by: Casey Kuhns		REV: v10
Date: 7/15/2014 11:07:00 AM	Sheet: 1/1	

ECG Monitor



Analog Front End (AFE)

OEM example with AD8232

SparkFun AD8232 Single Lead Heart Rate Monitor PCB

EasyEDA (Open hardware_Org)

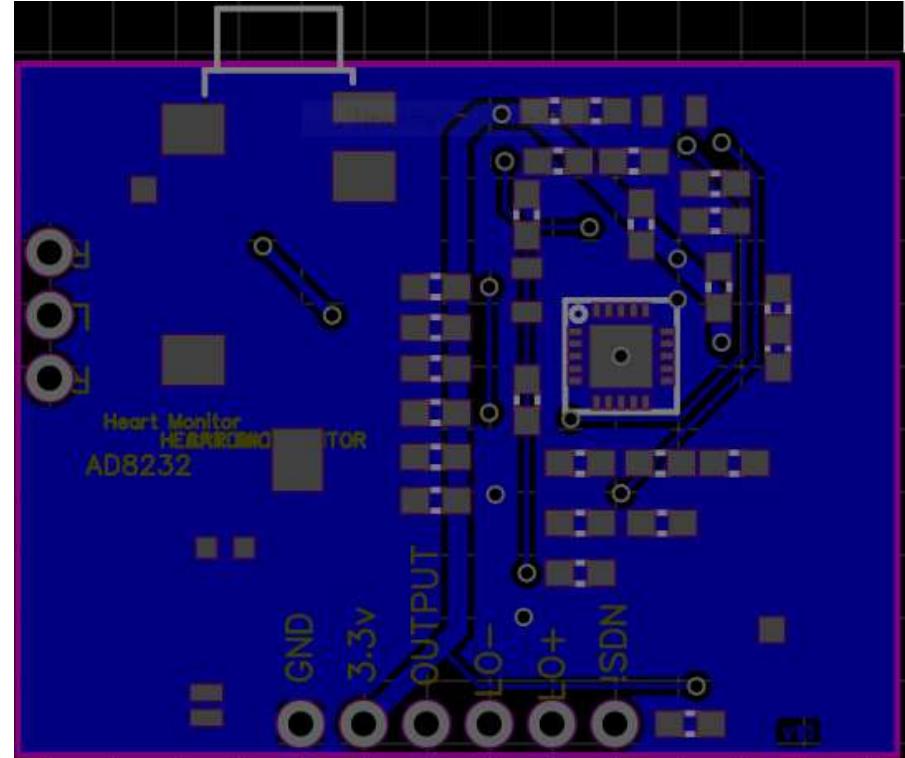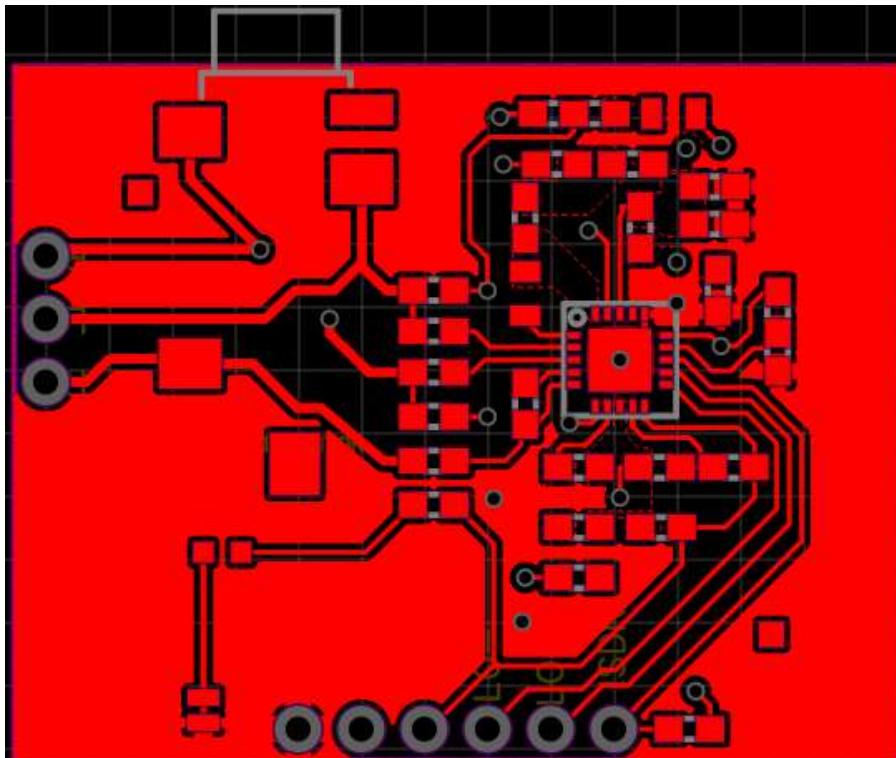https://easyeda.com/Sungchankim/Single_Lead_Heart_Rate_Monitor_AD8232_Open_hardware-2c0cavtPN_copy





ECG Monitor

Analog Front End (AFE)

OEM example with AD8232

SparkFun AD8232 Single Lead Heart Rate Monitor

Different Options

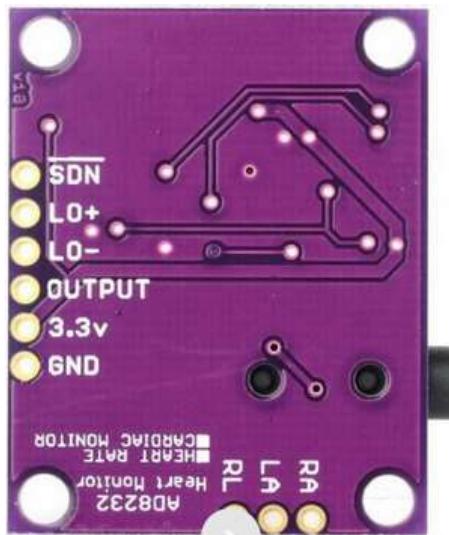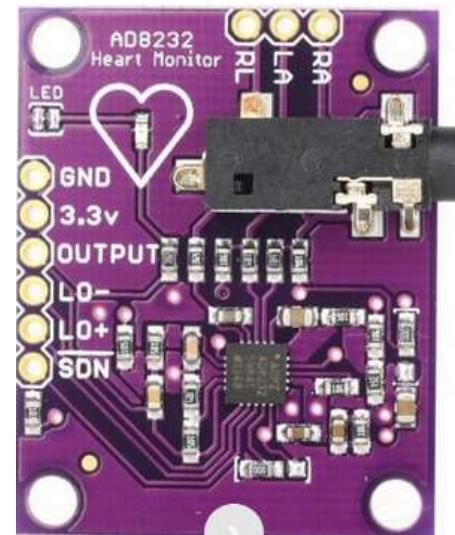



ECG Monitor

Analog Front End (AFE)

OEM example with AD8232

DFROBOT Gravity: Analog Heart Rate Monitor Sensor (ECG) For Arduino SKU:SEN0213

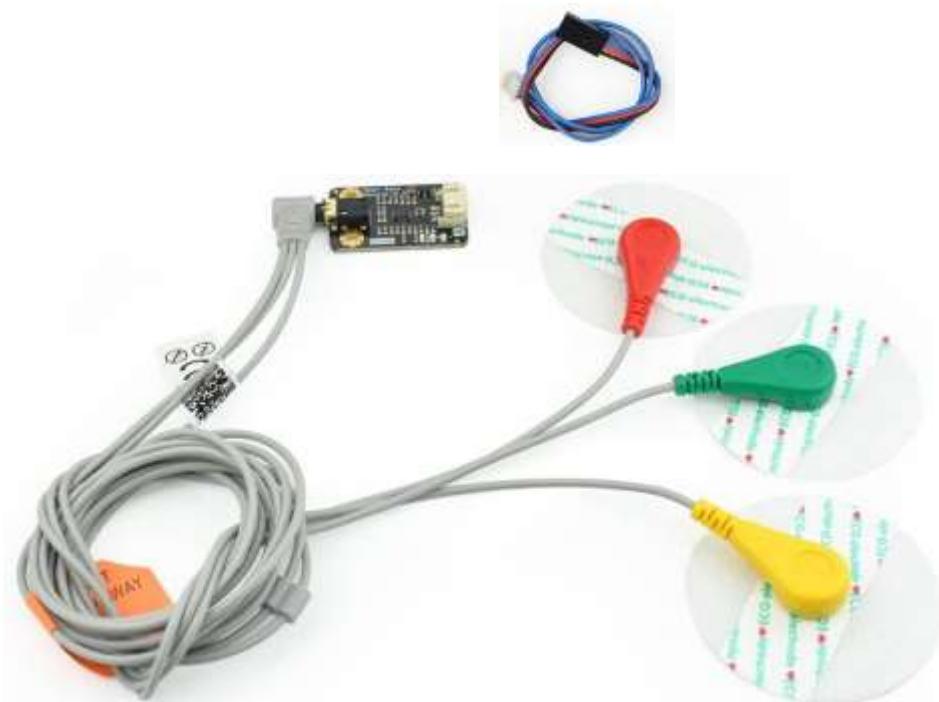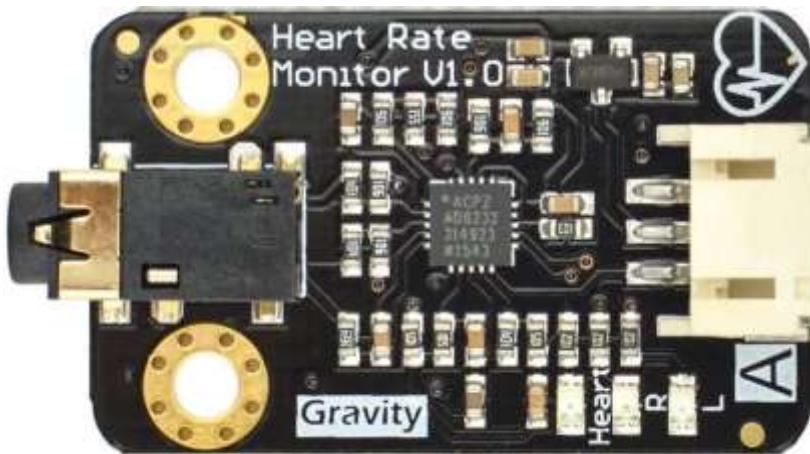https://wiki.dfrobot.com/AnalogHeartRateMonitorSensor_SKU_SKU_SEN0213




ECG Monitor

Analog Front End (AFE) OEM example with AD8232

DFROBOT Gravity: Analog Heart Rate Monitor Sensor (ECG) For Arduino SKU:SEN0213

https://wiki.dfrobot.com/Heart_Rate_Monitor_Sensor_SKU_SEN0213
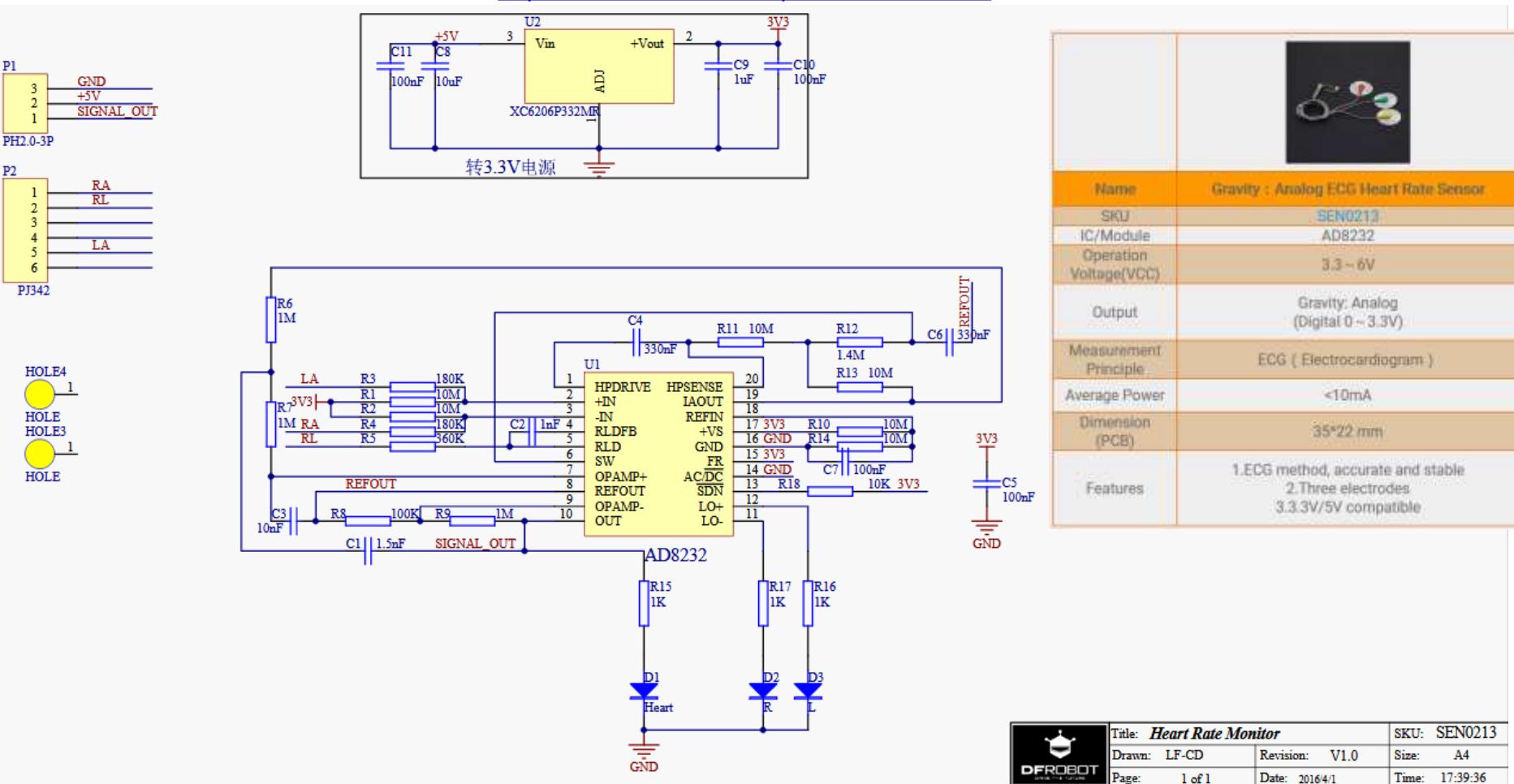
<https://www.dfrobot.com/product-1510.html>




ECG Monitor

Analog Front End (AFE)


OEM example with AD8232: MIKROE ECG 5 Click

<https://www.mikroe.com/ecg-5-click>

ECG 5 click can be used for the development of ECG and Heart-Rate (HR) applications. The Click board™ features the AD8232, an integrated bio-signal front end. This IC has many features necessary for providing accurate ECG measurements, including very high common-mode rejection ratio, high gain with DC blocking capability, adjustable high-pass and low-pass filters, integrated right leg drive (RLD), etc. Electrodes presence detection pin helps to reduce the overall power consumption, as it can be used to set the standby mode of the host MCU. The fully conditioned bio-signal is available at the analog output to be sampled by an external A/D converter.

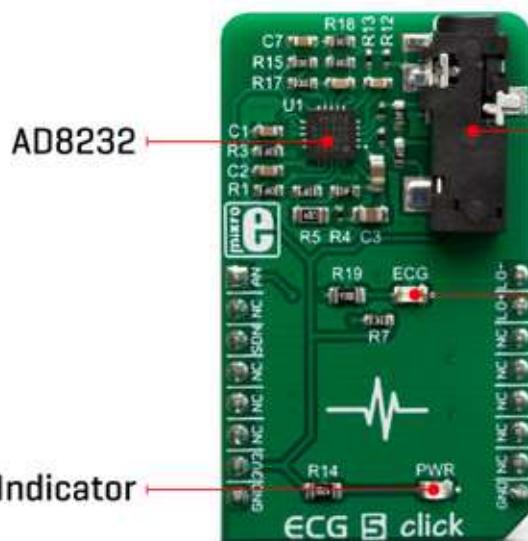

Notes	Pin	mikro™ BUS				Pin	Notes
Analog ECG signal OUT	AN	1	AN	PWM	16	LO-	Lead-off detection for IN-
	NC	2	RST	INT	15	LO+	Lead-off detection for IN+
Chip Enable	SDN	3	CS	RX	14	NC	
	NC	4	SCK	TX	13	NC	
	NC	5	MISO	SCL	12	NC	
	NC	6	MOSI	SDA	11	NC	
Power Supply	3.3V	7	3.3V	5V	10	NC	
Ground	GND	8	GND	GND	9	GND	Ground

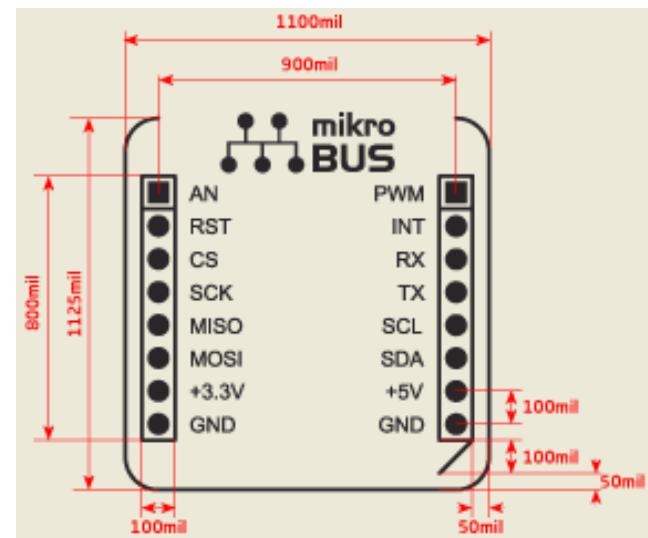


ECG Monitor

Analog Front End (AFE)

OEM example with AD8232

MIKROE ECG 5 Click Schematic

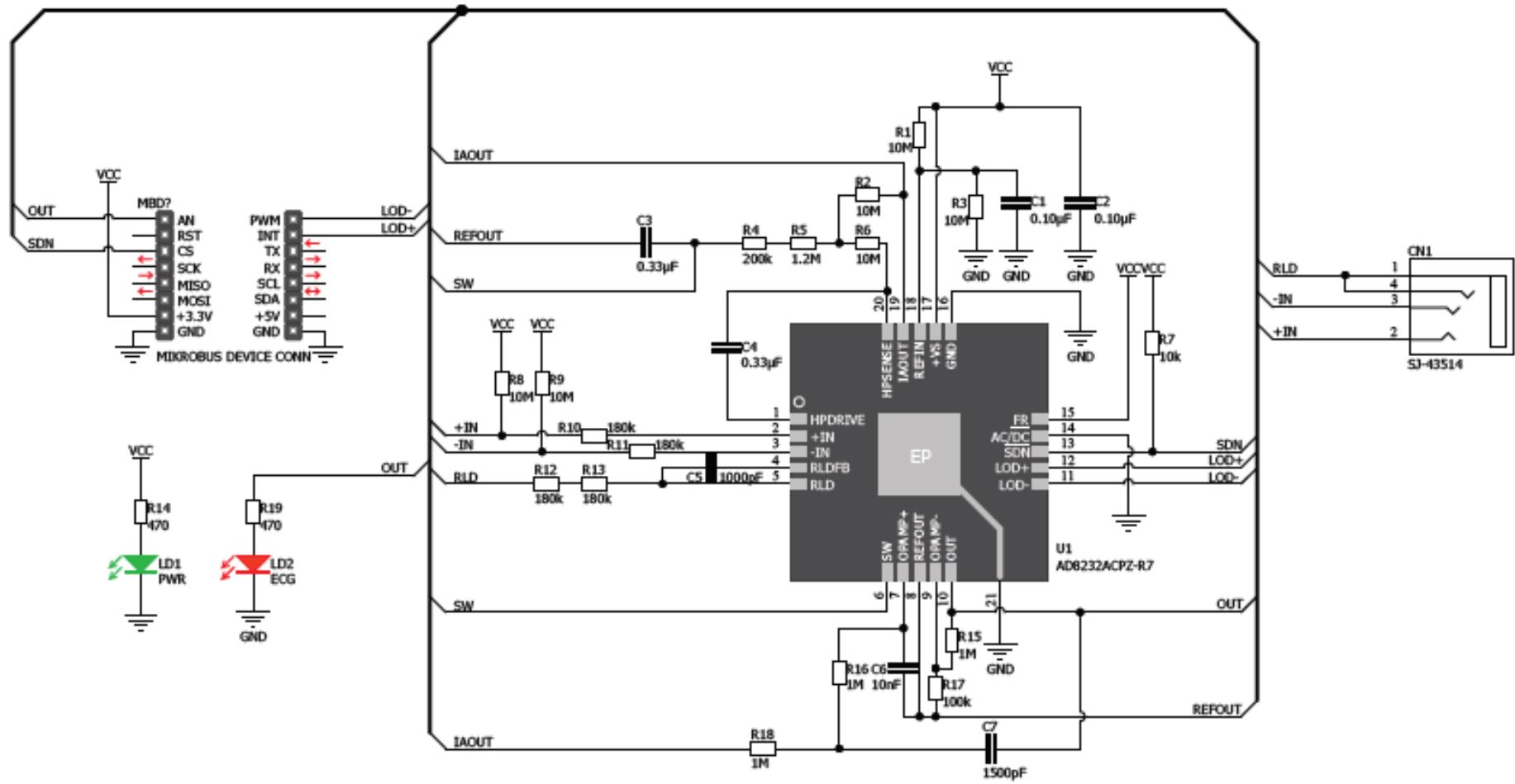

ECG Monitor

Analog Front End (AFE)


OEM example with ADS1194

<https://www.mikroe.com/ecg-2-click>

MIKROE ECG 2 click

ECG 2 click contains [ADS1194](#) 16-bit delta-sigma analog-to-digital converters from Texas Instruments, a built-in programmable gain amplifier (PGA), an internal reference, and an onboard oscillator.

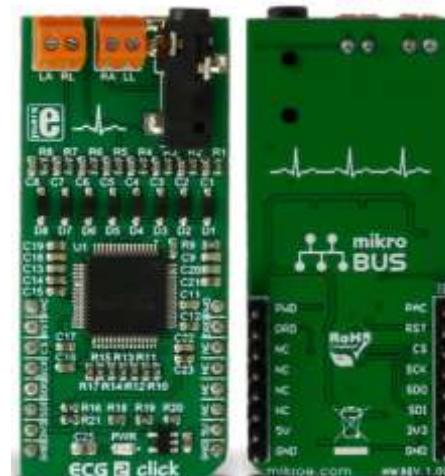The click communicates with the target MCU over SPI and the following mikroBUS pins: PWM, AN and INT. ECG 2 click runs on 3.3V and 5V power supply.




ECG Monitor

Analog Front End (AFE)

OEM example with ADS1294

MIKROE ECG 2 Click Schematic

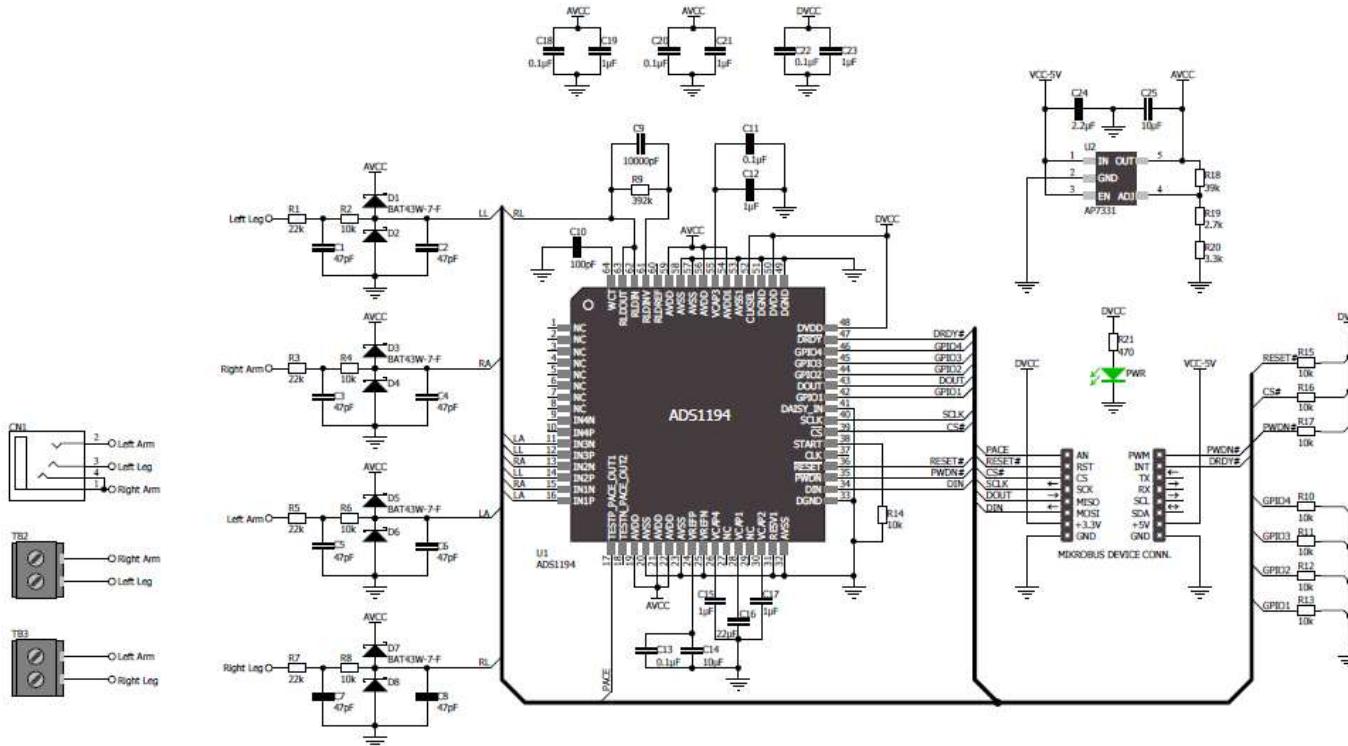

ECG Monitor

SMD Passive Components


Surface-mount technology (SMT) is a method for producing electronic circuits in which the components are mounted or placed directly onto the surface of printed circuit board (PCBs).
An electronic device so made is called a **surface-mount device (SMD)**

Dimensions (Surface Mount)



English	Metric	Length	Width
0402	1005	1.0mm (0.04")	0.5mm (0.02")
0603	1608	1.6mm (0.06")	0.8mm (0.03")
0805	2012	2.0mm (0.08")	1.2mm (0.05")
1206	3216	3.2mm (0.12")	1.6mm (0.06")
1210	3225	3.2mm (0.12")	2.5mm (0.10")
1812	4532	4.5mm (0.18")	3.2mm (0.12")
2225	5764	5.7mm (0.22")	6.4mm (0.25")

No Component Marking

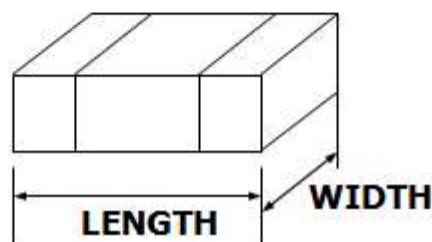

ECG Monitor Protection

Transient Protection

- Other equipment attached to the patient can present a risk to the machine.
- For example, in the operating suite, patients undergoing surgery usually have their ECGs continuously monitored during the procedure.
- If the surgical procedure involves the use of an electrosurgical unit, it can introduce onto the patient relatively high voltages that can enter the electrocardiograph or cardiac monitor through the patient's electrodes.
- If the ground connection to the electrosurgical unit is faulty or if higher-than-normal resistance is present, the patient's voltage with respect to ground can become quite high during coagulation or cutting.
- These high potentials enter the electrocardiograph or cardiac monitor and can be large enough to damage the electronic circuitry.

• Figure shows the basic arrangement of such protective circuits. Two-terminal voltage-limiting devices are connected between each patient electrode and electric ground. • After a certain voltage level these devices become short circuit and prevents high current flowing through ECG.

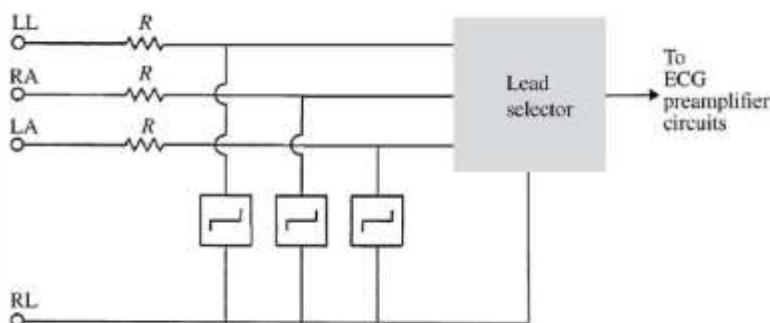


Figure 6.13 A voltage-protection scheme at the input of an electrocardiograph to protect the machine from high-voltage transients. Circuit elements connected across limb leads on left-hand side are voltage-limiting devices.


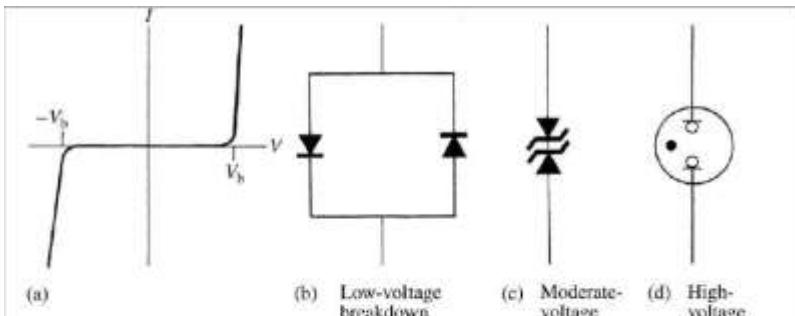


Figure 6.14 Voltage-limiting devices (a) Current–voltage characteristics of a voltage-limiting device, (b) Parallel silicon-diode voltage-limiting circuit, (c) Back-to-back silicon Zener-diode voltage-limiting circuit, (d) Gas-discharge tube (neon light) voltage-limiting circuit element.

- At voltages less than V_b , the breakdown voltage, the device allows very little current to flow and ideally appears as an open circuit.
- Once the voltage across the device attempts to exceed V_b , the characteristics of the device sharply change, and current passes through the device to such an extent that the voltage cannot exceed V_b .
- Under these conditions, the device appears to behave as a short circuit in series with a constant-voltage source of magnitude V_b .

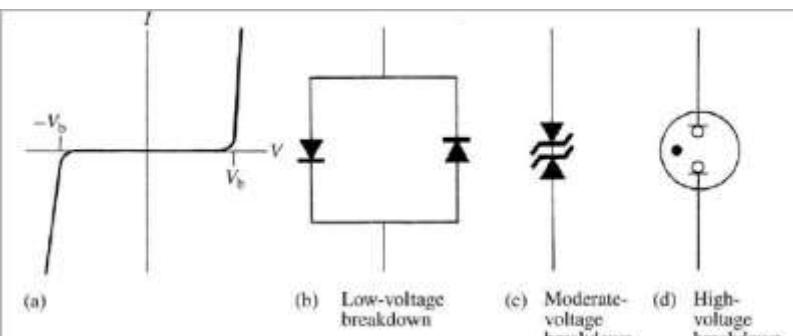

• Parallel silicon diodes, as shown in Figure 6.14(b), give a characteristic with a breakdown voltage of approximately 600 mV. The ECG itself does not approach such a voltage; it is possible under extreme conditions for dc-offset potentials.

• Zener diodes, connected back to back. When a voltage is connected across this circuit, one of the diodes is biased in the forward direction and the other in the reverse direction. The breakdown voltage in the forward direction is approximately 600 mV, but that in the reverse direction is in the range of 2 to 20 V.

• Gas-discharge tube appears as an open circuit until it reaches its breakdown voltage. It then switches to the conducting state and maintains a voltage that is usually several volts less than the breakdown voltage. Breakdown voltages ranging from 50 to 90 V are typical for this device.

ECG Monitor Protection

<https://www.microsemi.com/existing-parts/parts/137888>

Features

- Protects Electrocardiographic (ECG) Monitoring Equipment (ME) Against Effects of Defibrillation
- Very Small Size and Very Low Leakage
- Integrates Zener Diodes and SCRs into a Single IC
- Easily Expandable to M×5 Channels
- Facilitates Compliance with IEC 60601-2-25 and IEC 60601-2-27
- Extremely Fast Turn-On
- Five Terminals Plus Substrates
- 28-Pin QFN Package
- Medical-Level Traceability

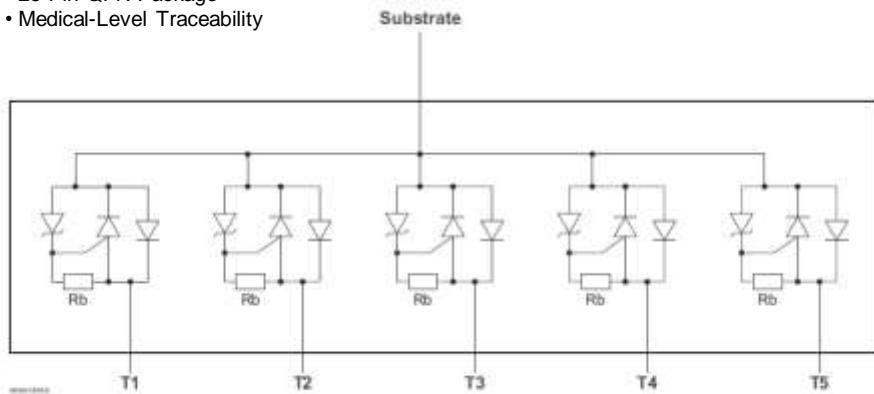


Figure 1 • ZL70590 Schematic Diagram

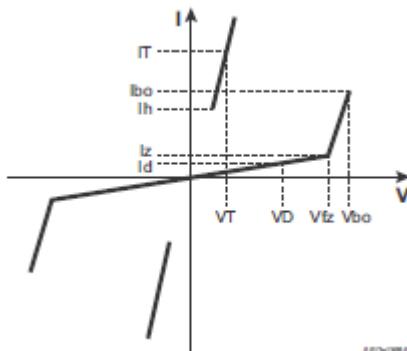


Figure 2-2 • Terminal-to-Terminal Characteristic

ZL70590 EKG/ECG Surge Protection Device


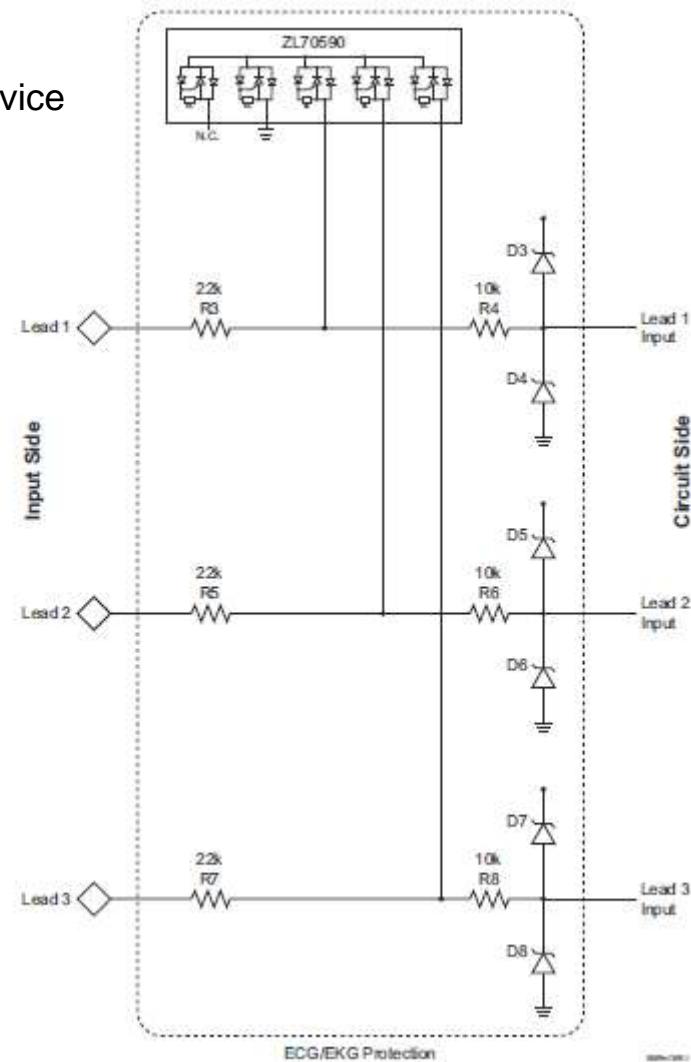
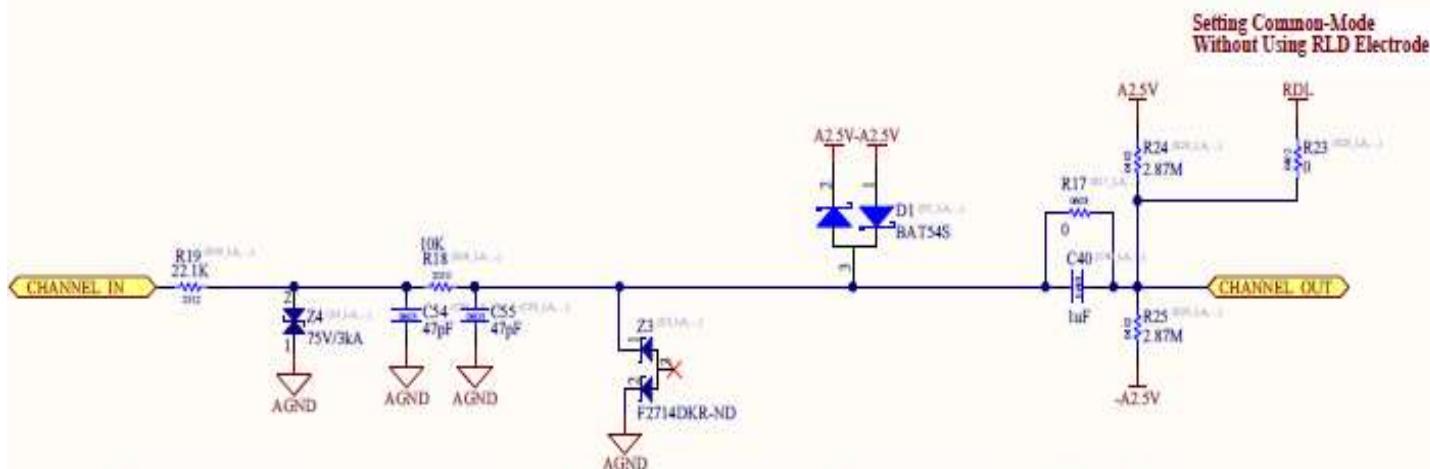
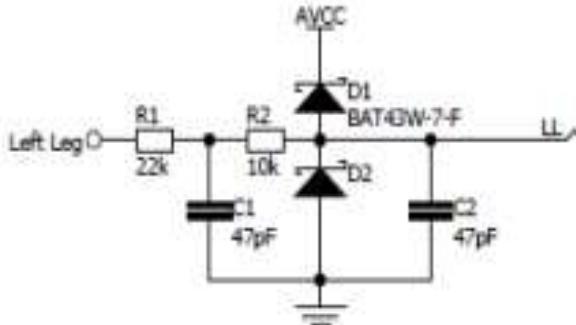


Figure 4-1 • Example Protection Scheme (Three-Lead EKG Example Shown)

ECG Monitor Protection

Input Protection Examples

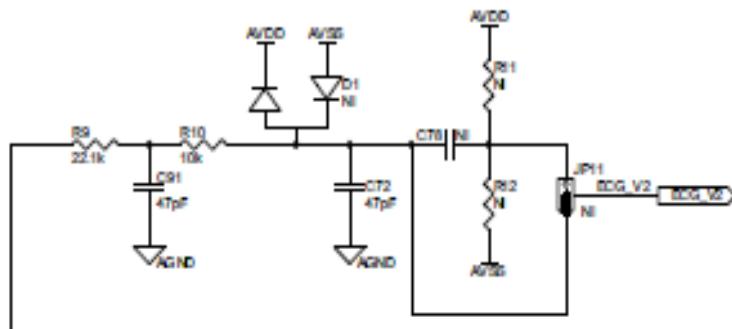

Transient protection
(very high current surges)

2nd order
low-pass filter

Transient protection
(very high voltage and low
current surge)

Transient protection
(low voltage)

High-pass filter

Gas discharge tubes (GDTs), or spark gap devices, are a notable exception: they combine the attributes of moderate clamping voltages, very high impedance in their uncharged state, and fast operation.

(including cable resistor 22k)

Center frequency

$f_c = 161251.208806[\text{Hz}]$

Q factor

$Q = 0.213849287169$

Damping ratio ζ

$\zeta = 2.3380952381$

Low capacitance of IpF @
VR=0V (MAX)

Forward voltage:

240mV @ IF = 0.1 mA


400mV @ IF = 10 mA

800mV @ IF = 100 mA


Cut-off frequency
 $f_c = 0.0504133490947[\text{Hz}]$

ECG Monitor Protection

Consider Input Protection

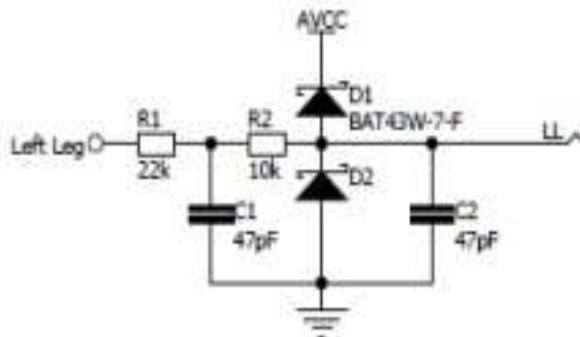

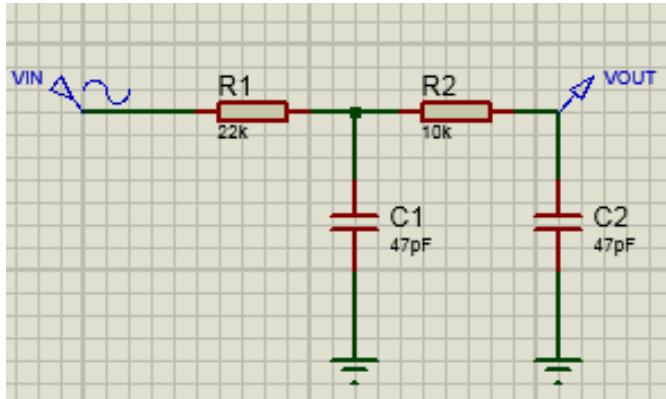Respuesta en frecuencia del circuito de protección (pasa bajo)




Bode de amplitud del circuito de protección. $f_{3dB} = 67.8$ KHz

ECG Monitor Protection


Driven-right-leg system

- The common-mode voltage on the body is sensed by the two averaging resistors R_a , inverted, amplified, and fed back to the right leg.
- This negative feedback drives the common-mode voltage to a low value.
- The body's displacement current flows not to ground but rather to the op-amp output circuit.
- This reduces the interference as far as the ECG amplifier is concerned and effectively grounds the patient

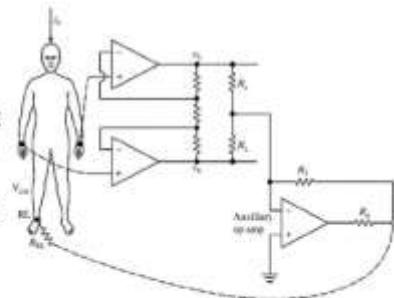

Driven-right-leg system

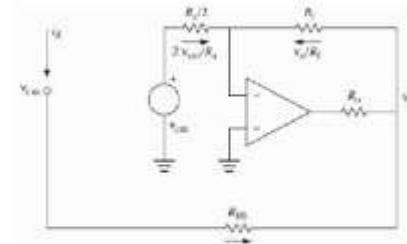- When the amplifier saturates, as would occur during a large transient V_{cm} , its output appears as the saturation voltage V_s . The right leg is now connected to ground through this source and the parallel resistances R_f and R_o .
- To limit the current, R_f and R_o should be large. Values as high as $5 M\Omega$ are used.




$$\frac{2v_{cm}}{R_a} + \frac{v_o}{R_f} = 0 \quad v_o = -\frac{2R_f}{R_a} v_{cm}$$

$$v_{cm} = R_{RL} i_d + v_o \quad v_{cm} = \frac{R_{RL} i_d}{1 + 2R_f/R_a}$$

Driven-right-leg system

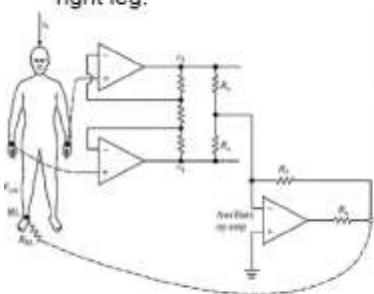- The common-mode voltage on the body is sensed by the two averaging resistors R_a , inverted, amplified, and fed back to the right leg.




$$\frac{2v_{cm}}{R_a} + \frac{v_o}{R_f} = 0 \quad v_o = -\frac{2R_f}{R_a} v_{cm}$$

$$v_{cm} = R_{RL} i_d + v_o \quad v_{cm} = \frac{R_{RL} i_d}{1 + 2R_f/R_a}$$

Driven-right-leg system

- When the amplifier is not saturated, we would like V_{cm} to be as small as possible or, in other words, to be an effective low-resistance path to ground.
- This can be achieved by making R_f large and R_a relatively small. R_f can be equal to R_o , but R_a can be much smaller.
- A typical value of R_a would be $25 k\Omega$.
- A worst-case electrode resistance R_{RL} would be $100 k\Omega$. The effective resistance between the right leg and ground would then be
- For the $0.2 mA$ displacement current, the common-mode voltage is

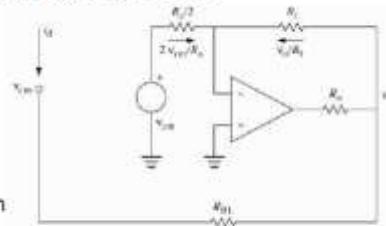

$$\frac{2v_{cm}}{R_a} + \frac{v_o}{R_f} = 0 \quad v_o = -\frac{2R_f}{R_a} v_{cm}$$

$$v_{cm} = R_{RL} i_d + v_o \quad v_{cm} = \frac{R_{RL} i_d}{1 + 2R_f/R_a}$$

$$\frac{100 k\Omega}{1 + \frac{2 \times 5 M\Omega}{25 k\Omega}} = 249 \Omega$$

$$v_{cm} = 249 \Omega \times 0.2 \mu A = 50 \mu V$$

ECG Monitor

Discrete ECG Amplifier with INA

Right Leg


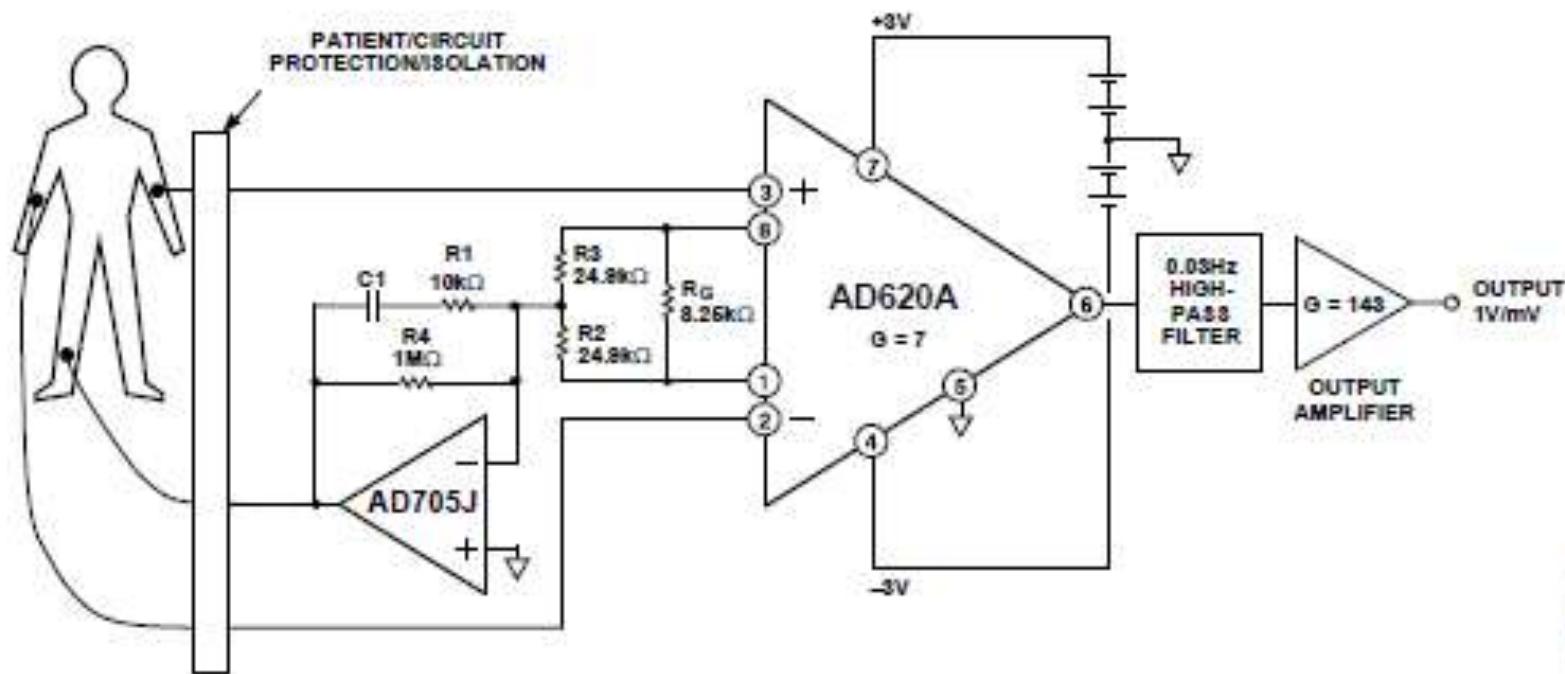


Figure 39. A Medical ECG Monitor Circuit

ECG Monitor

Discrete ECG Amplifier with INA

Right Leg and Protection

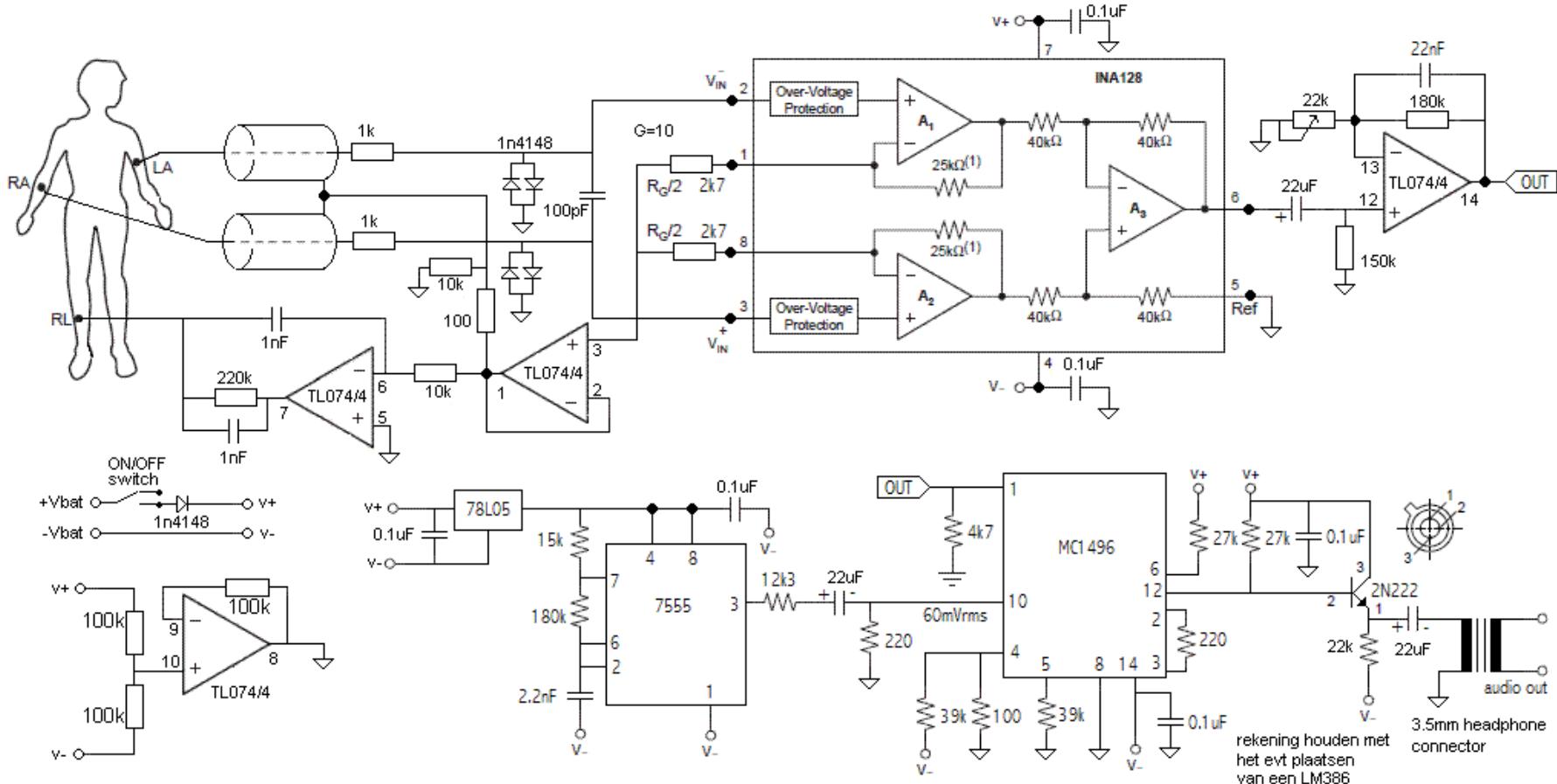

rekening houden met
het evt plaatsen
van een LM386

ECG Monitor EMI Suppression

Inductors, ferrite beads

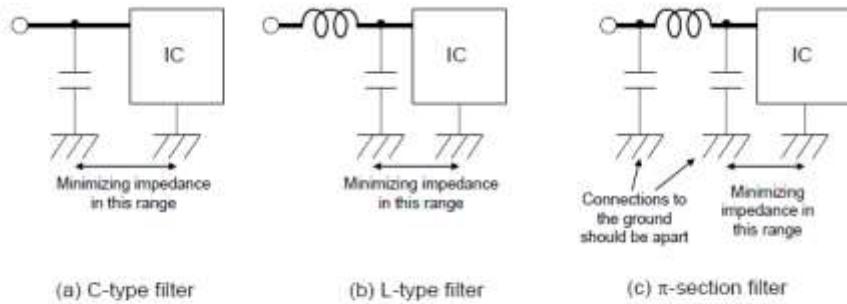


Figure 2-9 Filter configurations used for IC power supplies
(C-type, L-type and π -section)

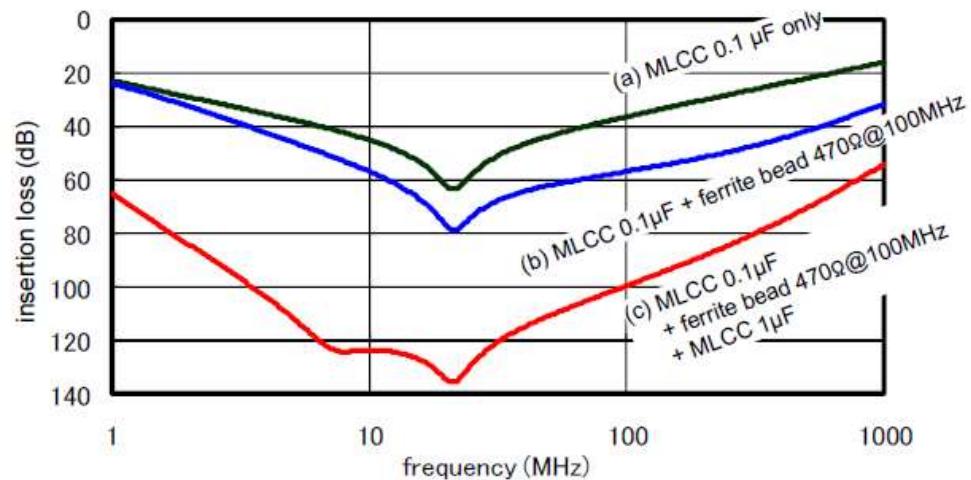


Figure 2-10 An example of insertion loss fluctuation when
an inductor is combined (calculated values)

ECG Monitor

EMI Suppression

Parallel connection of capacitors and antiresonance

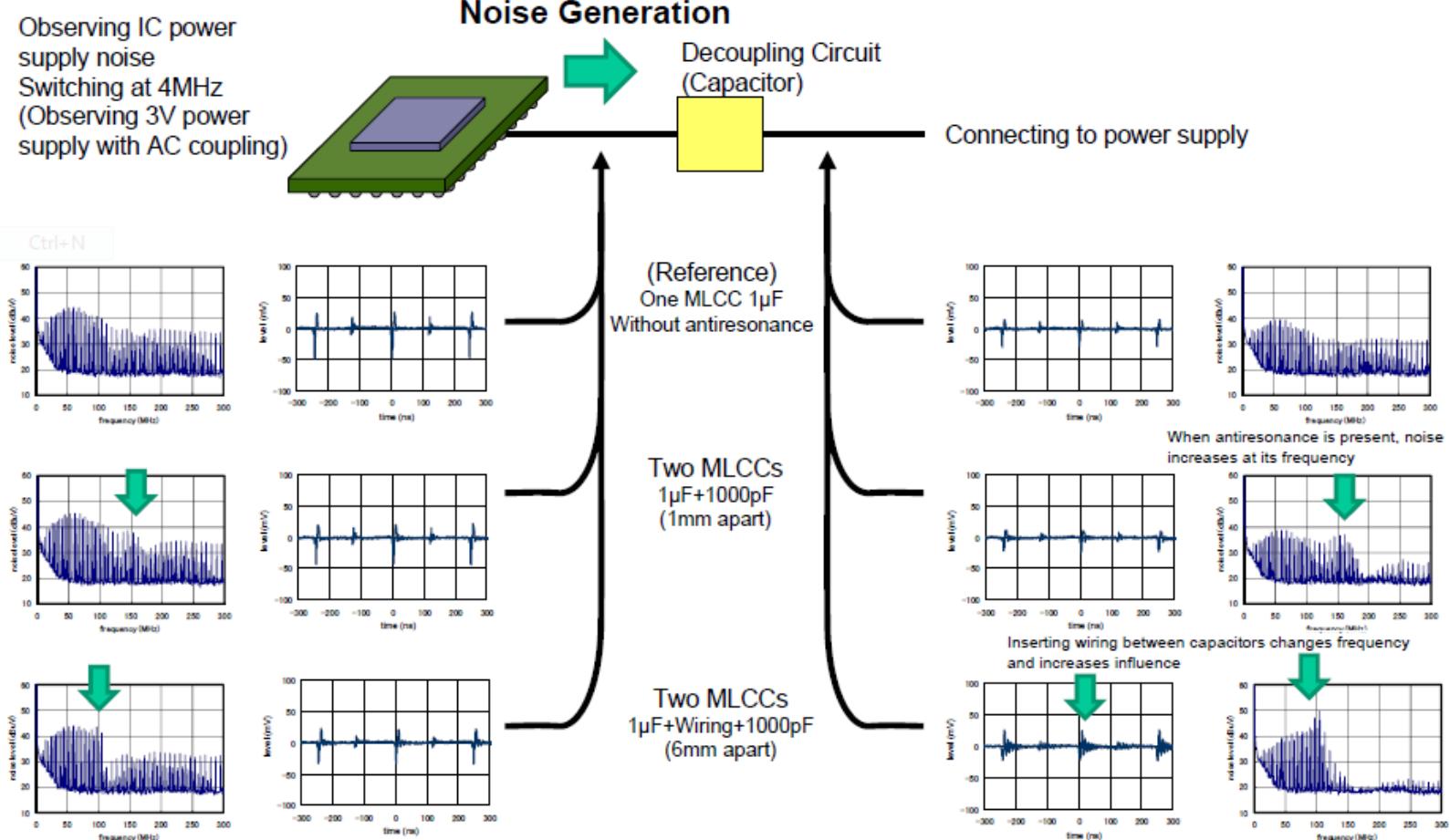


Figure 3-15 Examples of noise observation when antiresonance is present

ECG Monitor EMI Suppression

3-terminal capacitor

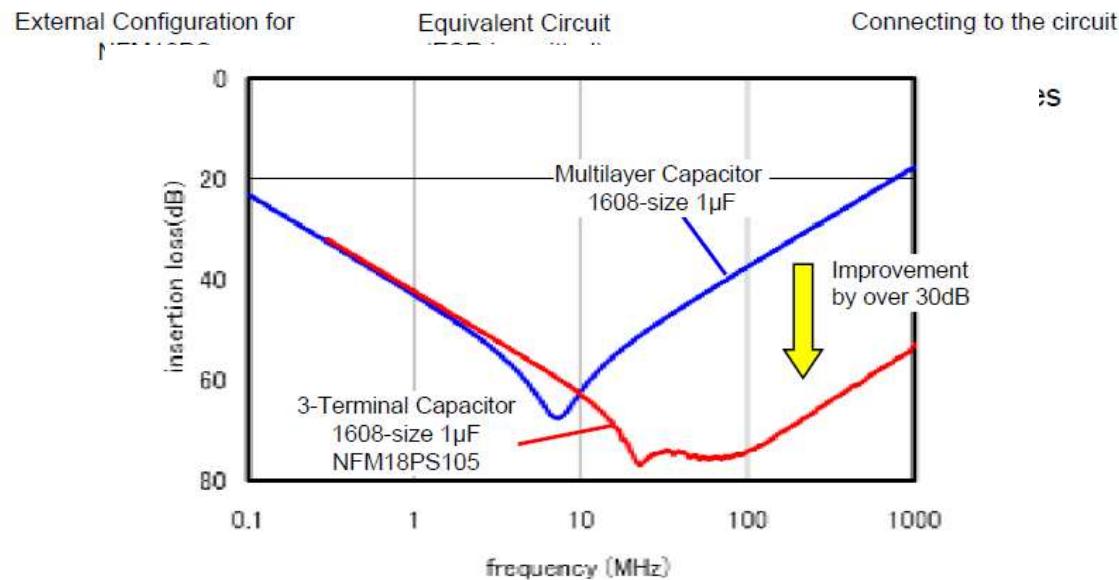
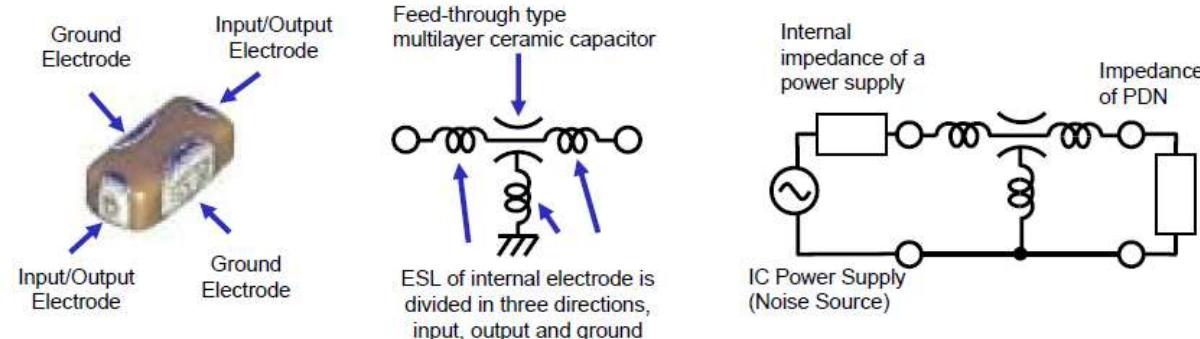


Figure 4-9 Insertion loss characteristics of a 3-terminal capacitor

ECG Monitor EMI Supression

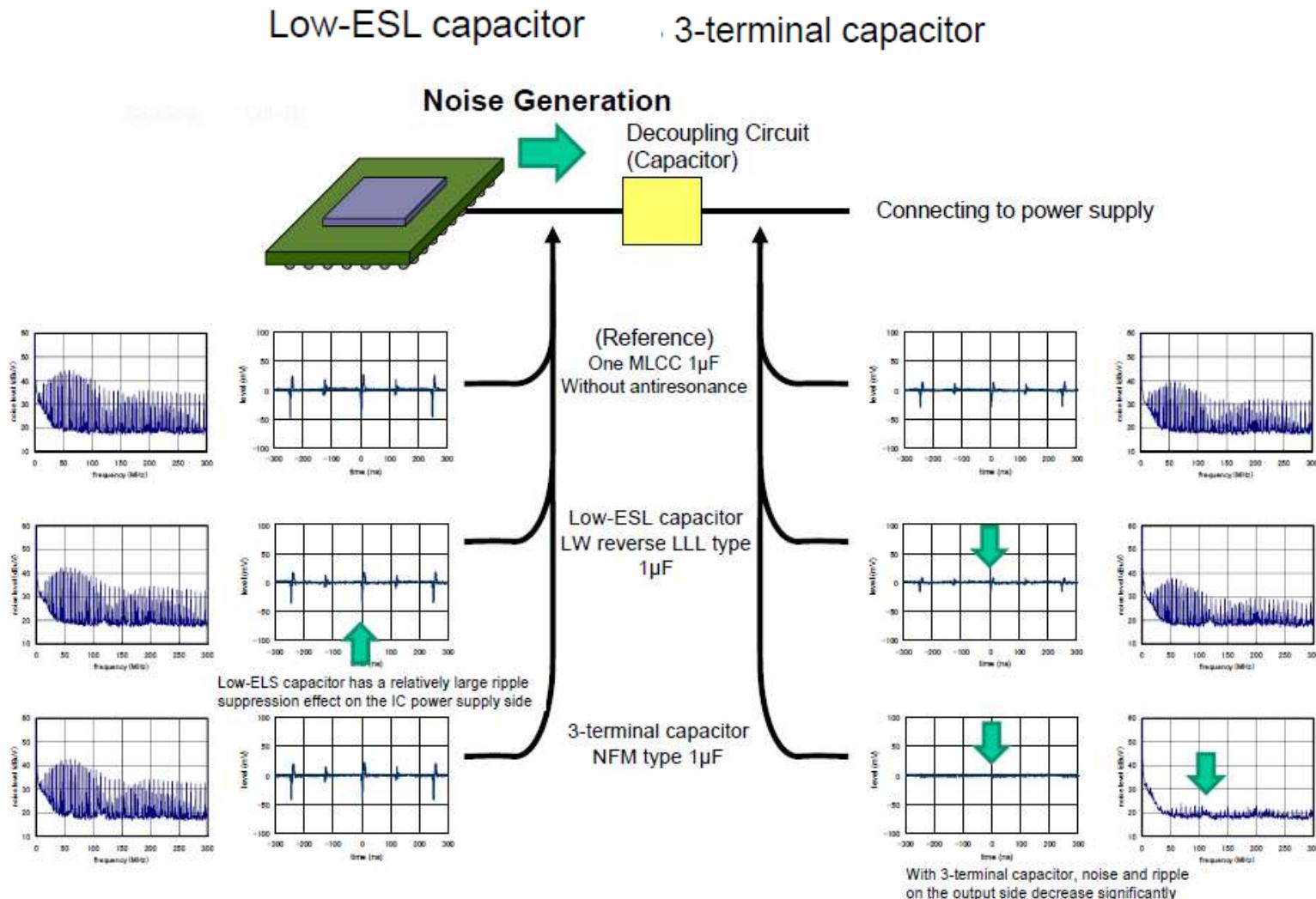


Figure 3-17 Measurement results when using low-ESL capacitors

ECG Monitor EMI Suppression

Characteristics for a combination of capacitors and inductors

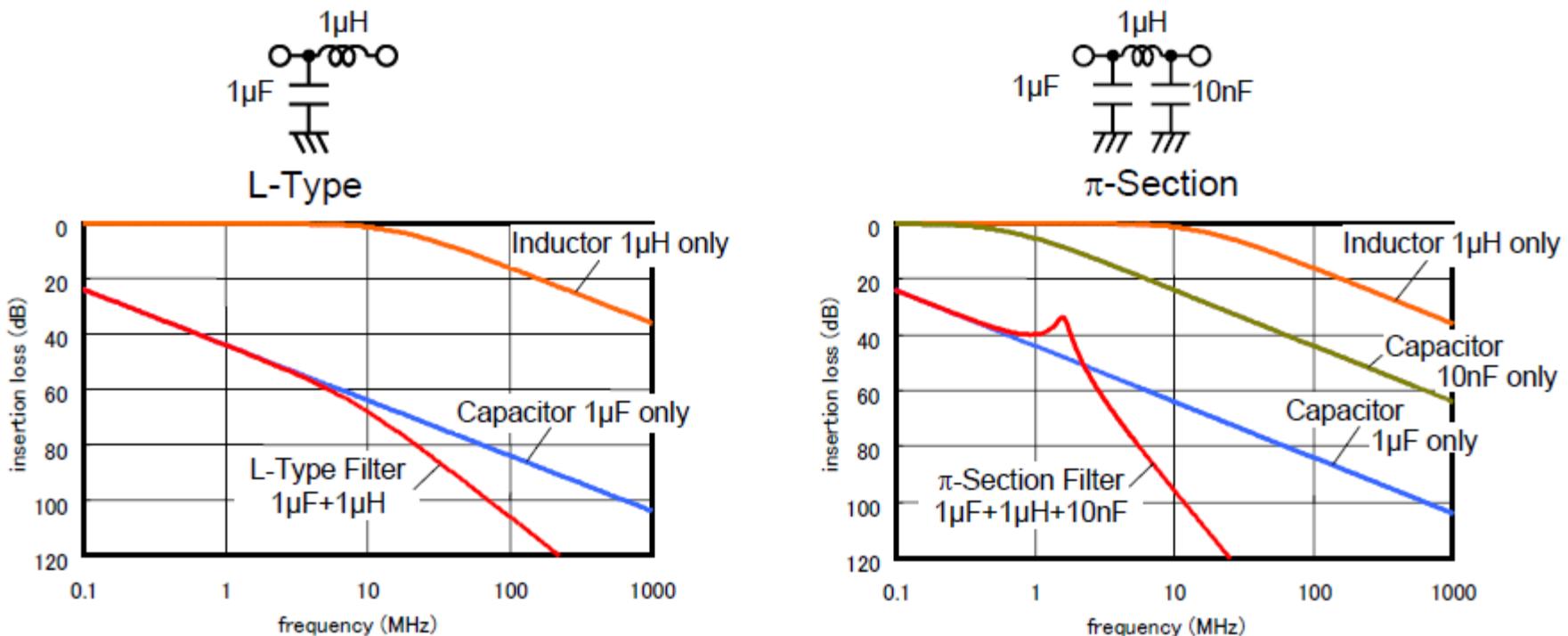


Figure 5-12 Examples of insertion loss characteristics of L-type and
π-section filters (calculated values)

ECG Monitor EMI Suppression

Characteristics for a combination of capacitors and inductors

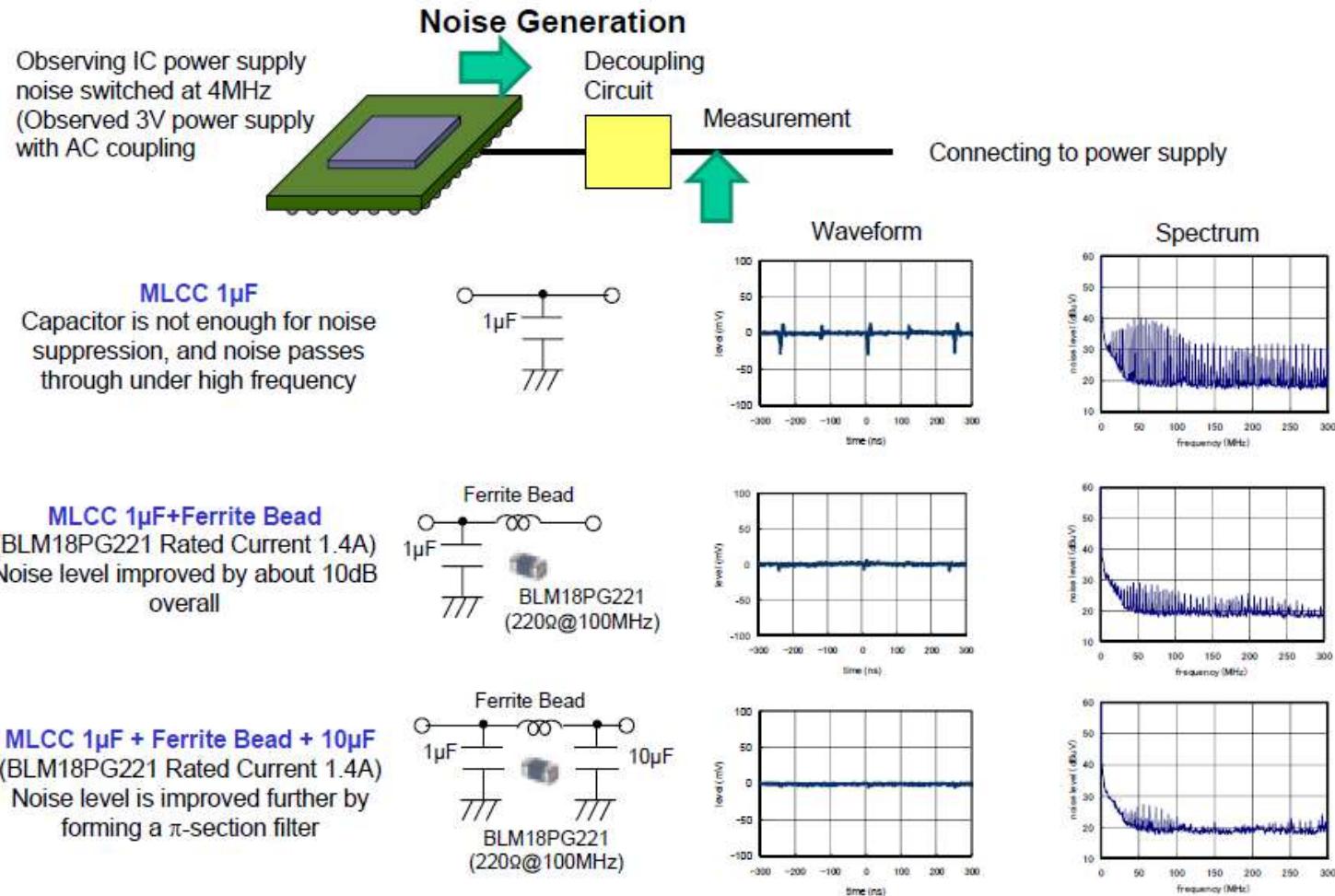


Figure 5-14 An example of noise suppression and improvement by ferrite beads

ECG Monitor EMI Suppression


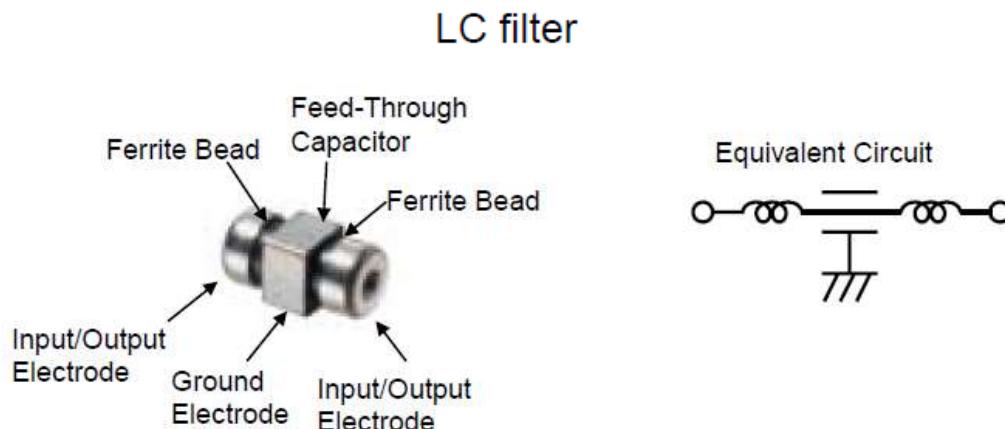


Figure 5-15 LC filter NFE31 for power supplies

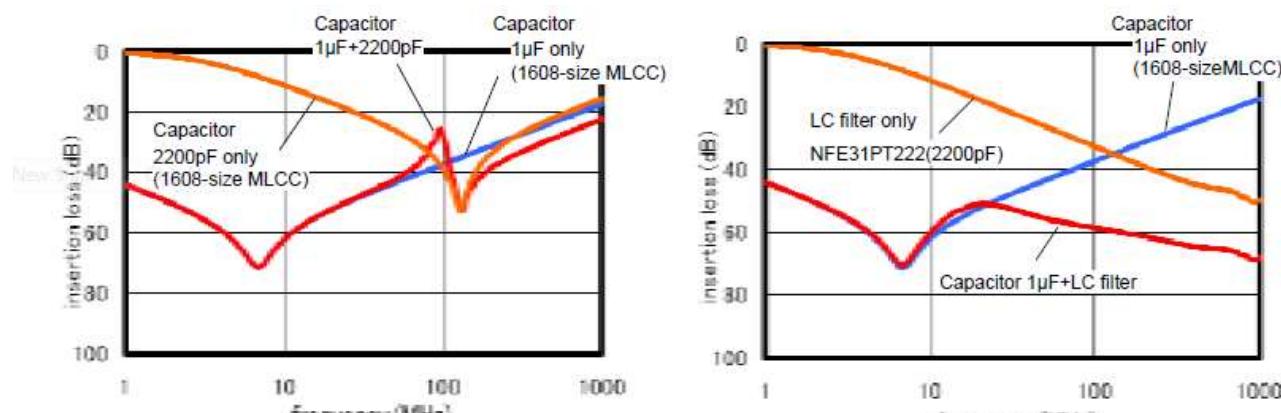

(a) When combining two capacitors

(b) When combining a capacitor and a LC filter

Figure 5-16 Frequency characteristics of a power supply filter (calculated values)

ECG Monitor

EMI Suppression

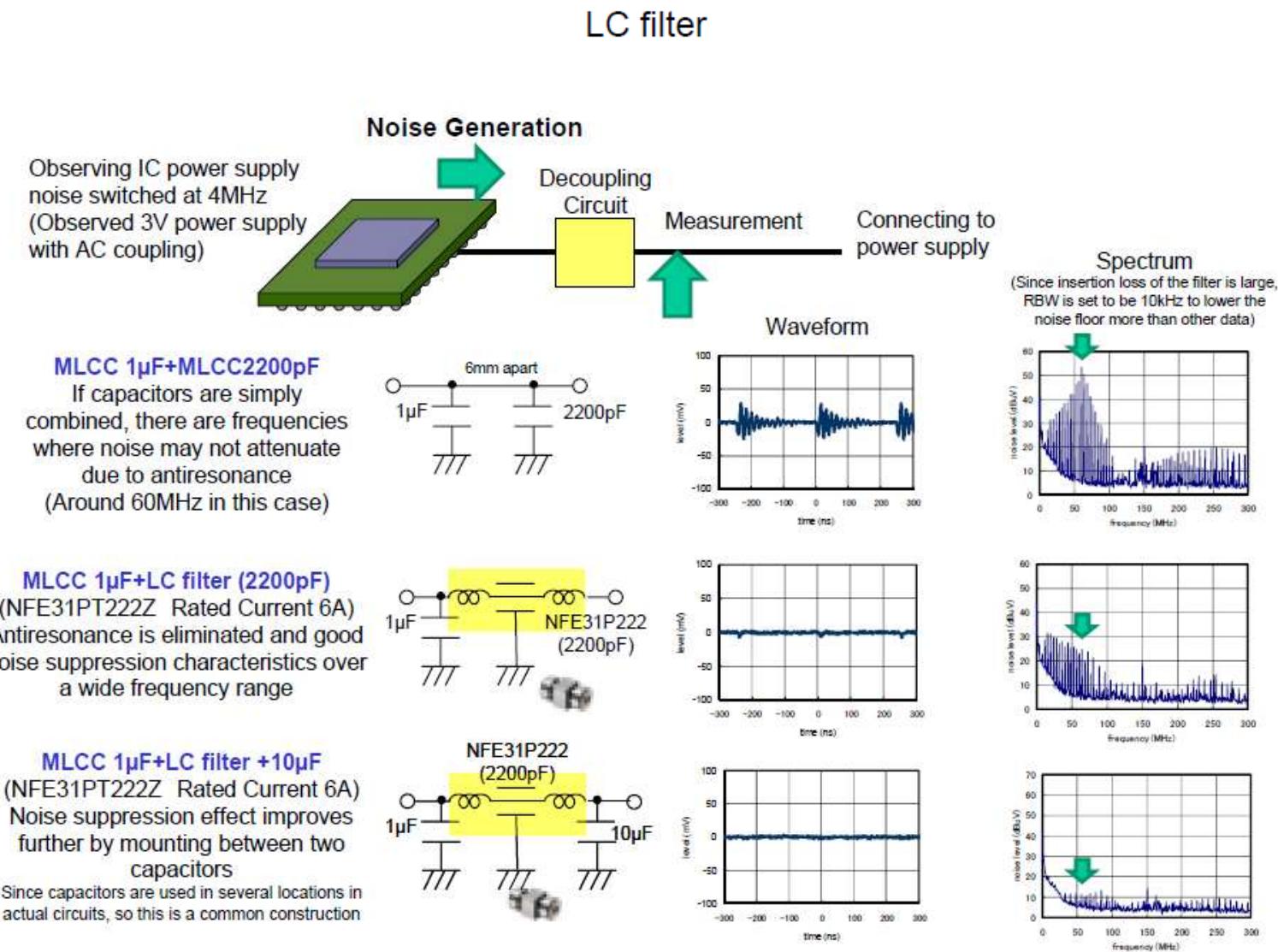


Figure 5-17 An example of improving noise suppression using an LC filter

ECG Monitor EMI Suppression

EMI suppression

<http://www.ti.com/lit/an/szza009/szza009.pdf>

<https://www.murata.com/products/emc/emifil/knowhow/basic>

<https://resources.altium.com/presentations/pcb-design-techniques-to-reduce-emi>

<https://resources.altium.com/ebooks/pcb-design-techniques-to-reduce-emi-ebook>

<https://resources.orcad.com/blog/techniques-to-reduce-emi-in-your-pcb-designs>

https://www.eetimes.com/author.asp?section_id=36&doc_id=1327269#


Considerar las opciones Murata (Murata_EMILFIL_c31e-794748.pdf):

Ferrite Bead: BLM18PG121SN1

Capacitor Type: NFM18PS105D0J3

Common Mode Choque Coil: No

Type	Features	Suitable Circuits
Ferrite Bead BLM/BLA Series	<ul style="list-style-type: none">· Miniaturized· GND connection unnecessary· Effective at low impedance line	<ul style="list-style-type: none">· Application set with less noise radiation· Low impedance line
Capacitor Type NFM/NFA/NFE/NFR/ NFL/NFW Series	<ul style="list-style-type: none">· Great noise suppression effect· With effect as By-Pass capacitor (Lineup for Power)· Good noise separation from signal (LC filter for Signal)· Effective at high impedance line	<ul style="list-style-type: none">· Application set with higher noise radiation· High impedance line· Circuit with By-Pass capacitor· Circuit driven by high frequency
Common Mode Choke Coil	<ul style="list-style-type: none">· Possible to suppress noise with less affect of ultra high speed signal· Great effect for common mode noise· Less magnetic saturation by current	<ul style="list-style-type: none">· High speed differential signal line· I/F cable driver· Power line

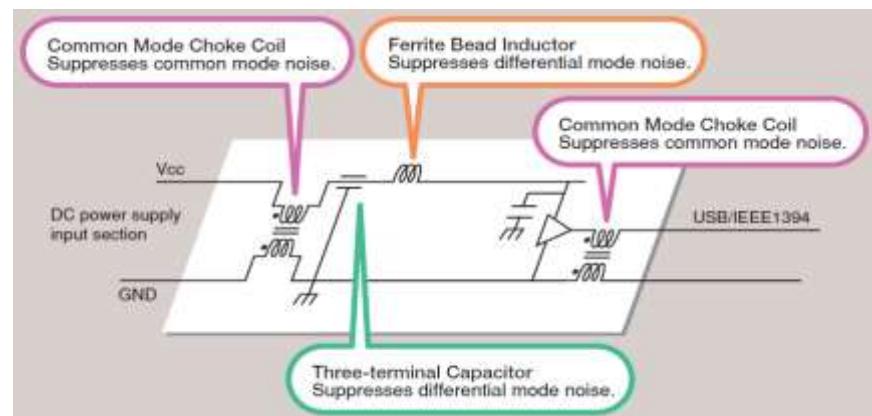

ECG Monitor EMI Supression

BL Series Introduction

● Example of Chip Ferrite Bead BLM Series Structure

● Line Up Classification of Chip Ferrite Bead

Series	Band Type	Frequency Range	Notes
BLM_G Series	High-GHz Band	High	• GA (for high speed signal lines) • GG (for general signal lines)
BLM_H Series	GHz Band	Medium	• HB(HD-HF) (for high speed signal lines) • HG(HK) (for general signal lines)
BLM_E Series	GHz Band	Medium	• EG (for general signal lines) • EB (for general signal lines / for power lines)
BLM standard line up	Low Noise Frequency Band	Low	• AK (for digital interface) • AG (for general signal lines) • AC (for high speed signal lines) • AX (for general signal lines / power lines)

● Rated Current (A): Small (Less than 1A) → Large (1A and more)

● Impedance-Frequency Characteristics (Graph showing Impedance (Ω) vs Frequency (MHz) for various part numbers: BLM18PG306SN1, BLM18PG305SN1, BLM18PG306SN1, BLM18PG121SN1, BLM18PG111SN1, BLM18PG221SN1, BLM18PG311SN1, BLM18PG471SN1. The graph shows multiple curves peaking around 1000-1500 MHz.)

● Notice (Rating): In operating temperature exceeding +85°C, derating of current is necessary for BLM18PG series. Please apply the derating curve shown in chart according to the operating temperature.

● Derating of Rated Current (Graph showing Rated Current (mA) vs Operating Temperature (°C) for BLM18PG471SN1. The graph shows a linear decrease in rated current as temperature increases from -55°C to +125°C.)

BLM Series Power Lines Type Chip Ferrite Bead BLM18P

BLM18P Series 0603/1608 (inch/mm)

Hi Power Pass OK Return OK

0603 size for power lines.
*Please refer to the products designed for both power lines and signal lines.

● Dimensions

● Equivalent Circuit

(Resistance element becomes dominant at high frequencies.)

● Packaging

Code	Packaging	Minimum Quantity
D	180mm Reel Paper Tape	4000
J	320mm Reel Paper Tape	10000
B	bulk(Bag)	1000

● Rated Value (□: packaging code)

Part Number	Impedance (at 100MHz/20°C)	Rated Current	DC Resistance	Operating Temperature Range
BLM18PG306SN1□	30Ω (Typ.)	1000mA	0.05Ω max.	-55°C to +125°C
BLM18PG305SN1□	30Ω ±25%	3000mA	0.025Ω max.	-55°C to +125°C
BLM18PG306SN1□	60Ω (Typ.)	500mA	0.10Ω max.	-55°C to +125°C
BLM18PG121SN1□	120Ω ±25%	2000mA	0.05Ω max.	-55°C to +125°C
BLM18PG111SN1□	180Ω ±25%	1500mA	0.03Ω max.	-55°C to +125°C
BLM18PG221SN1□	220Ω ±25%	1400mA	0.18Ω max.	-55°C to +125°C
BLM18PG311SN1□	330Ω ±25%	1200mA	0.15Ω max.	-55°C to +125°C
BLM18PG471SN1□	470Ω ±25%	1000mA	0.20Ω max.	-55°C to +125°C

Refer to pages from p.101 to p.103 for mounting information.

● Impedance-Frequency Characteristics

● Notice (Rating): In operating temperature exceeding +85°C, derating of current is necessary for BLM18PG series. Please apply the derating curve shown in chart according to the operating temperature.

● Derating of Rated Current

Continued on the following page. □

ECG Monitor EMI Suppression

NF □ Series Introduction

Example of 3-Terminal Capacitor Structure

Chip 3-terminal capacitor is a chip-shaped 3-terminal capacitor designed for noise suppression. Its inner structure, like a feed-through capacitor, makes its ground impedance quite low. Owing to this structure, the 3-terminal capacitor has a good noise suppression effect at a high frequency range up to several hundred MHz.

Series	Equivalent Circuit	Part Number
NFM Series (3-terminal capacitor)		<ul style="list-style-type: none"> ■ NFM18CC ■ NFM21CC ■ NFM18PC ■ NFM18PS ■ NFM21PC
NFL / NFW Series (LC filter)		<ul style="list-style-type: none"> ■ NFL18ST ■ NFL18BT
		<ul style="list-style-type: none"> ■ NFL18SP ■ NFL21SP ■ NFL31SP
NFR Series (PC filter)		<ul style="list-style-type: none"> ■ NFA21SL ■ NFA18SL ■ NFA18SD
		<ul style="list-style-type: none"> ■ NFR21GD ■ NFA31GD
NFE Series (feed through capacitors with some losses)		<ul style="list-style-type: none"> ■ NFE31PT ■ NFE61PT





ECG Monitor EMI Suppression

EMI
Suppression
Effect

NFM18PS Series

- High frequency performance of NFM18PS series

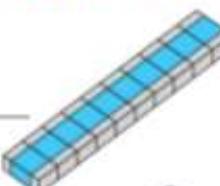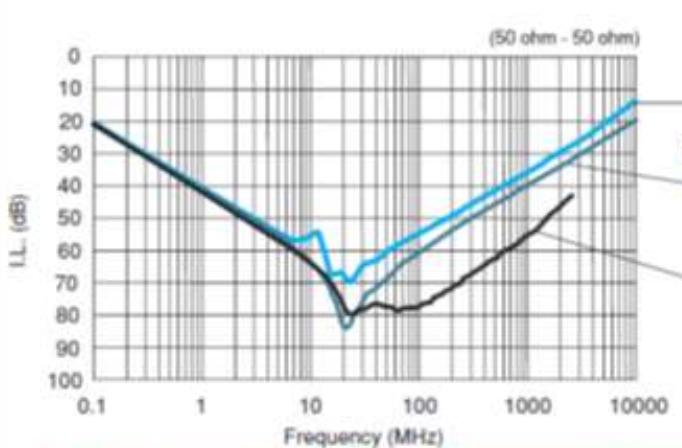

Chip 3-terminal capacitor

2 terminal MLCC: 2012mm size
(0.1 μ Fx10pcs parallel)


NFM18PC105R0J3 1pc
: 1608mm size (1.0 μ Fx1)

NFM18PS105R0J3 1pc
: 1608mm size (1.0 μ Fx1)

NFM18PS series has better high-frequency performance compared to normal chip 3 terminal capacitors.

- Optimize of bypass capacitors using chip 3-terminal capacitor

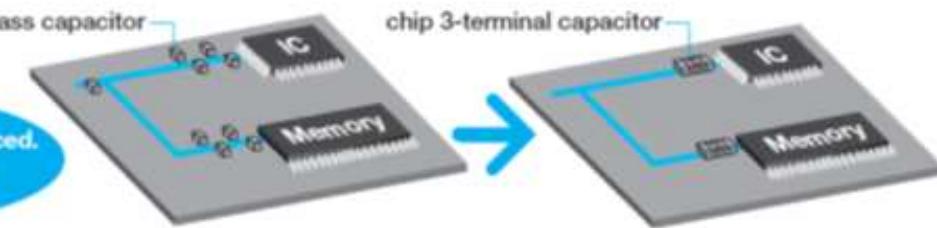
Number of parts can be reduced.
⇒ • Reduce PCB space
• Reduce mount cost



ECG Monitor EMI Supression


Comparison of performance as a bypass capacitor

Without capacitor

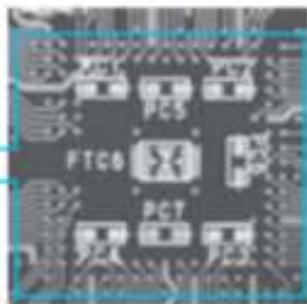


Micro computer

With MLCC 0.22 μ Fx4

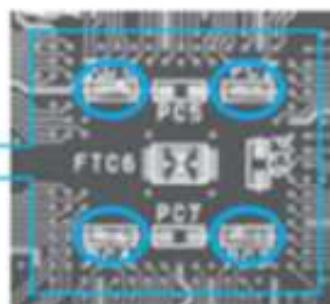




Micro computer

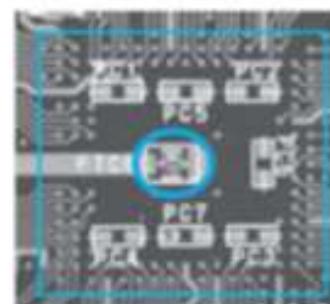With chip 3-terminal capacitor (NFM) 1 μ Fx1



Micro computer

Inner layer power pattern

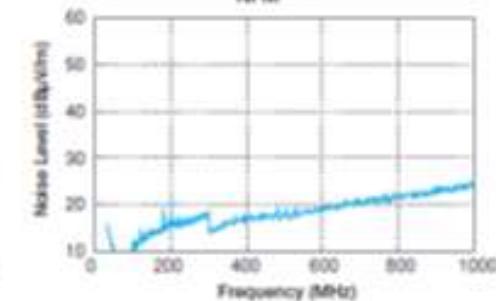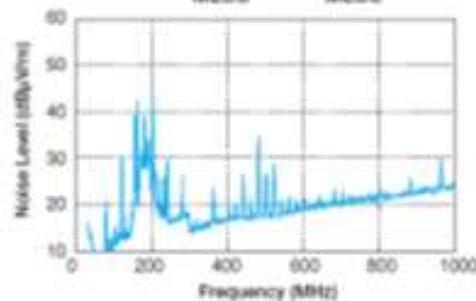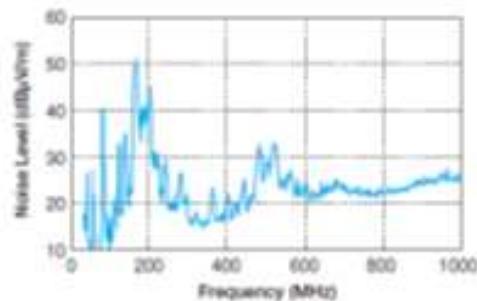

Noise suppression effect of NFM series is better than MLCCs (1 NFM is better than 4 MLCCs).

ECG Monitor EMI Supression


NFM Series Power Lines Type Chip EMIFIL®

NFM18PS Series 0603/1608 (inch/mm)

3-terminal capacitor for power lines whose ground impedance has reduced.


*Please refer to the products designed for both power lines and signal lines.

Dimensions

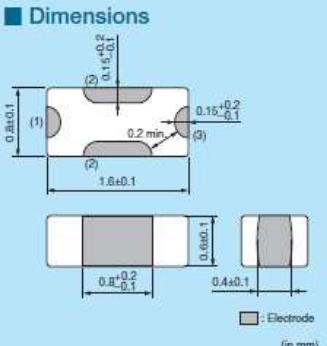(in mm)

Equivalent Circuit

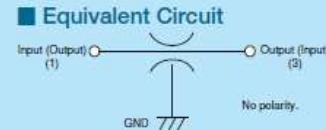

No polarity.

Packaging

Code	Packaging	Minimum Quantity
D	180mm Reel Paper Tape	4000
B	Bulk(Bag)	500


Refer to pages from p.156 to p.162 for mounting information.

■ Rated Value (□: packaging code)


Part Number	Capacitance	Rated Current	Rated Voltage	Insulation Resistance (min.)	Operating Temperature Range	Kit	≥1A
NFM18PS474R0J3□	0.47μF ±20%	2A	6.3Vdc	1000M ohm	-55°C to +125°C	New	Kit ≥1A
NFM18PS105D0J3□	1.0μF ±20%	2A	6.3Vdc	500M ohm	-55°C to +125°C	Kit	≥1A
NFM18PS105R0J3□	1.0μF ±20%	2A	6.3Vdc	500M ohm	-55°C to +105°C	Kit	≥1A

Number of Circuit: 1

■ Insertion Loss Characteristics

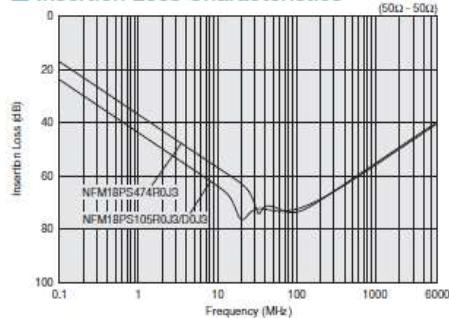

NFM18PS

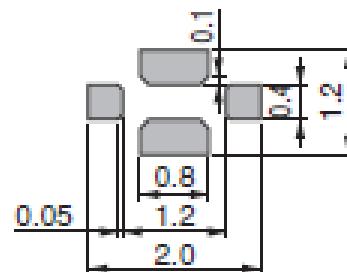


ECG Monitor

EMI Supression


Consider 3 terminal capacitor for power supply

La inclusión de 3-terminal capacitor + capacitor (configuración π) para 3.3 V del conector mikroBus logra atenuar el ruido en frecuencias mayores a 100 KHz que incluye las frecuencias del microcontrolador de la aplicación. Además, protege del ruido de módulos de comunicaciones tipo WiFi y Bluetooth.

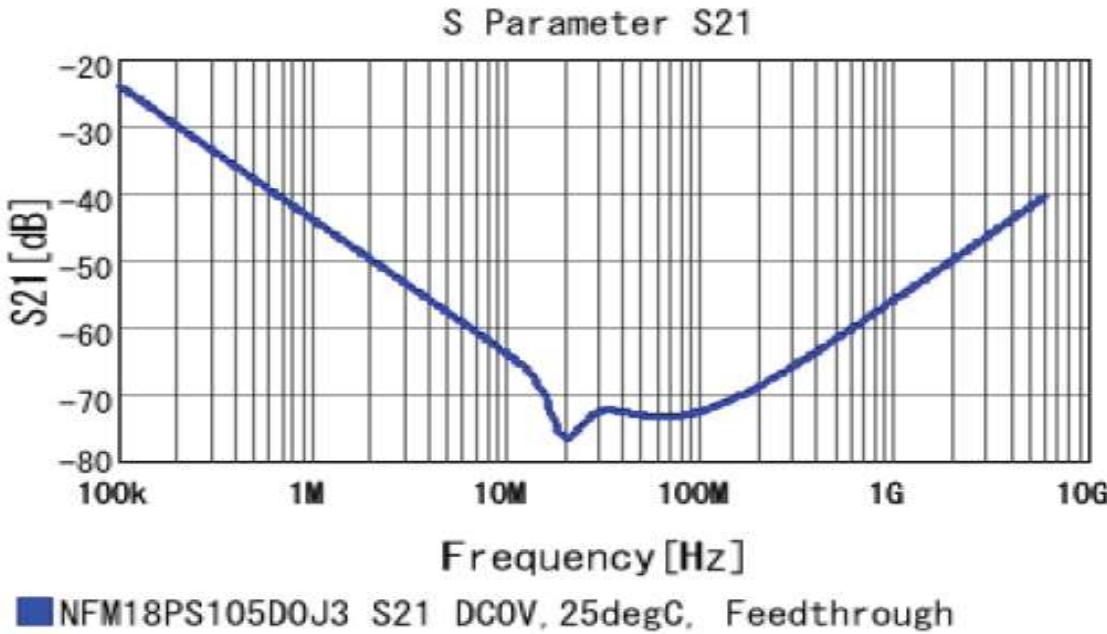Respuesta del NFM18PS105D0J3D sin los condensadores




Configuración tipo π *con condensadores*

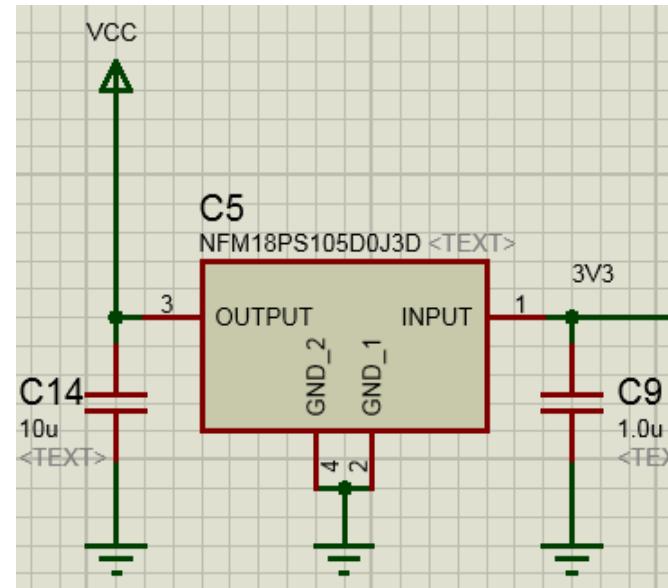

ECG Monitor

Proyecto IIa con Proteus

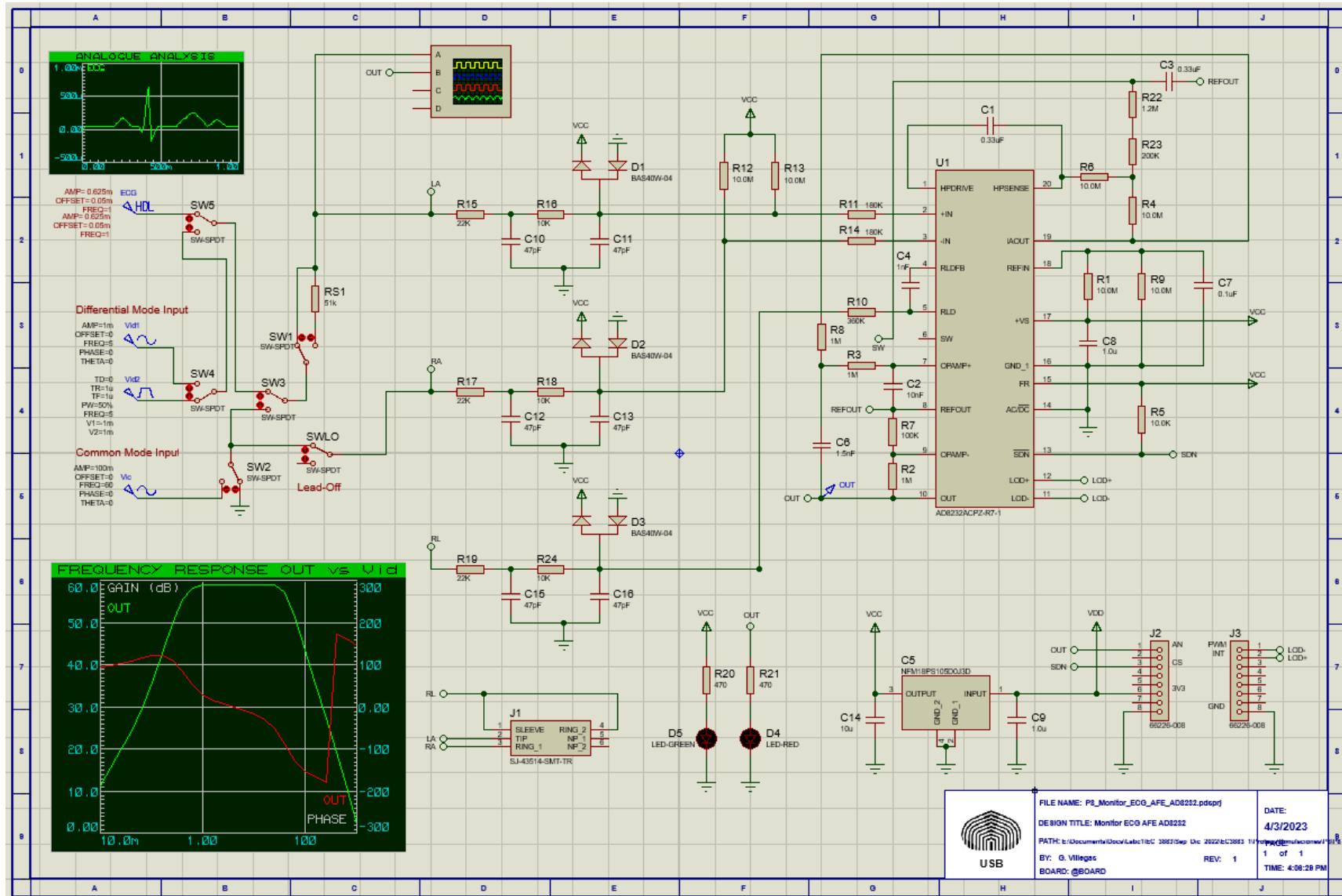Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)



ECG Monitor

Proyecto IIa con Proteus

Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)

Simulaciones:

Caso AD8232:

El modelo Spice no simula completamente el AD8232.

El modelo Spice fue modificado y se consiguió que:

Se produce una salida OUT con ganancia 900 @ 5 Hz y Voffset = 1.64 V.

Los pines del AD8232 que el modelo Spice no soporta correctamente son:

SW, AD_DC, SDN, LOD+, LOD-

Eliminar solo el cable conectado al pin SW:

- Para que la simulación con osciloscopio digital funcione.
- El modelo también funciona para el Bode de amplitud y fase de la ganancia modo diferencial.
- Pero no funciona para el Bode de amplitud y fase de la ganancia modo común.

Exclude from Simulation para osciloscopio digital:

66226-008

BAS40W-04 (produce atenuación)

Exclude from Simulation para GRAPH de frecuencia (Bode de amplitud y fase de la ganancia modo diferencial):

Generador de ECG HDL

BAS40W-04

LED-RED

LED-GREEN

66226-008 (conector header macho)

ECG Monitor

Proyecto IIa con Proteus


Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)

Bode de amplitud y fase de la ganancia modo diferencial Avd = Vo / Vid

Caso pasa bajo: fc = 43.6 Hz

Caso pasa alto: fc = 0.445 Hz.


Avd = 59,1 dB frecuencias medias

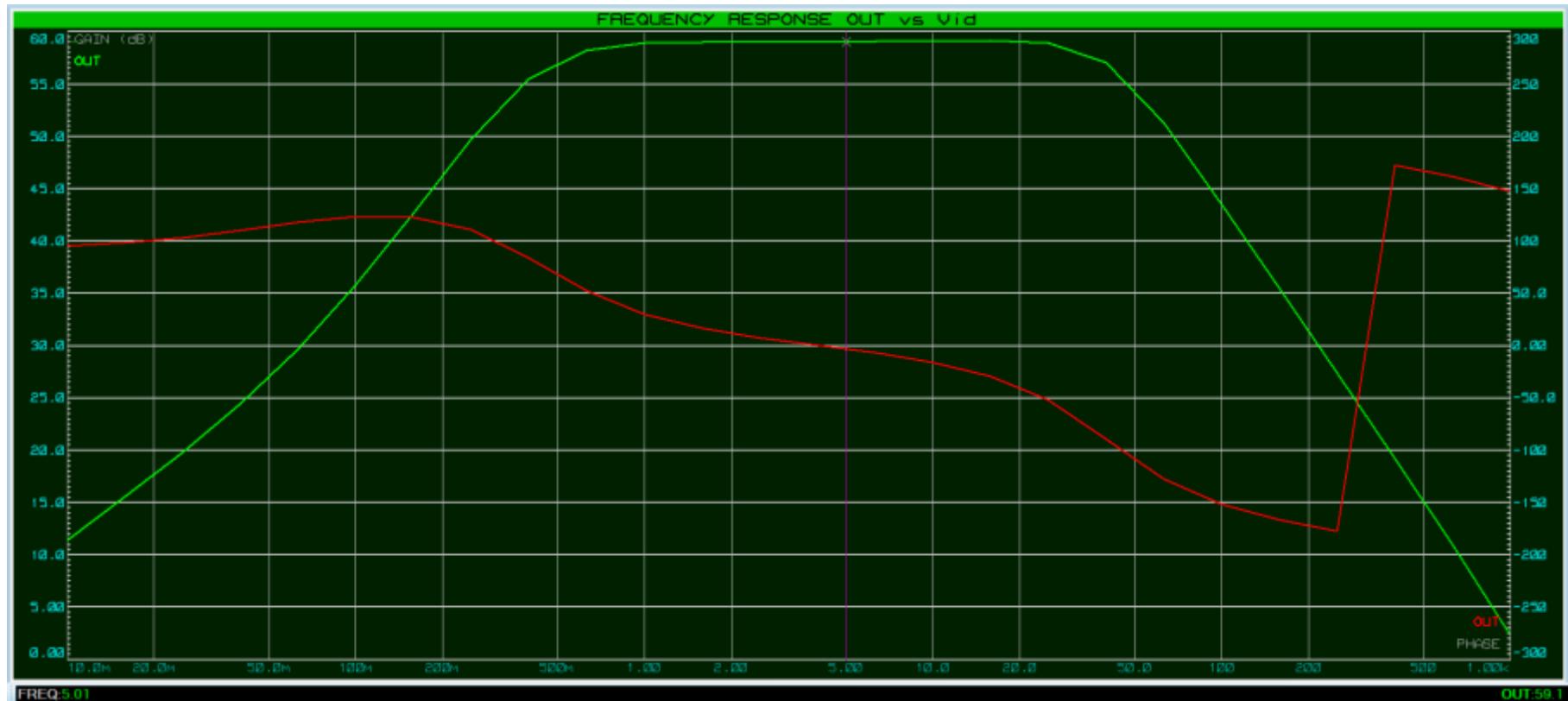

ECG Monitor

Proyecto IIa con Proteus

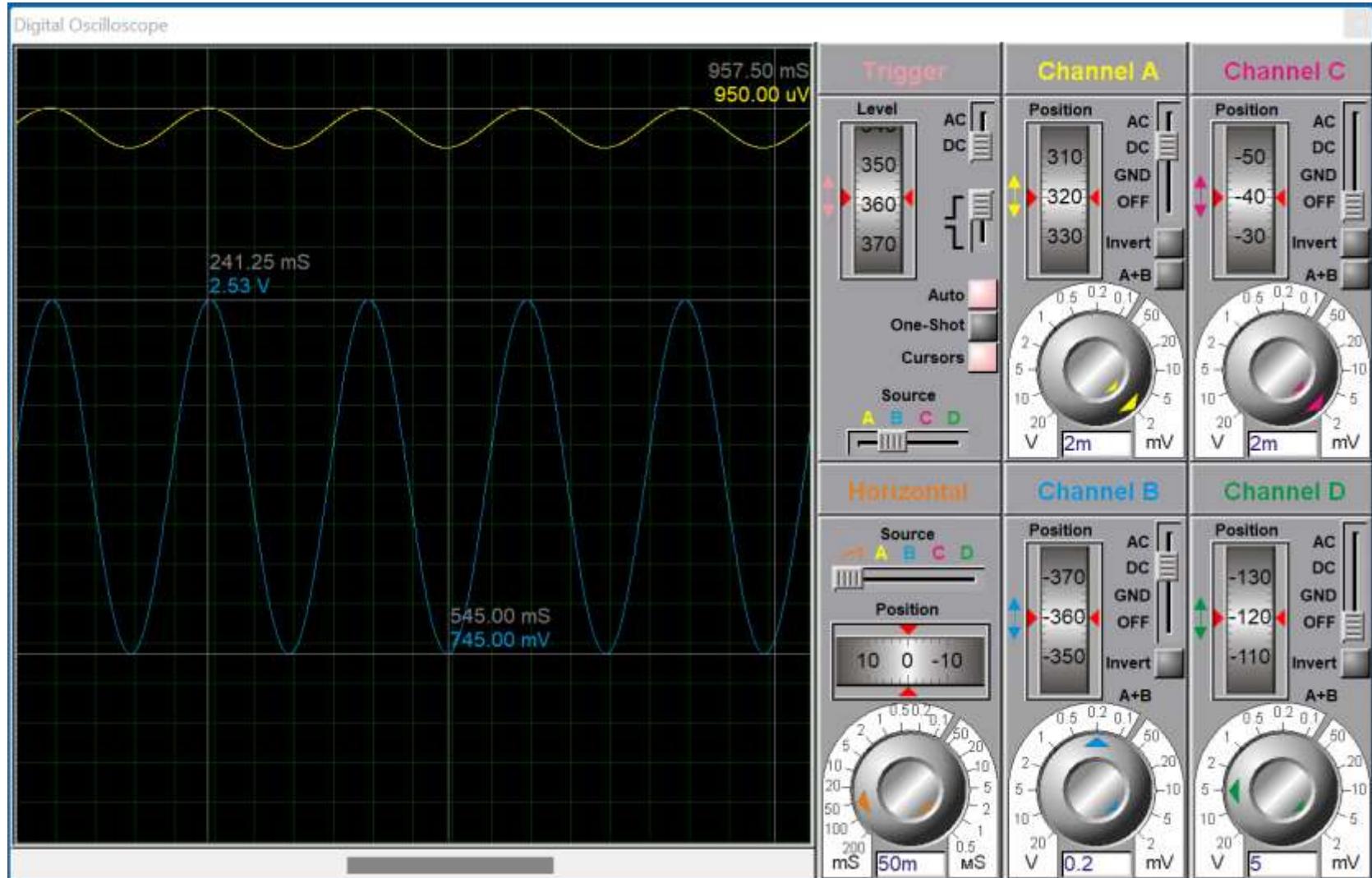Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)
Vid (onda senoidal 1 mVp @ 5 Hz) y Vo (OUT)




ECG Monitor

Proyecto IIa con Proteus

Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)

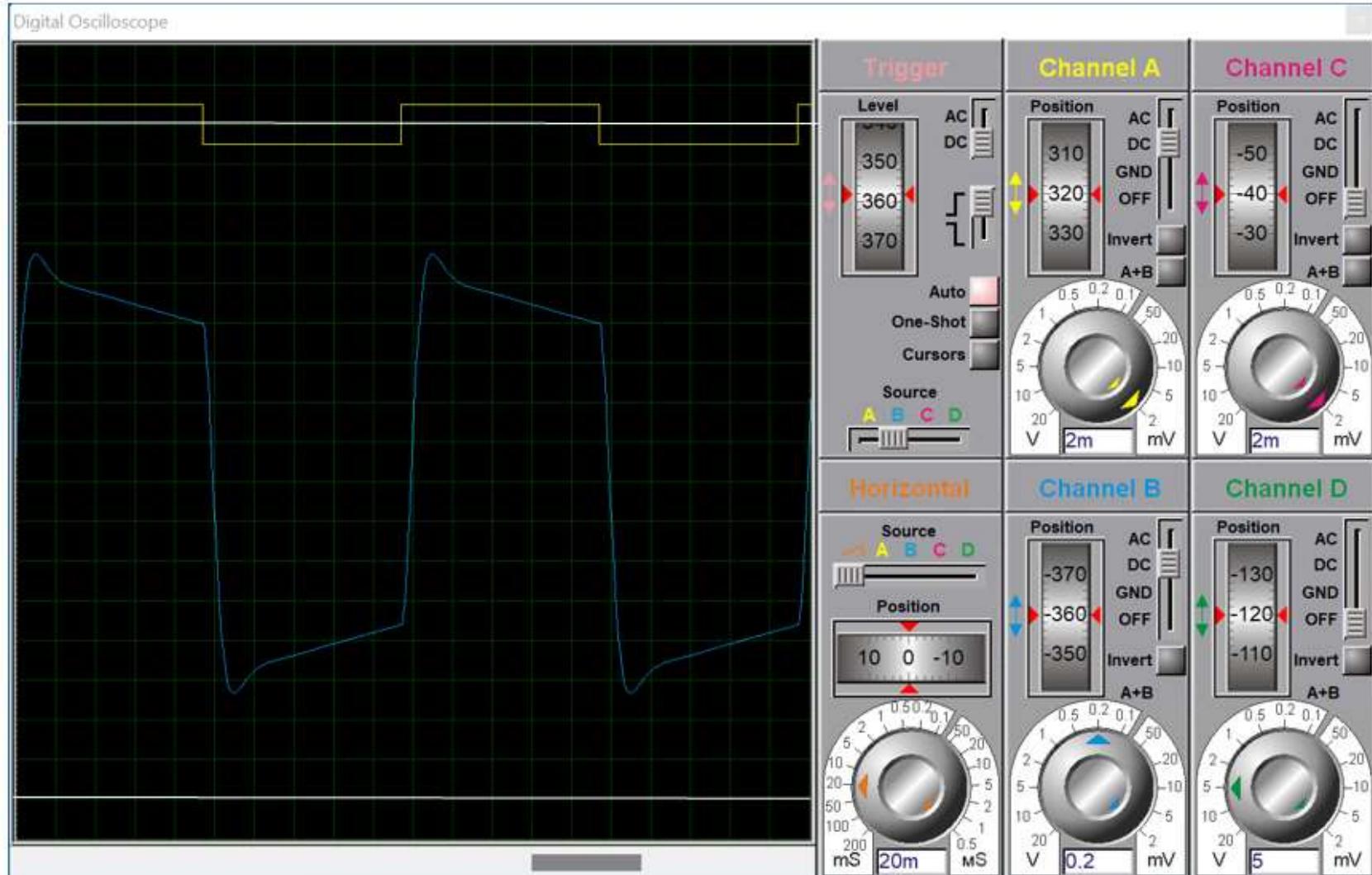
. Vid (onda cuadrada 1 mVp @5 Hz) y Vo (OUT)



ECG Monitor

Proyecto IIa con Proteus

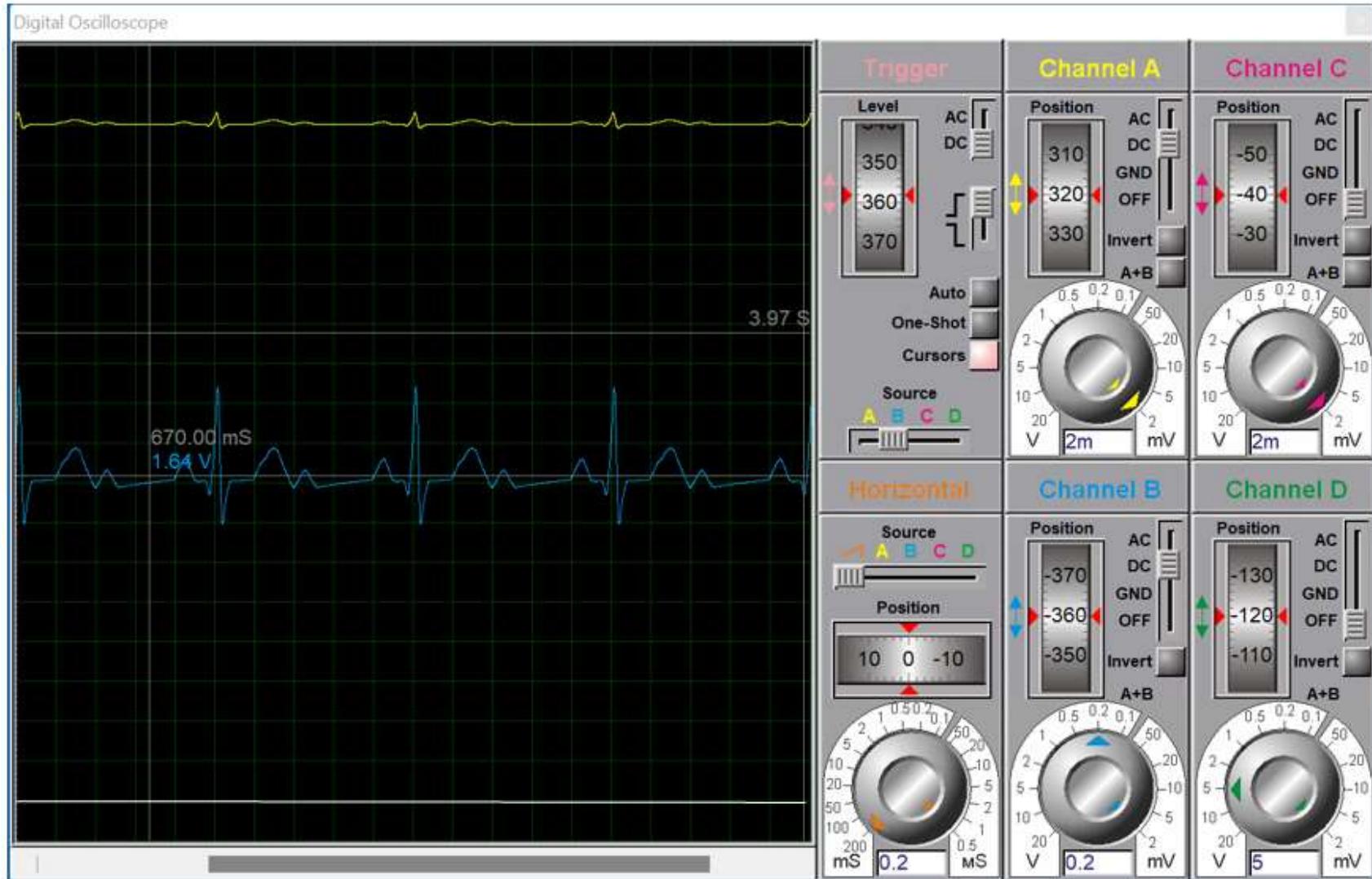Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)
Vid (ECG simulado 0.625 mVp) y Vo (OUT)



ECG Monitor

Proyecto IIa con Proteus

Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8)


BOM

Bill Of Materials for Monitor ECG AFE AD8232									
Design Title	Monitor ECG AFE AD8232								
Author	G. Villegas								
Document Number	1								
Revision	1								
Design Created	Monday, April 3, 2023								
Design Last Modified	Monday, April 3, 2023								
Total Parts In Design	56								
Category	Quantity	References	Value	Stock Code	Unit	Manufacturer	Manufacture Part Number	Description	PCB Package
Capacitors	2	C1,C2	0.33uF	Digitek 399-4195-2-ND	10.10	Kemet	C0603-104K9RACTU	CAP CERAM 33uF 5.0V X7R 0603	CAPC1600x37
Capacitors	1	C3	10uF	Digitek 399-1005-2-ND	10.10	Yageo	CC0603KX7R9BB0103	CAP 1000uF 50V CERAMIC X7R 0603	CAPC1600x37
Capacitors	1	C4	1uF	Digitek 399-1794-1-ND	10.10	Yageo	CC0603KX7R9BB0102	CAP 1000pF 50V CERAMIC X7R 0603	CAPC1600x37
Capacitors	1	C5	NFV18PS10501.00	Digitek 492-1794-1-ND	10.10	Murata Electronics	NFV18PS10501.00	NFV18PS10501.00	NFV18PS10501.00
Capacitors	1	C6	15uF	Digitek 399-1784-1-ND	10.10	Yageo	CC0603KX7R9BB0102	CAP 1500uF 50V CERAMIC X7R 0603	CAPC1600x37
Capacitors	1	C7	0.1uF	Digitek 492-3215-1-ND	10.12	AVX	0603V104KAT2A	CAP CERAM 1uF 10V X7R 0603	CAPC1600x37
Capacitors	2	C8-C9	1uF	Digitek 399-3217-1-ND	10.12	Kemet	C0603C10529VACCTU	CAP 1uF 10V Y5V SMD 0603	CAPC1600x37
Capacitors	6	C10-C13,C15-C16	47pF	Digitek 399-3205-1-ND	10.10	Yageo	CC0603UPNP038N470	CAP CERAMIC 47pF 50V X7R 0603	CAPC1600x37
Capacitors	1	C14	1uF	Digitek 399-3206-1-ND	10.14	Kemet	C0603C10529VACCTU	CAP CERAMIC 1uF 10V Y5V SMD 0603	CAPC1600x37
Resistors	6	R1,R4,R6,R8,R12-R14	10.0M	Digitek 399-1004-1-ND	10.10	Yageo	9C0603A2105PKHFT	PES 10.0M OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	3	R2,R3,R8	1M	Digitek PT100-1000-1-ND	10.10	Panasonic - ECG	ERJ-3GEY-100V	PES 1.0M OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	1	R5	10.0K	Digitek PT10K-HTR1-ND	10.10	Panasonic - ECG	ERJ-3EKF1002V	PES 10.0K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	1	R7	100K	Digitek PT100K-HTR1-ND	10.10	Panasonic - ECG	ERJ-3EKF1003V	PES 100K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	1	R10	360K	Digitek 399-360K-HTR1-ND	10.10	Yageo	9C0603A13603PKHFT	PES 360K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	2	R11,R14	100K	Digitek 399-1004-1-ND	10.10	Yageo	9C0603A11003LHFT	PES 100K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	3	R15,R17,R18	22K	Digitek 399-220K-LT1-ND	10.10	Yageo	9C0603A2202LHFT	PES 22K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	3	R16,R18,R24	10K	Digitek PT10K-LT1-ND	10.10	Panasonic - ECG	ERJ-3GEY-100V	PES 10K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	2	R20-R21	470	Digitek 399-470-1-ND	10.10	Yageo	9C0603A4705LHFT	PES 470 OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	1	R22	1.2M	Digitek PT1.2M-1-ND	10.10	Panasonic - ECG	ERJ-3GEY-100V	PES 1.2M OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Resistors	1	R23	200K	Digitek 399-200K-1-ND	10.10	Yageo	ERJ-3GEY-100V	PES 200K OHM 1W 5% 0603 (1008 metric) SMD	RESC1600x504
Integrated Circuits	1	U1	AD8232ACP2-R1-1	Digitek 399-0.0001-1-ND	10.17	Analog Devices	AD8232ACP2-R1	ANALOG DEVICES - AD8232ACP2-R1 - SIGNAL CONDITIONING	QFN50P40x24x20x21
Diodes	3	D1-D3	BA540W-04	Digitek BA540W-04-1-ND	10.34	Diodes Inc.	BA540W-04-7-F	Schottky -40.0V 0.200A 5.00ns Animated LED model (Red) Animated LED model (Green)	90124-09
Diodes	1	D4	LED-RED	Digitek BA540W-04-1-ND	10.34	Diodes Inc.	BA540W-04-7-F	Animated LED model (Red) Animated LED model (Green)	90124-09
Diodes	1	D5	LED-GREEN	Digitek BA540W-04-1-ND	10.34	Diodes Inc.	BA540W-04-7-F	Animated LED model (Red) Animated LED model (Green)	90124-09
Miscellaneous	1	J1	SJ4354-SMT-TR	Digitek JP-4354S-1-ND	\$1.06	CUI Devices	SJ-4354-SMT-TR	Phone Connectors Audio Jacks 8 Positions Single row Vertical Pin Connector	SJ4354-SMT-TR
Miscellaneous	2	J2-J3	65226-008	Digitek 65226-008-ND				Generic resistor symbol Interactive SPDT Switch (Latched Action)	C0N8_1x8_LFC
Miscellaneous	1	RS1	5%	Digitek 399-000-1-ND					NULL
Miscellaneous	6	SW1-SW5,SW1C,SW-SPDT		Digitek 399-000-1-ND					NULL

ECG Monitor

Proyecto IIa con Proteus

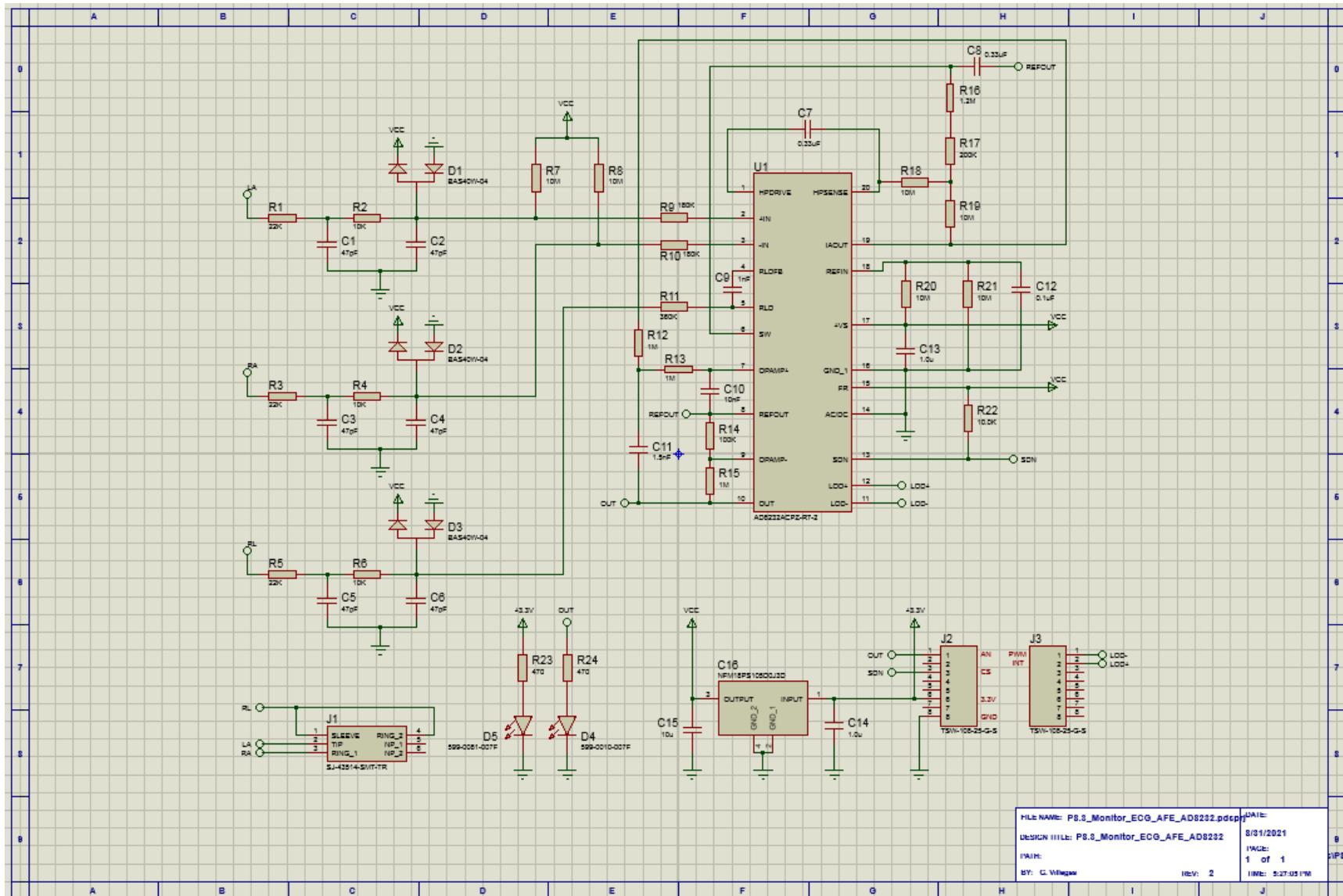Single Lead Heart Rate Monitor (based on AFE TI AD8232) Schematic (P8.3)



ECG Monitor

Proyecto IIa con Proteus


Single Lead Heart Rate Monitor basado en AFE TI AD8232 BOM (P8.3)

Bill Of Materials for P8_Monitor_ECG_AFE_AD8232									
Category	Quantity	References	Value	Stock Code	Unit Cost	Manufacturer	Manufacture Part Number	Description	PCB Package
Capacitors	6	C1-C6	47pF	Digikey 311-1065-1-ND	\$0.10	Yageo	C00603JRNPO9BN470	CAP CERAMIC 47pF 50V NPO 0603	CAPC1608X87
Capacitors	2	C7-C8	0.33uF	Digikey 399-4918-2-ND	\$0.46	Kemet	C0603C334K9RACTU	CAP CERM .33uF 6.3V X7R 0603	CAPC1608X87
Capacitors	1	C9	1nF	Digikey 311-1080-1-ND	\$0.10	Yageo	C00603KRX7R9BB102	CAP 1000pF 50V CERAMIC X7R 0603	CAPC1608X87
Capacitors	1	C10	10nF	Digikey 311-1085-2-ND	\$0.10	Yageo	C00603KRX7R9BB103	CAP 10000pF 50V CERAMIC X7R 0603	CAPC1608X87
Capacitors	1	C11	1.5nF	Digikey 311-1184-6-ND	\$0.10	Yageo	C00603KRX7R9BB152	CAP 1500pF 50V CERAMIC X7R 0603	CAPC1608X87
Capacitors	1	C12	0.1uF	Digikey 478-1239-1-ND	\$0.12	AVX	0603C104KAT2A	CAP CERM .1uF 10V 16V X7R 0603	CAPC1608X87
Capacitors	2	C13-C14	1.0u	Digikey 399-3217-1-ND	\$0.12	Kemet	C0603C105Z9VACTU	CAP 1uF 6.3V CER Y5V SMD 0603	CAPC1608X87
Capacitors	1	C15	10u	Digikey 399-5504-1-ND	\$0.32	KEMET	C0603C106M9PACTU	CAPACITOR, 0603 10uF +/-20% 6.3V	CAPC1608X87
Capacitors	1	C16	NFM18PS105D0J3D	Digikey 490-13394-2-ND	\$0.10	Murata Electronics	NFM18PS105D0J3D	1uF Feed Through Capacitor 6.3V 2A 30mOhm 0603	NFM18CC101R1C3D
Resistors	3	R1,R3,R5	22K	Digikey 311-22KGRCT-ND	\$0.10	Yageo	RC0603JR-0722KL	RES 22K OHM 1/10W 5% 0603 (1608 metric) SMD	RESC1608X50A
Resistors	3	R2,R4,R6	10K	Digikey P10KGCT-ND	\$0.10	Panasonic - ECG	ERJ-3GEYJ103V	RES 10K OHM 1/10W 5% 0603 (1608 metric) SMD	RESC1608X50A
Resistors	6	R7-R8,R18-R21	10M	Digikey P10MGCT-ND	\$0.10	Yageo	ERJ-3GEVJ106V	RESISTOR, 0603 10M Ohms +/-5% 1/10W	RESC1608X50A
Resistors	2	R9-R10	180K	Digikey 311-180KGRCT-ND	\$0.10	Yageo	RC0603JR-07180KL	RESISTOR, 0603 180K Ohms +/-5% 1/10W	RESC1608X50A
Resistors	1	R11	360K	Digikey 311-360KHRCT-ND	\$0.10	Yageo	RC0603JR-07360KL	RESISTOR, 0603 360K Ohms +/-5% 1/10W	RESC1608X50A
Resistors	3	R12-R13,R15	1M	Digikey P1.0MGCT-ND	\$0.10	Panasonic - ECG	ERJ-3GEYJ105V	RES 1.0M OHM 1/10W 5% 0603 (1608 metric) SMD	RESC1608X50A
Resistors	1	R14	100K	Digikey P100KHTR-ND	\$0.10	Panasonic - ECG	ERJ-3EKF1003V	RES 100K OHM 1/10W 1% 0603 (1608 metric) SMD	RESC1608X50A
Resistors	1	R16	1.2M	Digikey P1.2MGCT-ND	\$0.10	Panasonic - ECG	ERJ-3GEYJ125V	RES 1.2M OHM 1/10W 5% 0603 (1608 metric) SMD	RESC1608X50A
Resistors	1	R17	200K	Digikey 311-200KGRCT-ND	\$0.10	Yageo	RC0603JR-07200KL	RESISTOR, 0603 200K Ohms +/-5% 1/10W	RESC1608X50A
Resistors	1	R22	10.0K	Digikey P10.OKHTR-ND	\$0.10	Panasonic - ECG	ERJ-3EKF1002V	RES 10.0K OHM 1/10W 1% 0603 (1608 metric) SMD	RESC1608X50A
Resistors	2	R23-R24	470	Digikey 311-470GRCT-ND	\$0.10	Yageo	RC0603JR-07470RL	RESISTOR, 0603 470 Ohms +/-5% 1/10W	RESC1608X50A
Integrated Circuits	1	U1	AD8232ACPZ-R7-2	AD8232ACPZ-R7TR-ND	\$3.82	Analog Devices	AD8232ACPZ-R7	ANALOG DEVICES - ADACPZ-R7 - SIGNAL CONDITIONING	QFN50P400X400X80-21
Diodes	3	D1-D3	BA540W-04	Digikey BA540W-04FDICT-ND	\$0.34	Diodes Inc.	BA540W-04-7-F	Schottky - 40.0V 0.200A 5.00ns	SOT23-D9
Diodes	1	D4	599-0010-007F	Digikey 350-4346-1-ND	\$0.37	Dialight	5990010007F	Standard LEDs - SMD SMD 0603 RED	LEDC1608X90N
Diodes	1	D5	599-0081-007F	Digikey 350-4351-1-ND	\$0.61	Dialight	5990081007F	Standard LEDs - SMD SMD 0603 GREEN	LEDC1608X90N
Miscellaneous	1	J1	SJ-43514-SMT-TR	Digikey CP-43514SJCT-ND	\$1.06	CUI Devices	SJ-43514-SMT-TR	Phone Connectors Audio Jacks	SJ43514SMTTR
Miscellaneous	2	J2-J3	TSW-108-25-G-S	Digikey TSW-108-25-G-S-ND	\$1.40	Samtec Inc.	TSW-108-25-G-S	8 Position, Single Row, Classic PCB Header Strips, 0.1 in pitch	TSW-108-XX-YY-S

ECG Monitor

Proyecto IIa con Proteus

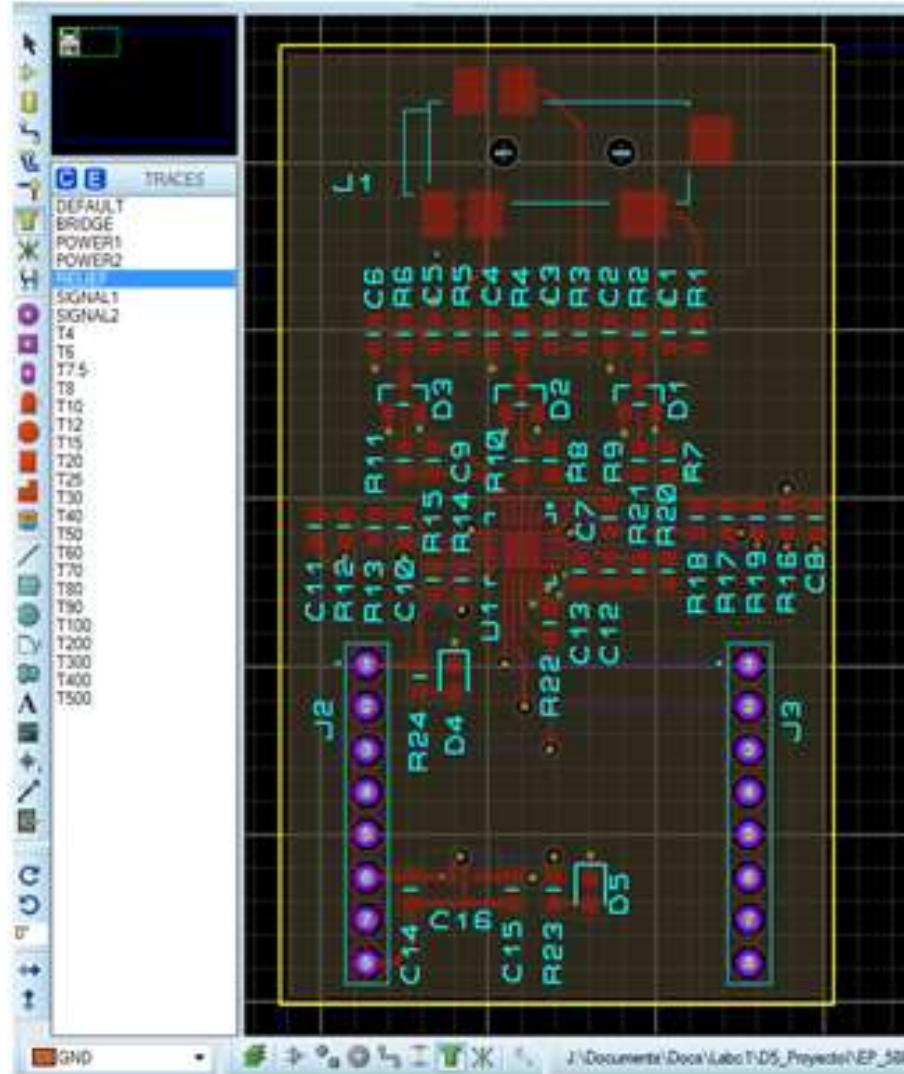Single Lead Heart Rate Monitor basado en AFE TI AD8232 PCB Layout



ECG Monitor

Proyecto IIa con Proteus

Single Lead Heart Rate Monitor basado en AFE TI AD8232 3D Model

